

$\pm 2g$ Acceleration Sensing Module Based on a $\pm 40g$ Integrated Accelerometer

by: Arnaud Delpoux
Application Engineer, Toulouse, France
and
Brandon Loggins
Application Engineer, Phoenix, USA

INTRODUCTION

Micromachined accelerometers, with built-in signal conditioning and calibration are widely used in automotive safety devices such as airbag modules. Automotive applications for accelerometers also include comfort features such as active suspension. For such an application, a $\pm 2g$ accelerometer is required. But most accelerometers

offered today that are able to provide sufficient sensitivity are expensive and/or unavailable in production volumes. With the circuitry described herein, the accelerometer can be used for sensing acceleration in the range of $\pm 2g$, with performance in line with the technical requirements of this application.

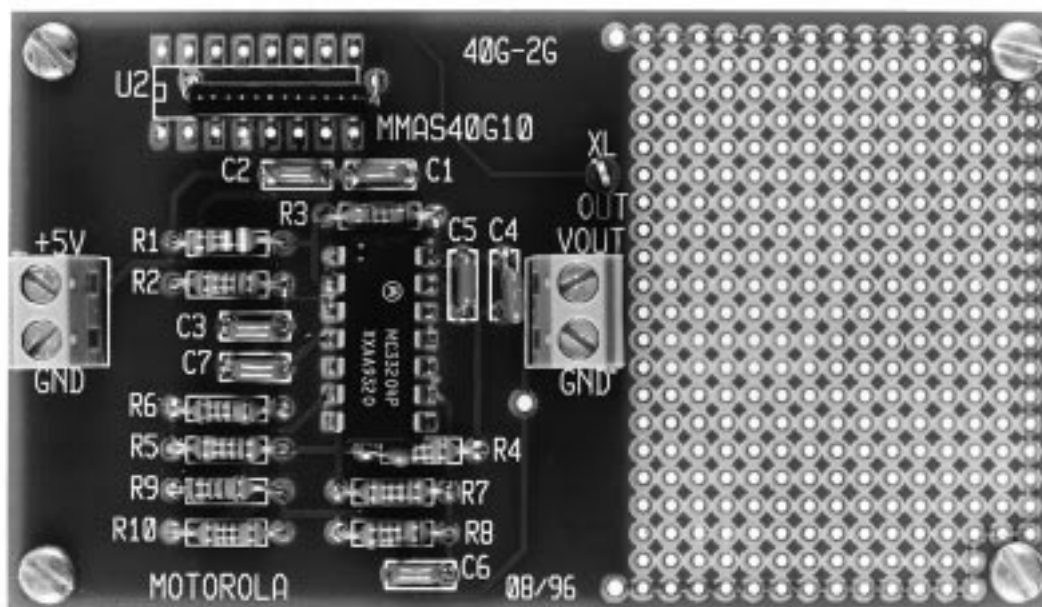


Figure 1. 40G-2G $\pm 2g$ Sensing Module Evaluation Board

EVALUATION BOARD DESCRIPTION

The information required to use evaluation board “40G–2G” follows and a discussion of the design appears in the Design Considerations section.

Function

The evaluation board shown in Figure 1, when supplied with an accelerometer, provides a ±2g full scale acceleration measurement.

The output is an analog signal. It nominally supplies 2.1 volts at zero g and has a sensitivity of 1000 mV/g. It is easily interfaced with a microcontroller’s A/D input.

A through-hole area is provided on the PCB for the designer to add other circuitry as needed.

Electrical Characteristics

The following electrical characteristics are included as a guide to operation.

Characteristics	Symbol	Min	Typ	Max	Units
Supply Voltage	V _{CC}	4.75	5.0	5.25	Volts
Supply Current	I _O	—	7.0	—	mA
Acceleration Range	G	-2.0	—	+2.0	g
Zero G Output	V _{off}	2.0	2.1	2.2	Volts
Sensitivity	ΔV/ΔG	850	1000	1150	mV/g
Low Cutoff Frequency	—	0.8	0.9	1.0	Hz
High Cutoff Frequency	—	4.0	5.0	6.0	Hz
Operating Temperature	T _a	-40	—	+85	°C

Table 1. Electrical Characteristics

Frequency Response

Below is the simulated typical output frequency response using the devices listed in the parts list below. The system provides a gain of 25 over a 5 Hz bandwidth.

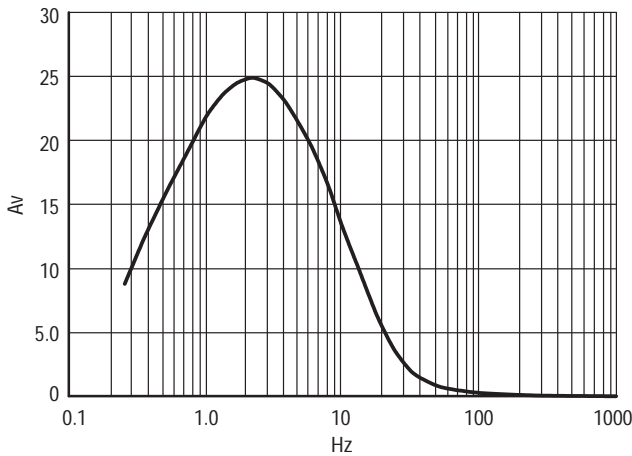


Figure 2. ±2g Biquad Filter with Additional Gain Stage Frequency Response

Evaluation Board Content

Board contents are described in the parts list shown in Table 2. A schematic and silk screen plot are shown in Figures 4 and 5.

Designator	Qty.	Description	Value/Part Number
R1	1	1/4 Watt Resistor	90.9 K
R2, R8	2	1/4 Watt Resistor	162 K
R5, R6, R7, R9, R10	5	1/4 Watt Resistor	11 K
R3, R4	2	1/4 Watt Resistor	432 K
C1–C6	6	Ceramic Capacitor	0.1 μF
U1	1	Quad Rail-to-Rail Op Amp	MC33204P
U2	1	40g Accelerometer	MMA2200W

Table 2. Parts List

DESIGN CONSIDERATIONS

Using a 40g accelerometer to measure ±2g of acceleration can be tricky. Motorola’s accelerometer provides a wide bandwidth of 400 Hz for acceleration sensing. In many low g applications, such as active suspension, the bandwidth requirements are considerably lower. Limiting the bandwidth of the accelerometer can reduce noise. After reducing the bandwidth, gain can be applied to provide higher sensitivity for low g acceleration measurements.

The design challenge is how to bandpass filter the accelerometer’s output with gain using a few low cost components. To accommodate the accelerometer’s wide dynamic range, since the supply voltage is limited to 5 volts, it is necessary to use rail to rail operational amplifiers, such as Motorola’s MC33204P.

In this design, the output signal passes through a biquad filter stage, then through an additional low-pass gain stage to provide ±2g sensing capability. The biquad filter, shown in Figure 3, with some gain, is a good choice for bandpass filtering the accelerometer output when a high quotient factor, Q, is desired. The gain is set by R_g and R_b with the high cutoff frequency being set by R_b and C1. The low cutoff frequency is set by R_f and C2.

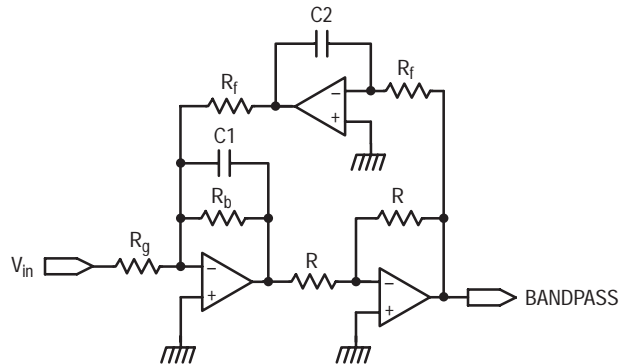


Figure 3. Biquad Active Filter

APPLICATION

Integrating the accelerometer with the biquad amplifier is quite simple. First, in order to minimize the noise level, the accelerometer is properly bypassed, as indicated in the data sheet, with one $0.1\ \mu\text{F}$ ceramic capacitor between V_{CC} (pin 8)

and Ground (pin 7). The self-test feature remains unused in this design. Pin 11 is tied to V_{CC} , as indicated in the data sheet. The output signal is taken on pin 5. The remaining pins of the accelerometer are unused.

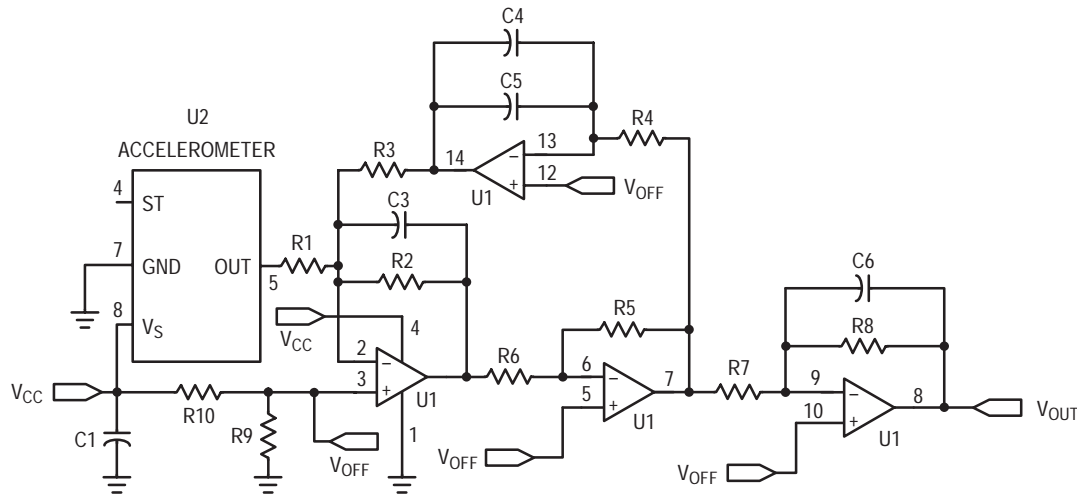


Figure 4. $\pm 2\text{g}$ Acceleration Sensing Module EVB Schematic

In this design, the biquad filter stage gain is set to 1.76 with R_2 ($160\ \text{k}\Omega$) and R_1 ($91\ \text{k}\Omega$). A higher gain cannot be set for this stage, otherwise some operational amplifiers saturate when the accelerometer output drifts over temperature. The upper cutoff frequency is set with R_2 ($160\ \text{k}\Omega$) and C_3 ($0.1\ \mu\text{F}$). Two capacitors, C_4 ($0.1\ \mu\text{F}$) and C_5 ($0.1\ \mu\text{F}$), are needed to set the lower cutoff frequency.

A final low pass filter stage, with a gain of 14.55, brings the overall gain to 25. Resistors R_8 ($160\ \text{k}\Omega$) and R_7 ($11\ \text{k}\Omega$) set the gain. The amplifier is low passed with C_6 ($0.1\ \mu\text{F}$) to remove any high frequency noise in the signal. The output can then be connected to a microcontroller's A/D converter by a simple direct connection from the evaluation board analog

output V_{OUT} to the A/D input. Using the MC68HC11 as an example, the output is connected to any of the E ports.

Since the accelerometer signal passes through 3 inverter stages, the positive direction of acceleration is reversed.

CONCLUSION

Perhaps the most noteworthy aspect to the $\pm 2\text{g}$ sensing module described here is the ease with which it can be designed. Only two dual, or one quad, operational amplifier and a few resistors and capacitors are required. The result is a simple and inexpensive circuit that is capable to measure acceleration within the range of $\pm 2\text{g}$ with an analog output that can be directly interfaced to a microcontroller.

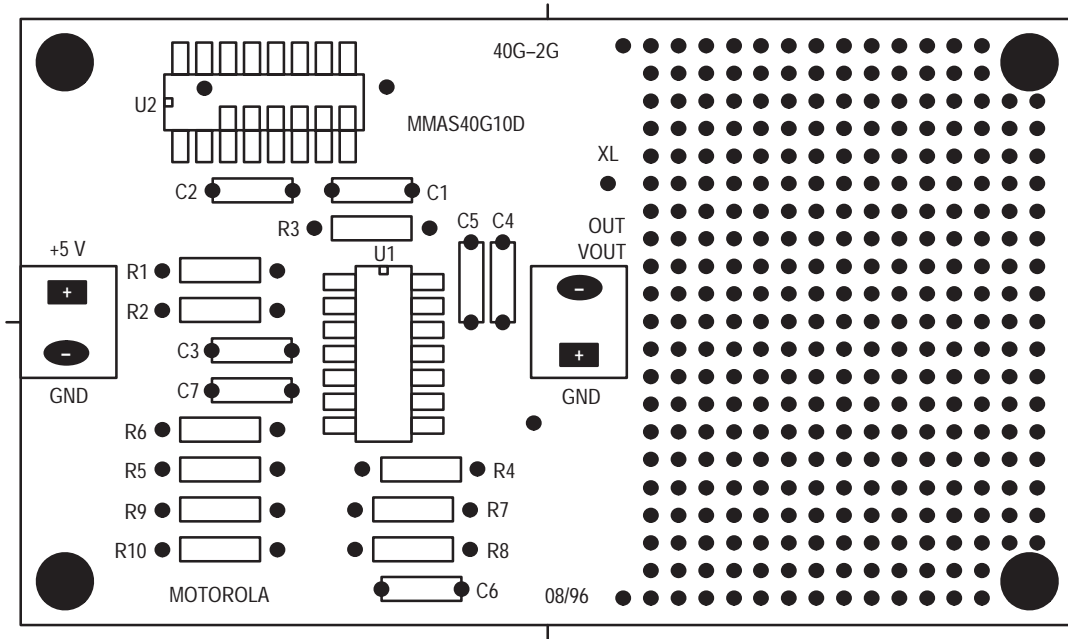



Figure 5. Silk Screen

Mfax is a trademark of Motorola, Inc.

Motorola reserves the right to make changes without further notice to any products herein. Motorola makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does Motorola assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation consequential or incidental damages. "Typical" parameters which may be provided in Motorola data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. Motorola does not convey any license under its patent rights nor the rights of others. Motorola products are not designed, intended, or authorized for use as components in systems intended for surgical implant into the body, or other applications intended to support or sustain life, or for any other application in which the failure of the Motorola product could create a situation where personal injury or death may occur. Should Buyer purchase or use Motorola products for any such unintended or unauthorized application, Buyer shall indemnify and hold Motorola and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that Motorola was negligent regarding the design or manufacture of the part. Motorola and  are registered trademarks of Motorola, Inc. Motorola, Inc. is an Equal Opportunity/Affirmative Action Employer.

How to reach us:

USA/EUROPE/Locations Not Listed: Motorola Literature Distribution; P.O. Box 5405, Denver, Colorado 80217.
1-303-675-2140 or 1-800-441-2447

JAPAN: Motorola Japan Ltd.; SPS, Technical Information Center, 3-20-1, Minami-Azabu, Minato-ku, Tokyo 106-8573 Japan.
81-3-3440-3569

ASIA/PACIFIC: Motorola Semiconductors H.K. Ltd.; Silicon Harbour Centre, 2 Dai King Street, Tai Po Industrial Estate, Tai Po, N.T., Hong Kong. 852-26668334

Customer Focus Center: 1-800-521-6274

Mfax™: RMFAX0@email.sps.mot.com – TOUCHTONE 1-602-244-6609
Motorola Fax Back System – US & Canada ONLY 1-800-774-1848
– http://sps.motorola.com/mfax/

HOME PAGE: <http://motorola.com/sps/>