

Here's a nifty construction project that will improve the quality of your signal without adding an extra watt.

Build Your Own Microphone Equalizer

BY CORNELIO NOUEL*, KG5B

It is a proven fact that speech frequencies between about 200 Hz and 4000 Hz contribute the most to intelligibility. Frequencies above and below these limits serve mainly to give identity or personality to the individual's voice.

In order to save frequency spectrum, present-day communication equipment restricts the bandwidth of the audio channel to those essential frequencies, both on transmit and receive. Under ideal conditions an overall flat frequency response will provide the best results; however, there are times when some intervening factor, such as the operator's voice or the microphone response or room acoustics, may affect the clarity required, especially under noisy conditions.


The unit described here, although not a cure-all, will help to modify the response of the audio to be transmitted within the passband of the equipment.

Description

The equalizer is a very simple and inexpensive unit. It can be built in a couple of evenings by practically anyone with a little experience. The circuit consists of a preamplifier, a low-frequency network, and a high-frequency network. These are also called **bass** and **treble** networks.

The amplifier provides about 30 dB gain, while the network losses add up to about 10 dB. Therefore, 20 dB of extra gain is available to compensate for variations in microphone levels.

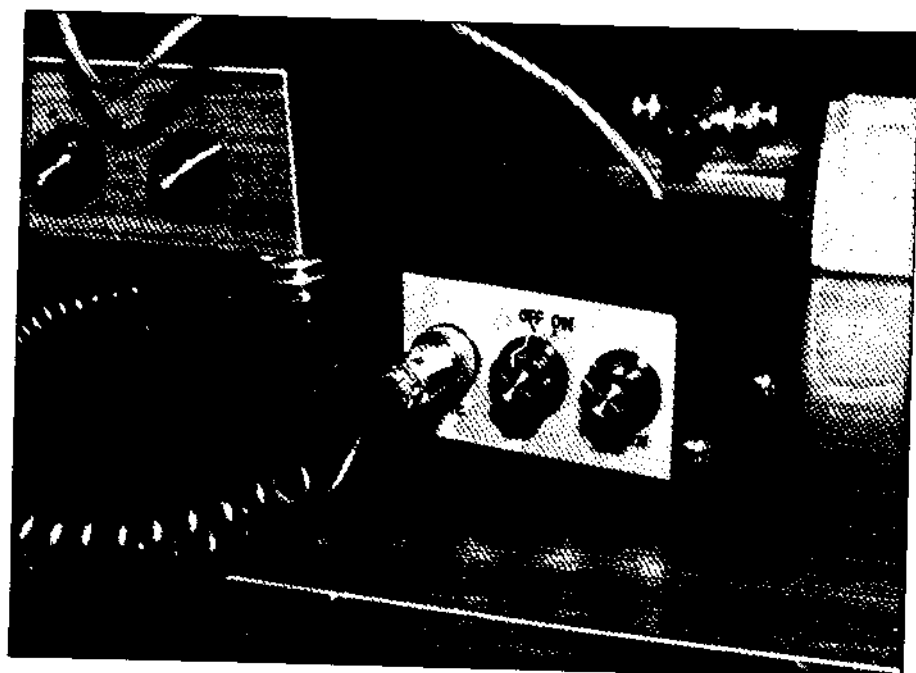In the schematic diagram (fig. 1) R5 controls the low frequencies, while R9 controls the high frequencies. The action of each control is quite independent of the other controls. The amount of **boost** or **cut** can be appreciated from the frequen-



Front view of the microphone equalizer.

cy response chart (fig. 4), which is an actual plot of the unit shown in the photograph and the schematic. A 20 dB spread is possible within the normal communications passband. R10 is a 10K ohm audio taper potentiometer which adjusts the output level of the equalizer so that it will not exceed the required amount.

The input signal goes through selector switch S1, a three-pole two-position rotary switch which selects the **In** or **Out** operation. This switch also turns the battery on or off. Battery current drain is only about a half ma at 9 volts. The equalizer will work with microphones with impedances from a few hundred to several thousand ohms.

When the **bass** and **treble** controls are set at their mid-position, the overall re-

sponse of the unit is virtually flat from 20 Hz to over 20,000 Hz with little distortion.

To prevent r.f. feedback, the input circuit is provided with an LC low-pass filter consisting of a 330 μ Hy miniature ferrite-core choke and a 270 pF capacitor. No r.f. feedback has been observed while operating on the h.f. bands using a tuned antenna system and 100 watts output.

The 2N3390 transistor shown in the diagram is a high-gain, low-noise, audio-type NPN, but there is no reason why similar transistors cannot be substituted (for example, the RCA SK3245, or equivalent).

Construction

My equalizer was built in a small metal cabinet (Radio Shack Cat. # 270-251) to

*1445 W. Saint Francis, Brownsville, TX 78520

Attention Moonbouncers and Satellite Communications Enthusiasts

Introducing New Ultra High Performance Antennas from KLM Electronics, Inc.

KLM Electronics is fueling the Moonbounce and Oscar 10 revolution with Antenna Equipment that delivers truly Out-of-This-World performance.

For the Moonbouncer, our New 2M-16LBX is designed to be the highest gain 2 meter antenna available on the market today by more than a full db, making the 2M-16LBX an outstanding performer as a single antenna or in Moonbounce (EME) arrays.

The New 432-30LBX follows the same pattern as the 2M-16LBX, and soon will become the industry's standard of comparison.


Featuring straight forward construction, and an innovative tapered boom that greatly reduces windload and adds strength and durability. Virtually unbreakable, insulated, 3/16" rod parasitic elements are anchored through the boom to insure years of trouble-free performance.

For the satellite enthusiasts, the 2M-22C high gain 2 meter, circular polarized antenna, features the same rugged construction and total flexibility as our very popular 2M-14C with a 2db increase in gain.


Four or more 2M-22Cs make an excellent array for Moonbounce (EME) by eliminating Faraday fading.

Fiberglass/aluminum stacking frames are available as well as 2 and 4 port power dividers and phasing harnesses to optimize the performance of these type arrays.

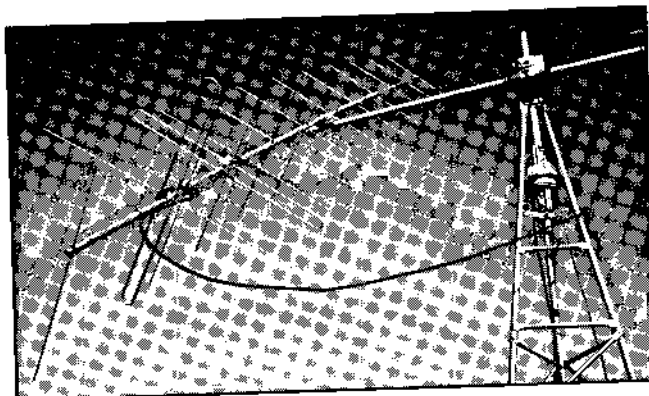Watch for our new elevation drive system coming soon.




2M-22C	
BANDWIDTH	144-148 MHz
*GAIN	13 dBdc
BEAMWIDTH	(E) 32°, (H) 32°
FEED IMP	50 ohms unbal.
BALUN	(2) 4:1 coaxial
BOOM LENGTH	19 ft. 1 in. (tapered)
VSWR	1.5:1
WINDLOAD	1.85 sq. ft. max.
ELLIPTICITY	± 1.5 dB max.
CIRCULARITY SWITCHER	CS-3 included
WT. (lbs.)	11 lbs.

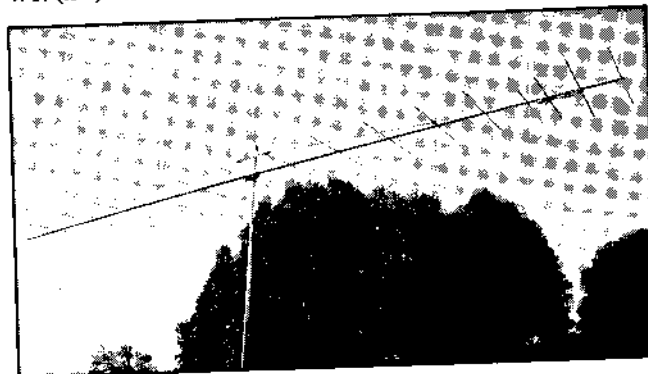

2M-16LBX	
BANDWIDTH	144-146 MHz
*GAIN	(144 MHz) 14.5 dBd
BEAMWIDTH	(E) 26°, (H) 29°
FEED IMP	50 ohms unbal.
BALUN	4:1 coaxial, 2 KWPEP
BOOM LENGTH	28 ft. 1 in. (tapered)
VSWR	1.5:1
WINDLOAD	(H) 1.75 sq. ft. (V) 2.44 sq. ft. max.
WT. (lbs.)	10 lbs.
TURNING RADIUS	15 ft. 5 in.

See the complete line of KLM antennas and equipment at your local dealer, or write for our catalog.

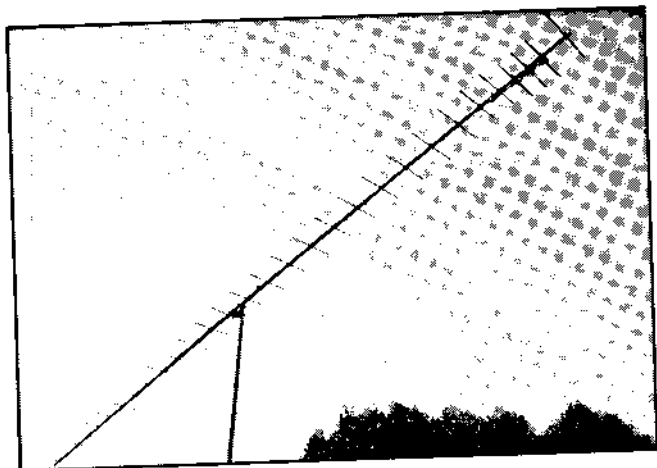*To provide a more accurate and consistent gain figure, performance of this KLM antenna has been carefully measured and correlated in accordance with National Bureau of Standards Note #688. This gain figure may appear somewhat conservative when compared with others commonly found in conventional industry literature and based on older, less exacting rating methods.



432-30LBX	
BANDWIDTH	430-440 MHz
*GAIN	17.3 dBd
BEAMWIDTH	(E) 19°, (H) 20°
FEED IMP	50 ohms unbal.
BALUN	included
BOOM LENGTH	21 ft. 11 in.
F/B	20 dB F/S
VSWR	1.5:1
WINDLOAD	1.71 sq. ft. (max.)
TURNING RADIUS	12 ft. 4 in.
WT. (lbs.)	9 lbs.

KLM electronics, Inc.
P.O. Box 816
Morgan Hill, CA 95037

Say You Saw It In CQ

July 1984 • CQ • 23


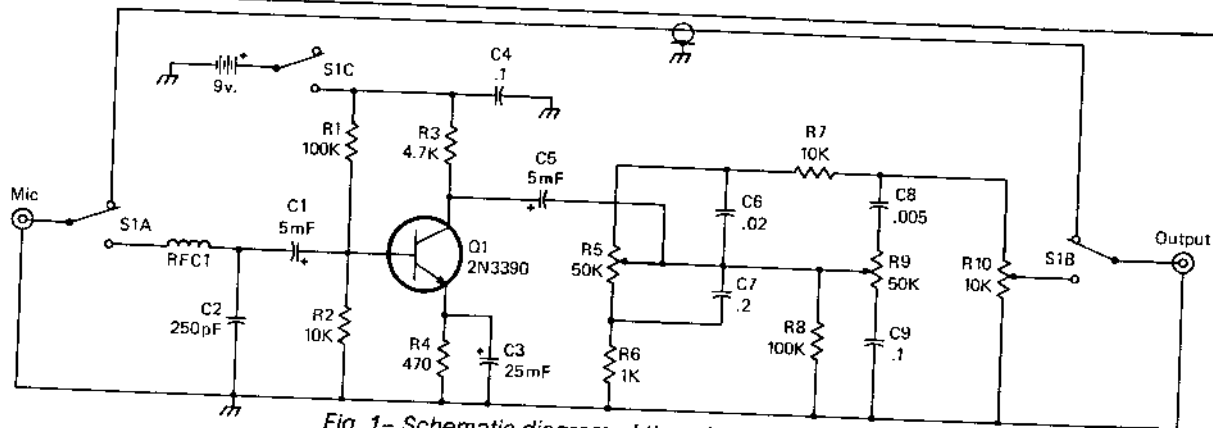


Fig. 1— Schematic diagram of the microphone equalizer.

Parts List

- | | | | |
|--------|-----------------------------------------------------------|--------|--------------------------------------------------------------------------------------------------------------------------------------------|
| C1, C5 | 4.7 μ F 16 volt electrolytic or tantalum | R5, R9 | 50K ohms carbon pot, linear taper |
| C2 | 270 pF 50 volt ceramic or similar | R6 | 1K ohm $\frac{1}{4}$ watt |
| C3 | 22 μ F 16 volt electrolytic or tantalum | R7 | 10K ohms $\frac{1}{4}$ watt |
| C4, C9 | .1 μ F 50 volt metal film, PC-mount type or similar | R8 | 100K ohms $\frac{1}{4}$ watt |
| C6 | .022 μ F 50 volt metal film, PC-mount type or similar | R10 | 10K ohms, carbon pot, audio taper |
| C7 | .22 μ F 50 volt metal film, PC-mount type or similar | S1 | 3-pole 2-position rotary switch |
| C8 | .005 μ F 50 volt metal film or ceramic | Q1 | 2N3390 transistor or equivalent (see text) |
| R1 | 100K ohms $\frac{1}{4}$ watt | RFC1 | miniature ferrite-core choke 300-500 μ Hy (not critical) |
| R2 | 10K ohms $\frac{1}{4}$ watt | Misc. | circuit board, cabinet, knobs, battery, hook-up wire, small-diameter shielded wire (RG174U coax), hardware, microphone, output jacks, etc. |
| R3 | 4.7K ohms $\frac{1}{4}$ watt | | |
| R4 | 470 ohms $\frac{1}{4}$ watt | | |

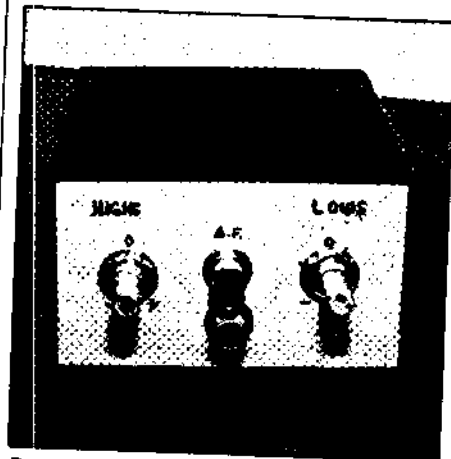

Rear view of the equalizer. You can add knobs to the controls if you want to.

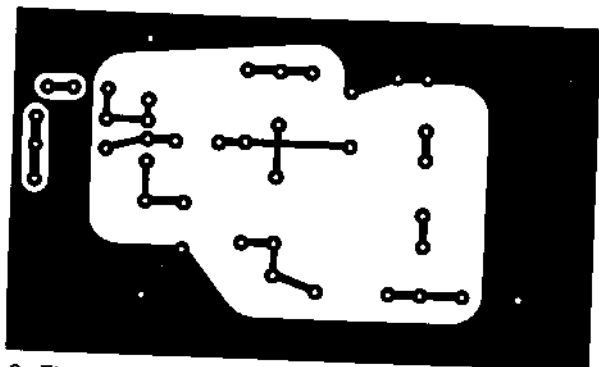


Fig. 2— The equalizer PC board as seen from the foil side. This is shown actual size.


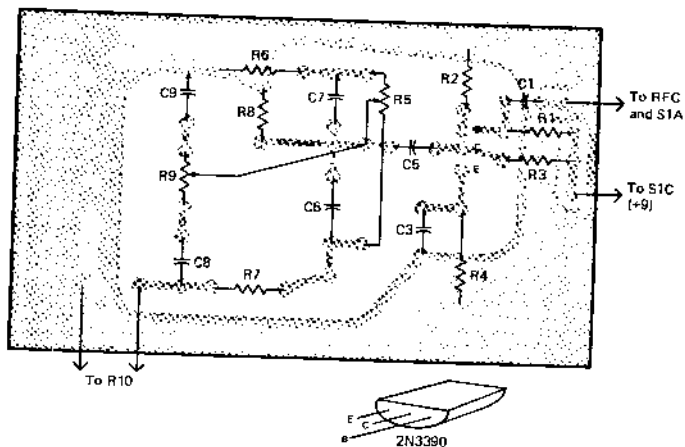


Fig. 3— The PC board shown from the component side. This is also the parts placement.

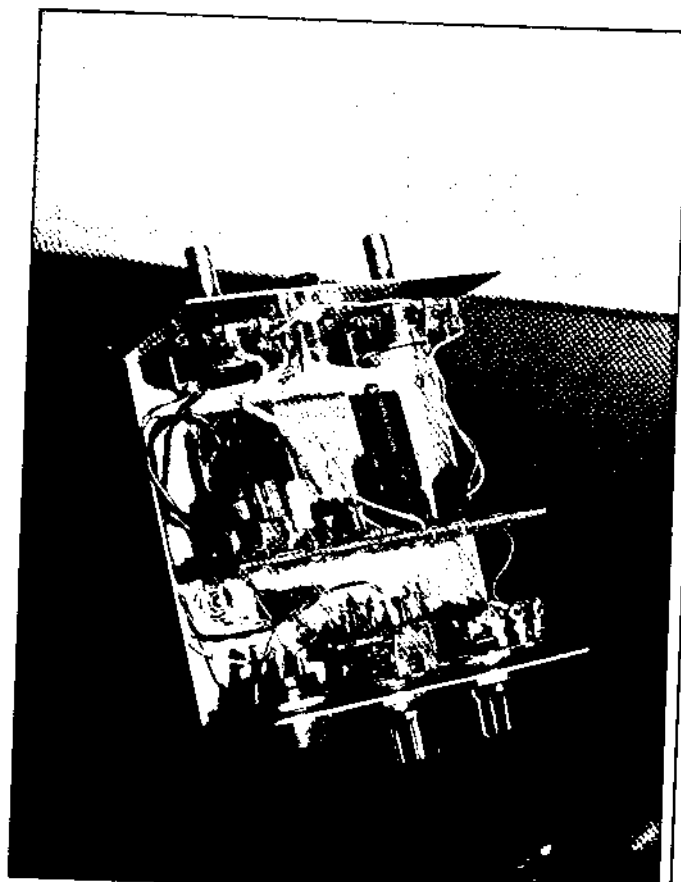

Interior view of the equalizer showing the PC board and the point-to-point construction.

ANTENNAS & TOWERS

Cushcraft

A3 3-element 10-15-20m Triband	215.95
A4 4-element 10-15-20m Triband	279.95
R3 10-15-20m Vertical	269.95
214B SSB/214FB FM 2m Boomers	77.95
ARX-2B 2m Ringo Ranger	36.50
A3219 2m Boomer	90.95
410B 10-element 432-435 MHz	54.95
424B 24-element 435-437 MHz	76.95
10-4CD 4-element 10m	104.95
15-4CD 4-element 15m	118.95
40-2CD 2-element 40m	279.95
Other Cushcraft models available	CALL

TELEX hy-gain

391S TH7DX 7-ele 10-15-20m Triband	412.95
393S TH5DX 5-ele 10-15-20m Triband	355.95
398S Explorer 14 10-15-20m Triband	269.95
203 3-element 2-meter Beam	16.95
208 8-element 2-meter Beam	28.95
214 14-element 2-meter Beam	34.75
BN86 Beam Bahun	16.50
V2S 2-meter Vertical	37.50
V4S 440 MHz Vertical	55.95
Other Hy-Gain models available	CALL

KLM

KT34A 4-element 10-15-20m Triband	337.95
KT34XA 6-element 10-15-20m Triband	485.95
2M-13LBA 13-element 2-meter	78.95
432-16LB 16-element 430 MHz	64.95
CS-2 Polarity Switcher	50.95

M-E-I

Mosley Electronics, Inc.

CL-33 3-element Triband Beam	269.95
TA-33 3-element 10-15-20m Triband	242.95
Pro 37 7-element 10-15-20m Triband	468.95
RV-4C 10-40m Vertical	CALL

HUSTLER

6-BTV 10-80m Vertical with 30m	126.95
5-BTV 10-80m Vertical	107.95
4-BTV 10-40m Vertical	84.95
MO-1/MO-2 Mast	19.95
BM-1 Bumper Mount	15.50
CG-144B 2-meter Base Vertical	76.95
G7-144 2-meter Base Vertical	112.50
CG-440 440 MHz Base Vertical	89.95
MOBILE RESONATORS	Standard Super
10 and 15 meter	10.95 16.95
20 meters	14.50 20.85
30 and 40 meters	16.95 22.95
75 meters	18.95 34.95

AEA ISOPOLES	
144 2-meter Antenna	41.95
220 220 MHz Vertical	41.95
440 440 MHz Vertical	57.95

MORE ANTENNAS	
AVANTI HM 151.3G 2m On-glass	30.95
LARSEN LM-150 5/8 Mag Mount	38.95
MINIQUAD HQ-1	147.95
BUTTERNUT HF6V 10-80m Vertical	114.95
BUTTERNUT 2M CVS 2m	37.50
VOCOM 5/8-wave 2m Handheld	14.95

ANTENNAS FOR OSCAR	
Cushcraft 416TB Twist	58.95
Cushcraft A14410T 10-ele	48.95
Cushcraft A14420T 20-ele	69.95
Cushcraft AOP1 Package	139.95
KLM 2m-14C 2m 14-ele Circular	88.95
KLM 435-18C 18-ele Circ Polar	65.95

ege, inc.

Prices subject to change without notice or obligation

13646 Jefferson Davis Highway
Woodbridge, Virginia 22191
(703) 643-1063
Order Hours: M-F 11 a.m.-7 p.m.
Saturday 10 a.m.-4 p.m.

Unarco-Rohn

Self-supporting towers:	
HBX40 40-feet with Base	201.60
HBX48 48-feet with Base	276.20
HBX56 56-feet with Base	350.00
HDBX40 40-feet/higher load	253.95
HDBX48 48-feet/higher load	344.30

Guyed foldover towers:	
FK2548 48-feet, 25G	825.00
FK2558 58-feet, 25G	891.00
FK2568 68-feet, 25G	924.00
FK4544 44-feet, 45G	1185.00
FK4554 54-feet, 45G	1254.00
FK4564 64-feet, 45G	1353.00

Foldovers shipped freight paid.
10% higher west of the Rockies.

Straight Sections:	
20G Straight Section	33.85
20AG Top Section	37.45
25G Straight Section	47.25
25AG 2, 3, 4 Top Section	60.75
45G Straight Section	110.10
45AG 3, 4 Top Section	120.15
25G Foldover Double Guy Kit	306.00
45G Foldover Double Guy Kit	324.00

TELEX hy-gain

HG37SS 37-feet tall	627.95
HG52SS 52-feet tall	903.95
HG54HD 54-feet/higher load	1458.95
HG70HD 70-feet/higher load	2323.95

Shipped freight paid. Order Hy-Gain tower, Hy-Gain antenna, and Hy-Gain rotor to receive free shipping on all.



W36 36-feet tall	549.00
WTS1 51-feet tall	929.00
LM354 54-feet/higher load	1575.00
DXB6 86-feet/motor/highest load	Call

Shipping not included. Shipped direct from factory to save you money.

TOWER ACCESSORIES	
3/16" EHS Guywire	18¢/ft
1/4" EHS Guywire	20¢/ft
3/8 x 6 Turnbuckle	9.50
1/2 x 12 Turnbuckle	17.60
Insulators 504	3.60
1/2 x 12 Base Bolt	2.90
3/4 x 12 Pier Pin	2.90

ROTORS	
Alliance HD73	97.95
Hy-Gain CD45 II	124.95
Hy-Gain Ham IV	195.95
Hy-Gain Tailtwister T2X	245.95
Hy-Gain Heavy-duty 300	474.95

CABLE BY SAXTON	
RC213 Mil Spec	29¢/ft
RC9/U Foam 95% Shield	25¢/ft
8-wire Rotor 2 #18, 6 #22	17¢/ft
Mini-8	13¢/ft
HARDLINE BY CABLEWAVE	CALL

PACKAGES

Call for Special Pricing on Tower/Antenna Packages
Ask for Don

Orders & Quotes Toll Free:
800-336-4799
In Virginia: 800-572-4201
Dealer Inquiries Invited



provide shielding and other conveniences, but any similar metal enclosure will do.

The circuit is quite simple and requires no special precautions. I used a 1 3/4" by 3" piece of perforated board with point-to-point wiring. A PC circuit board can be made from the drawings if desired. The board is mounted vertically with two small brackets to save space and to provide a good mechanical and electrical connection.

The microphone jack, the On-Off switch, and the level or gain control were mounted on the front panel, while the bass and treble pots were mounted on the rear panel. A couple of RCA-type phono jacks—one for the output audio and the other for the microphone push-to-talk circuit—were also mounted on the rear. C1, C3, and C5 are 16 volts electrolytic or tantalum capacitors. C2 and C4 are not mounted on the board, but should be soldered on the foil side with short leads.

The network capacitors—C6, C7, C8, and C9—should be good-quality 10% mylar or ceramic capacitors. The bass and treble potentiometers should be of the linear type; be sure to connect both variable arms together, since only one wire comes from the circuit board. The 9 volt battery should be fastened to the bottom of the cabinet with a metal or plastic clamp to avoid tumbling.

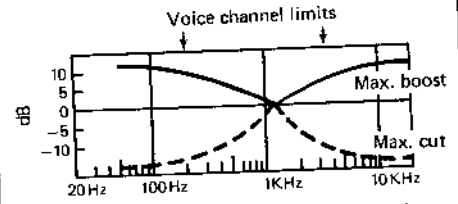


Fig. 4—Frequency response of the microphone equalizer.

Using the Equalizer

Perhaps the best way to evaluate the unit is to get the help of a friend to monitor your test transmissions. If recording capabilities are available, they should be used, and a series of well-documented tests should be made; later you can listen to the recordings and choose the desired settings. Remember that anything done at the receiving end may affect the tests.

The equalizer can be used with almost any phone transmitting equipment of modern design. It may also be used with recording or public-address systems and even with audio equipment. Make sure that all interconnecting cables are shielded to avoid hum or r.f. pick-up and that the level control is set to the proper level.

(Bibliography: *Transistor Manual*, General Electric Co.; *Radio Handbook*, Editors and Engineers; Radiotron designer, RCA; Reference data for radio engineers, I.T.T.)