

# CHOOSING COMPONENT VALUES FOR L-C RESONANT TANK CIRCUITS

Resonant 'tank' circuits consist of combinations of inductance ( $L$ ) and capacitance ( $C$ ) elements configured in such a manner that a single frequency — or more correctly a very narrow band of frequencies — is selected, while frequencies removed from the selected frequency are rejected.

By Joseph J. Carr

THE selection of a specific frequency occurs when the inductive reactance ( $+X_L$ ) and capacitive reactance ( $-X_C$ ) have equal magnitude, so therefore cancel each other. Figure 1 shows two forms of LC resonant tank circuit, and a plot of impedance versus frequency. The parallel resonant form is shown in Fig. 1a, while the series resonant form is shown in Fig. 1b. The following rules apply to these forms (see Fig. 1c):

1. a parallel resonant circuit has a maximum impedance at its resonant frequency ( $F_0$ ); and
2. a series resonant circuit has a minimum impedance at its resonant frequency ( $F_0$ ).

In some cases, one of these types is clearly preferred over the other, but in other cases either could be used if it is used correctly. For example, in a wave

trap — i.e., a circuit that prevents a particular frequency from passing — a **parallel resonant circuit in series with the signal line** will block its resonant frequency while passing all frequencies removed from resonance; a **series resonant circuit shunted across the signal path** will bypass its resonant frequency to common (or 'ground'), while allowing frequencies removed from resonance to pass.

LC resonant tank circuits are used to tune radio receivers; it is these circuits that select the station to be received, while rejecting others. A superheterodyne radio receiver (the most common type) is shown in simplified form in Fig. 2. According to the superhet principle, the radio frequency being received ( $F_{RF}$ ) is converted to another frequency, called the **intermediate frequency** ( $F_{IF}$ ), by being mixed with a **local oscillator** signal ( $F_{LO}$ ) in a non-linear mixer stage. The output of the untuned mixer would be a collection of frequencies defined by:

$$F_{IF} = mF_{RF} \pm nF_{LO} \quad (1)$$

Where  $m$  and  $n$  are either integers or

zero. For the simplified case which is the subject of this article, only the first set of products ( $m=n=1$ ) are considered, so the output spectrum will consist of  $F_{RF}$ ,  $F_{LO}$ ,  $[F_{RF} - F_{LO}]$  (difference frequency), and  $[F_{RF} + F_{LO}]$  (sum frequency). In older radios, for practical reasons the difference frequency was selected for  $F_{IF}$ ; today, either sum or difference frequencies can be selected depending on the design of the radio.

There are several LC tank circuits present in this notional superhet radio. The antenna tank circuit ( $C_1-L_1$ ) is found at the input of the RF amplifier stage, or if no RF amplifier is used it is at the input to the mixer stage. A second tank circuit ( $L_2-C_2$ ), tuning the same range as  $L_1-C_1$  is found at the output of the RF amplifier, or the input of the mixer. Another LC tank circuit ( $L_3-C_3$ ) is used to tune the local oscillator; it is this tank circuit that sets the frequency that the radio will receive.

Additional tank circuits (only two shown) may be found in the IF amplifier section of the radio. These tank circuits will be fixed tuned to the IF frequency, which in common AM broadcast band (BCB) radio receivers is typically

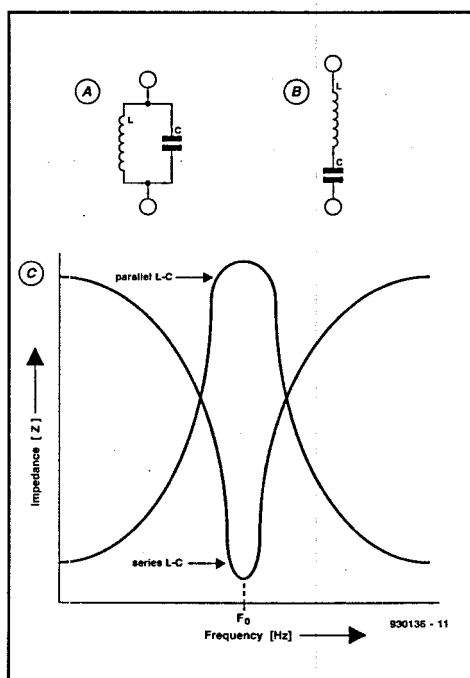


Fig. 1. a) Parallel resonant tank circuit; b) series resonant tank circuit; c) impedance-versus-frequency curves for series and parallel tank circuits.

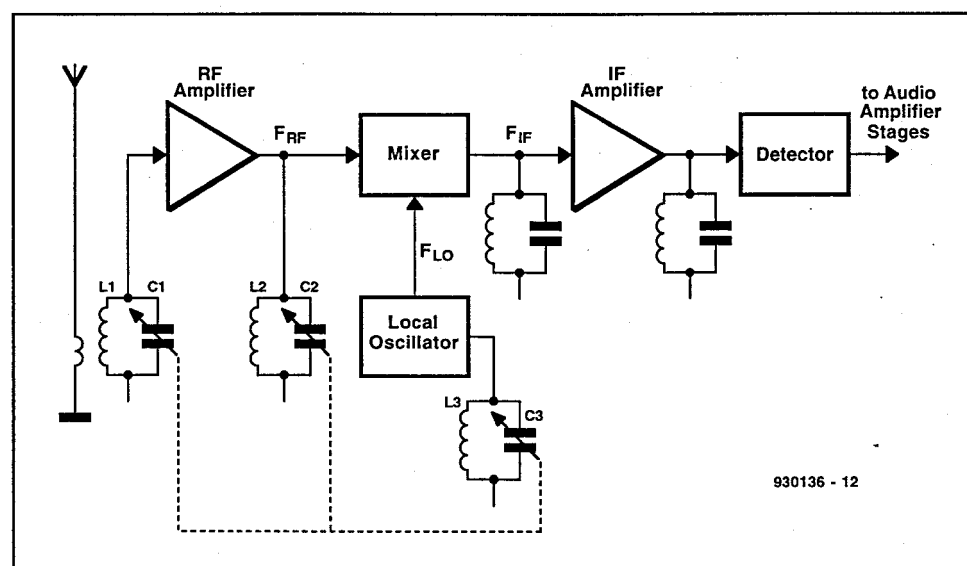


Fig. 2. LC tank circuits in a superheterodyne receiver.

450 kHz, 455 kHz, 460 kHz, or 470 kHz depending on the designer's choices (and sometimes country of origin). Other IF frequencies are also seen, but these are most common. FM broadcast receivers typically use a 10.7 MHz IF, while short-wave receivers might use a 1.65 MHz, 8.83 MHz, 9 MHz or an IF frequency above 30 MHz.

## The tracking problem

On a radio that tunes the front-end with a single knob, which is almost all receivers today, the three capacitors ( $C_1$ ,  $C_2$  and  $C_3$  in Fig. 2) are typically ganged, i.e., mounted on a single rotor shaft. These three tank circuits must track each other; i.e., when the RF amplifier is tuned to a certain radio signal frequency, the LO must produce a signal that is different from the RF frequency by the amount of the IF frequency. Perfect tracking is probably impossible, but the fact that your single knob tuned radio works is testimony to the fact that the tracking isn't too terrible.

The issue of tracking LC tank circuits for the AM broadcast band (BCB) receiver has not been a major problem for many years: the band limits are fixed over most of the world, and component manufacturers offer standard adjustable inductors and variable capacitors to tune the RF and LO frequencies. Indeed, some even offer three sets of coils: antenna, mixer input/RF amp output and LO. The reason why the antenna and mixer/RF coils are not the same, despite tuning the same frequency range, is that these locations see different distributed or 'stray' capacitances. In the U.S.A., it is standard practice to use a 10 to 365-pF capacitor and a 220  $\mu$ H inductor for the 540 to 1600 kHz AM BCB. In some other countries, slightly different combinations are sometimes used: 320 pF, 380 pF, 440 pF, 500 pF and others are seen in catalogues (see, for instance, the Maplin Electronics catalogue. Address: P.O. Box 3, Rayleigh, Essex SS6 2BR, England).

Recently, however, two events coincided that caused me to examine the method of selecting capacitance and inductance values. First, I embarked on a design project to produce an AM DXers receiver that had outstanding performance characteristics. Second, the AM broadcast band was recently extended so that the upper limit is now 1700 kHz, rather than 1600 kHz. The new 540 to 1700 kHz band is not accommodated by the now-obsolete 'standard' values of inductance and capacitance. So I calculated new candidate values.

## The RF amplifier/antenna tuner problem

In a typical RF tank circuit, the inductance is kept fixed (except for a small adjustment range that is used for

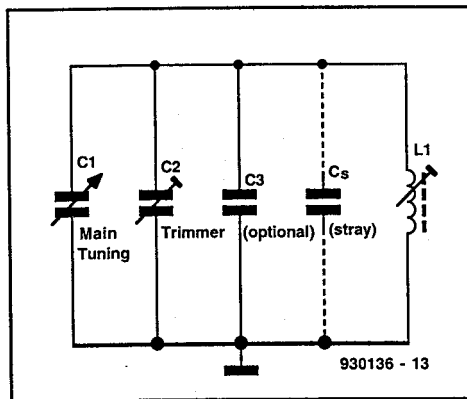


Fig. 3. Parallel resonant tuning circuit.

overcoming tolerance deviations) and the capacitance is varied across the range. Figure 3 shows a typical tank circuit main tuning capacitor ( $C_1$ ), trimmer capacitor ( $C_2$ ) and a fixed capacitor ( $C_3$ ) that is not always needed. The stray capacitance ( $C_s$ ) includes the interwiring capacitance, the wiring to chassis capacitance, and the amplifier or oscillator device input capacitance. The frequency changes as the square root of the capacitance change. If  $F_1$  is the minimum frequency in the range, and  $F_2$  is the maximum frequency, then the relationship is:

$$\frac{F_2}{F_1} = \sqrt{\frac{C_{\max}}{C_{\min}}} \quad (2)$$

or, in a rearranged form that some find more congenial:

$$\left(\frac{F_2}{F_1}\right)^2 = \frac{C_{\max}}{C_{\min}} \quad (3)$$

In the case of the new AM receiver, I wanted an overlap of about 15 kHz at the bottom end of the band, and 10 kHz at the upper end, so needed a resonant tank circuit that would tune from 525 kHz to 1710 kHz. In addition, because variable capacitors are widely available in certain values based on the old standards, I wanted to use a 'standard' AM BCB variable capacitor. A 10 to 380 pF unit from a vendor was selected.

The minimum required capacitance,  $C_{\min}$ , can be calculated from:

$$\left(\frac{F_2}{F_1}\right)^2 C_{\min} = C_{\min} + \Delta C \quad (4)$$

Where:

- $F_1$  is the minimum frequency tuned;
- $F_2$  is the maximum frequency tuned;
- $C_{\min}$  is the minimum required capacitance at  $F_2$ ;
- $\Delta C$  is the difference between  $C_{\max}$  and  $C_{\min}$ .

### Example

Find the minimum capacitance needed to tune 1710 kHz when a 10 to 380 pF capacitor ( $\Delta C = 380 - 10$  pF = 370 pF) is

used, and the minimum frequency is 525 kHz.

**Solution:**

$$\left(\frac{F_2}{F_1}\right)^2 C_{\min} = C_{\min} + \Delta C$$

$$\left(\frac{1710 \text{ kHz}}{525 \text{ kHz}}\right)^2 C_{\min} = C_{\min} + 370 \text{ pF}$$

$$10.609 C_{\min} = C_{\min} + 370 \text{ pF}$$

$$C_{\min} = 38.51 \text{ pF}$$

The maximum capacitance must be  $C_{\min} + \Delta C$ , or  $38.51 + 370$  pF = 408.51 pF. Because the tuning capacitor ( $C_1$  in Fig. 3) does not have exactly this range, external capacitors must be used, and because the required value is higher than the normal value additional capacitors are added to the circuit in parallel to  $C_1$ . Indeed, because somewhat unpredictable 'stray' capacitances also exist in the circuit, the tuning capacitor values should be a little smaller than the required values in order to accommodate strays plus tolerances in the actual — versus published — values of the capacitors. In Fig. 3, the main tuning capacitor is  $C_1$  (10 to 380 pF),  $C_2$  is a small value trimmer capacitor used to compensate for discrepancies,  $C_3$  is an optional capacitor that may be needed to increase the total capacitance, and  $C_s$  is the stray capacitance in the circuit.

The value of the stray capacitance can be quite high, especially if there are other capacitors in the circuit that are not directly used to select the frequency (e.g., in Colpitts and Clapp oscillators the feedback capacitors affect the LC tank circuit). In the circuit that I was using, however, the LC tank circuit is not affected by other capacitors. Only the wiring strays and the input capacitance of the RF amplifier or mixer stage need be accounted. From experience I apportioned 7 pF to  $C_s$  as a trial value.

The minimum capacitance calculated above was 38.51, there is a nominal 7 pF of stray capacitance, and the minimum available capacitance from  $C_1$  is 10 pF. Therefore, the combined values of  $C_2$  and  $C_3$  must be  $(38.51 - 10 - 7)$  pF, or 21.5 pF. Because there is considerable reasonable doubt about the actual value of  $C_s$ , and because of tolerances in the manufacture of the main tuning variable capacitor ( $C_1$ ), a wide range of capacitance for  $C_2 + C_3$  is preferred. It is noted from several catalogues that 21.5 pF is near the centre of the range of 45 pF and 50 pF trimmer capacitors. For example, one model lists its range as 6.8 pF to 50 pF, its centre point is only slightly removed from the actual desired capacitance. Thus, a 6.8 to 50 pF trimmer was selected, and  $C_3$  is not used.

Selecting the inductance value for  $L_1$  (Fig. 3) is a matter of picking the frequency and associated required capaci-

```

100 'PROGRAM TO CALCULATE L-C TANK CIRCUIT VALUES
110 'A color monitor is needed for this program. If no color monitor is
120 'is used, then delete Line Nos. 140 and 150.
130 CLS:KEY OFF
140 SCREEN 9
150 GOSUB 1030:'Get graphic of circuit diagram
160 'Start of program
170 CLS:KEY OFF:SCREEN SCR:PI = 22/7
180 IF SCR > 0 THEN COLOR 1,7
190 LOCATE 6,15:PRINT "Calculate L-C tank circuit values from knowledge"
200 LOCATE 7,15:PRINT "of desired frequency range and variable capacitor"
210 LOCATE 8,15:PRINT "values (in picofarads)."
220 LOCATE 10,15:PRINT "Enter MINIMUM frequency (F1) in kilohertz (KHz):"
230 INPUT F1$:' Obtain value of lowest frequency
240 F1 = VAL(F1$):' Test input of F1 to see if zero
250 IF F1 = 0 THEN BEEP
260 IF F1 = 0 THEN 220 ELSE 270
270 LOCATE 12,15:PRINT "Enter MAXIMUM frequency (F2) in kilohertz (KHz):"
280 INPUT F2$:' Obtain value of highest frequency
290 F2 = VAL(F2$):' Test input of F2 to see if zero
300 IF F2 = 0 THEN BEEP
310 IF F2 = 0 THEN 270
320 IF F2 < F1 THEN GOSUB 1440:'Test for incorrect freq. input
330 IF F1 > F2 THEN GOSUB 1440
340 IF F2 = F1 THEN 160 ELSE 350
350 IF F1 > F2 THEN 160 ELSE 360
360 LOCATE 14,15:PRINT "Select Capacitor Values..."
370 LOCATE 15,15:PRINT "Enter MINIMUM value of capacitor in picofarads (pF):"
380 INPUT CMIN$
390 CMIN = VAL(CMIN$)
400 IF CMIN = 0 THEN BEEP
410 IF CMIN = 0 THEN 360 ELSE 420
420 LOCATE 18,15:PRINT "Enter MAXIMUM value of capacitor in picofarads (pF):"
430 INPUT CMAX$
440 CMAX = VAL(CMAX$)
450 IF CMAX = 0 THEN BEEP
460 IF CMAX = 0 THEN 420 ELSE 470
470 IF CMIN > CMAX THEN GOSUB 1480:'Test for incorrect cap. input
480 IF CMIN > CMAX THEN GOSUB 1480:'and display error message
490 IF CMIN = CMAX THEN 360 ELSE 500
500 IF CMIN > CMAX THEN 360 ELSE 510
510 CLS:'Clear screen and print all entered values
520 LOCATE 6,15:PRINT "Minimum frequency (F1):";F1;" KHz"
530 LOCATE 7,15:PRINT "Maximum frequency (F2):";F2;" KHz"
540 LOCATE 9,15:PRINT "Minimum capacitance in C1: ";CMIN;" pF"
550 LOCATE 10,15:PRINT "Maximum capacitance in C1: ";CMAX;" pF"
560 FRATIO = F2/F1:'Calculate frequency ratio
570 CRATIO = CMAX/CMIN:'Calculate capacitance ratio
580 CDELTA = CMAX-CMIN
590 LOCATE 11,15:PRINT "Frequency ratio: ";
600 PRINT USING "###.##";FRATIO:PRINT ":1"
610 LOCATE 12,15:PRINT "Required capacitance ratio: ";
620 PRINT USING "###.##";CRATIO:PRINT ":1"
630 LOCATE 13,15:PRINT "Capacitance differential: ";
640 PRINT USING "###.##";CDELTA:PRINT " pF"
650 XMIN = CDELTA/(CRATIO - 1):'Calculate min. total cap. needed
660 XMAX = CDELTA * XMIN:' Calculate max. total cap. needed
670 TRIMCAP = XMIN - CMIN
680 IF TRIMCAP < 0 THEN GOSUB 1580 ELSE 690
690 IF TRIMCAP < 0 THEN 160 ELSE 700
700 LOCATE 15,15:PRINT "Trimmer capacitance needed: ";
710 PRINT USING "###.##";TRIMCAP:PRINT " pF"
720 LUH = 1/(4*PI^2*F1^2*XMAX*10^-12)
730 LOCATE 16,15:PRINT "Inductance needed: ";
740 PRINT USING "###.##";LUH:PRINT " uH"
750 LOCATE 18,15:PRINT "Allocate a few pF for strays and then make up"
760 LOCATE 19,15:PRINT "remaining capacitance with either fixed or variable"
770 LOCATE 20,15:PRINT "trimmer capacitors."
780 LOCATE 22,15:GOSUB 1630:'Get press any key subroutine
790 CLS:'clear screen for new message
800 LOCATE 10,15:PRINT "The trimmer capacitance will include all capacitances"
810 LOCATE 11,15:PRINT "seen by the inductor, and that could include a large"
820 LOCATE 12,15:PRINT "capacitance in other parts of the circuit. In certain"
830 LOCATE 13,15:PRINT "oscillator circuits, especially Colpitts and Clapp"
840 LOCATE 14,15:PRINT "oscillators, the other capacitances are large."
850 LOCATE 15,15:PRINT "Check a good oscillator design handbook for further"
860 LOCATE 16,15:PRINT "information."
870 LOCATE 18,15:GOSUB 1630
880 CLS:LOCATE 12,15:PRINT "(D)o Another Problem?"
890 LOCATE 13,15:PRINT "(E)nd Program?"
900 CHOICES$ = INPUT$(1)
910 IF CHOICES = "D" THEN CHOICE = 1
920 IF CHOICES = "d" THEN CHOICE = 1
930 IF CHOICES = "E" THEN CHOICE = 2
940 IF CHOICES = "e" THEN CHOICE = 2
950 IF CHOICE < 1 THEN 880 ELSE 960
960 IF CHOICE > 2 THEN 880 ELSE 970
970 IF INT(CHOICE) = CHOICE THEN 980 ELSE 880
980 ON CHOICE GOTO 160,990
990 CLS:LOCATE 12,20:PRINT "Program Ended...Goodbye"
1000 TIMELoop=TIMER:WHILE TIMER < TIMELoop + 2:WEND
1010 CLS
1020 END
1030 'Subroutine to draw circuit picture on screen
1040 CLS:LINE (45,100)-(100,100):'Draw connecting rails
1050 LINE (450,200)-(100,200)
1060 LINE (175,180)-(165,120),,B:'Draw inductor L1
1070 LINE (170,200)-(170,180)
1080 LINE (170,200)-(170,100)
1090 LINE (175,180-22)-(165,180-22)
1100 ZZ = ZZ + 5
1110 IF ZZ = 60 GOTO 1130
1120 GOTO 1090
1130 LINE (250,200)-(250,153):'Draw C1 (main tuning capacitor)
1140 LINE (250,147)-(250,100)
1150 LINE (265,153)-(235,153)
1160 LINE (265,147)-(235,147)
1170 LINE (365,165)-(235,135)
1180 LINE (350,200)-(350,153):'Draw C2 (trimmer capacitor)
1190 LINE (350,147)-(350,100)
1200 LINE (365,153)-(335,153)
1210 LINE (365,147)-(335,147)
1220 LINE (365,165)-(335,135)
1230 LINE (450,200)-(450,153):'Draw stray capacitances
1240 LINE (450,147)-(450,153)
1250 LINE (465,153)-(435,153)
1260 LINE (465,147)-(435,147)
1270 LINE (102,102)-(98,98),1,B
1280 LINE (102,202)-(98,198),1,B
1290 LINE (252,202)-(248,198),1,BF
1300 LINE (252,102)-(248,98),1,BF
1310 LINE (352,202)-(348,198),1,BF
1320 LINE (352,102)-(348,98),1,BF
1330 LINE (172,202)-(168,198),1,BF
1340 LINE (172,102)-(168,98),1,BF
1350 LOCATE 11,19:PRINT "L1":'Add alphabetic labels
1360 LOCATE 11,27:PRINT "C1"
1370 LOCATE 11,40:PRINT "C2"
1380 LOCATE 11,49:PRINT "Stray"
1390 LOCATE 16,15:PRINT "C1 is main tuning capacitor"
1400 LOCATE 17,15:PRINT "C2 is trimmer + fixed capacitors"
1410 LOCATE 18,15:PRINT "Stray is wiring capacitances plus other"
1420 LOCATE 19,15:PRINT "capacitors in the circuit."
1430 LOCATE 21,15:GOSUB 1630:CLS:RETURN:'End of Subroutine
1440 ' Error Message Subroutine (Incorrect Frequency Input)
1450 BEEP:LOCATE 20,15:PRINT "ERROR! F2 must be greater than F1"
1460 LOCATE 19,15:GOSUB 1630:' Go get press any key subroutine
1470 RETURN:'End of Subroutine
1480 'Error Message Subroutine (Incorrect Capacitance Input)
1490 BEEP:LOCATE 20,15:PRINT "ERROR! CMAX must be greater than CMIN"
1500 LOCATE 22,15:GOSUB 1630:' Go get press any key subroutine
1510 GOSUB 1530:'Clear screen and reprint F1 and F2
1520 RETURN:' End of Subroutine
1530 'Subroutine to clear screen and reprint values of F1 and F2
1540 CLS
1550 LOCATE 6,15:PRINT "Minimum frequency (F1):";F1;" KHz";
1560 LOCATE 7,15:PRINT "Maximum frequency (F2):";F2;" KHz"
1570 RETURN:'End of Subroutine
1580 'Subroutine for Too Small Trimmer Capacitance
1590 CLS
1600 LOCATE 12,15:PRINT "ERROR!!! Not a viable combination...try again"
1610 LOCATE 14,15:GOSUB 1630:'Go get press any key subroutine
1620 RETURN
1630 ' Press Any Key... Subroutine
1640 PRINT "Press Any Key To Continue..."
1650 AS = INKEY$:IF AS = "" THEN 1650 ELSE 1660
1660 RETURN:'End of Subroutine

```

930136-16

tance at one end of the range, and calculating from the standard resonance equation solved for  $L$ :

$$L = \frac{10^6}{4\pi^2 F_{\text{low}}^2 C_{\text{max}}} \mu\text{H} \quad (5)$$

$$L = \frac{10^6}{4\pi^2 (525,000)^2 (4.085 \times 10^{-10})}$$

$$L = 224.97 = 225 \mu\text{H}$$

The RF amplifier input  $LC$  tank circuit and the RF amplifier output  $LC$  tank circuit are slightly different cases because the stray capacitances are somewhat different. In the example, I am assuming a JFET transistor RF amplifier, and it has an input capacitance of only a few picofarads. The output capacitance is not a critical issue in this specific case because I intend to use a 1 mH RF choke in order to prevent JFET oscillation. In the final receiver, the RF amplifier may be deleted altogether, and the  $LC$  tank circuit described above will drive a mixer input through a link coupling circuit.

## The local oscillator (LO) problem

The local oscillator circuit must track the RF amplifier, and must also tune a frequency range that is different from the RF range by the amount of the IF frequency (455 kHz). In keeping with common practice I selected to place the LO frequency 455 kHz above the RF frequency. Thus, the LO must tune the range 980 kHz to 2,165 kHz.

There are three methods for making the local oscillator track with the RF amplifier frequency when single shaft tuning is desired: the **trimmer capacitor** method, the **padder capacitor** method, and the **different-value cut-plate capacitor** method.

The trimmer capacitor method was shown in Fig. 3, and is the same as the RF  $LC$  tank circuit. Using exactly the same method as before, but with a frequency ratio of (2165/980) to yield a capacitance ratio of  $(2165/980)^2 = 4.88:1$ , solves this problem. The results were a minimum capacitance of 95.36 pF, and a maximum capacitance of 465.36 pF. An inductance of 56.7  $\mu\text{H}$  is needed to resonate these capacitances to the LO range.

There is always a problem associated with using the same identical capacitor for both RF and LO. It seems that there is just enough difference that tracking between them is always a bit off. Figure 6 shows the ideal LO frequency and the calculated LO frequency. The difference between these two curves is the degree of non-tracking. The curves

Fig. 4. BASIC program to calculate RF tank circuit component values.

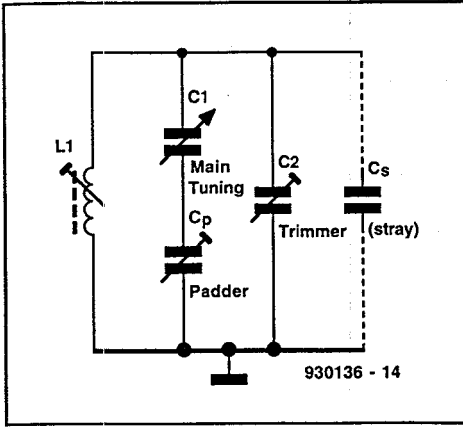


Fig. 5. Parallel resonant tank circuit using the padder capacitor method.

overlap at the ends, but are awful in the middle. There are two cures for this problem. First, use a **padder capacitor** in series with the main tuning capacitor (Fig. 5). Second, use a **different-value cut-plate capacitor**.

Figure 5 shows the use of a padder capacitor ( $C_p$ ) to change the range of the LO section of the variable capacitor. This method is used when both sections of the variable capacitor are identical. Once the reduced capacitance values of the  $C_1/C_p$  combination are determined the procedure is identical to above. But first, we have to calculate the value of the padder capacitor and the resultant range of the  $C_1/C_p$  combination. The padder value is found from:

$$\frac{C_{1_{max}} C_p}{C_{1_{max}} + C_p} = \left(\frac{F_2}{F_1}\right)^2 \left(\frac{C_{1_{min}} C_p}{C_{1_{min}} + C_p}\right) \quad (6)$$

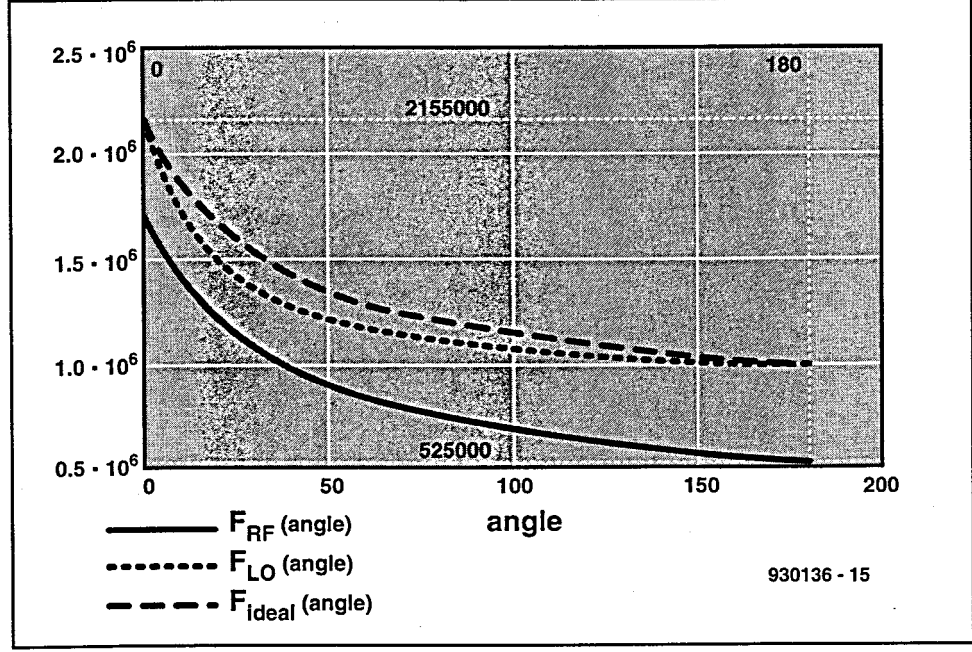


Fig. 6. MathCAD 3.1 plot of RF, LO (ideal) and LO (actual) tuning as a function of capacitor shaft angle.

...and solving for  $C_p$ . For the values of the selected main tuning capacitor and LO:

$$\frac{(380 \text{ pF}) C_p}{(380 + C_p) \text{ pF}} = (4.88) \left( \frac{(10 \text{ pF}) C_p}{(10 + C_p) \text{ pF}} \right)$$

Solving for  $C_p$  by the least common denominator method (crude, but it works) yields a padder capacitance of 44.52 pF. The series combination of 44.52 pF and a 10 to 380 pF variable yields a range of 8.2 pF to 39.85 pF. An inductance of

661.85  $\mu\text{H}$  is needed for this capacitance to resonate over 980 kHz to 2,165 kHz.

A practical solution to the tracking problem that comes close to the ideal is to use a **cut-plate capacitor**. These variable capacitors have at least two sections, one each for RF and LO tuning. The shape of the capacitor plates are especially cut to a shape that permits a constant change of **frequency** for every degree of shaft rotation. With these capacitors, when well done, it is possible to produce three-point tracking, or better. ■

### Books from Elektor Electronics (Publishing)

The following books are currently available:

301 Circuits	£9-95	\$14.50
302 Circuits	£9-95	\$14.50
303 Circuits	£10-95	\$17.90
304 Circuits	£12-95	\$23.95
305 Circuits†	£14-95	\$27.70
SMT Projects	£ 9-95	\$14.50
Microprocessor Data Book	£10-95	\$19.90
Data Sheet Book 2	£9-95	\$18.50
Data Book 3: Peripheral Chips	£10-95	\$19.95
Data Book 4: Peripheral Chips	£10-95	\$19.95
Data Book 5: Application Notes	£10-95	\$19.95

address, see order form on p. 79) or direct from our Dorchester office (private customers only\*) on the order form on page 79.

\* Orders other than from private customers, for instance, bookshops, schools, colleges, should be sent to

**Gazelle Book Services Ltd**  
**Falcon House**  
**Queen Square**  
**Lancaster LA1 1RN**  
**England**  
**Telephone (0524) 68765; Fax (0524) 63232**

† Not available until late December/early January

The books may be obtained from bookshops\*, Old Colony Sound Lab (USA and Canadian readers only—for