

The Perfect Morse Machine

— send and receive CW with a dedicated micro

Author's note: I will supply a photocopy of the PC board artwork for \$4.00. I will also program reader-supplied 2708s for \$6.00. Both are payable by money order or certified check. I also wish to thank Mike Hadley WA7NLM for his audio filter design.

Have you seen all of the ads coming out for "automatic" Morse keyboards and readers with one big alphanumeric "eye" that gives you a readout as someone is sending code? Then there are the "complete" sta-

tions which will do both on a TV screen for only \$600. The item I am about to describe can do all of this and more, with many possible options, for less than \$100.


About three years ago at the Dayton Hamvention, I picked up a program for

a computer-controlled Morse code station. This program was written with the MC6800 computer in mind and was fathered by Don Jackson W7GKU and Jim Bainter WA7VKZ. The computer and the program in our story have changed

significantly, but still are based on their algorithms. The original program was designed for use with the old Mikbug® evaluation module, and used the on-board ACIA (Asynchronous Communications Interface Adapter) serial port for communications with a TTY or CRT terminal.

Well, after I finally got to the point where I had a little knowledge of the 6800, I decided to try to make this thing work. Keep in mind that a little knowledge is dangerous! I had to do some work, but after a while, a wire-wrapped version appeared on a card within my computer. I didn't believe it, but it really worked. The only problem I had with it was the way it copied code. It was so perfect that all of those with sorry fists would really mess it up. With all of the means available to generate decent code, whether keyer or keyboard, there is really no excuse for a poor fist.

Well, enough of my soapbox. With this gizmo, everybody can have perfect CW capabilities. After the original version, wire-

 

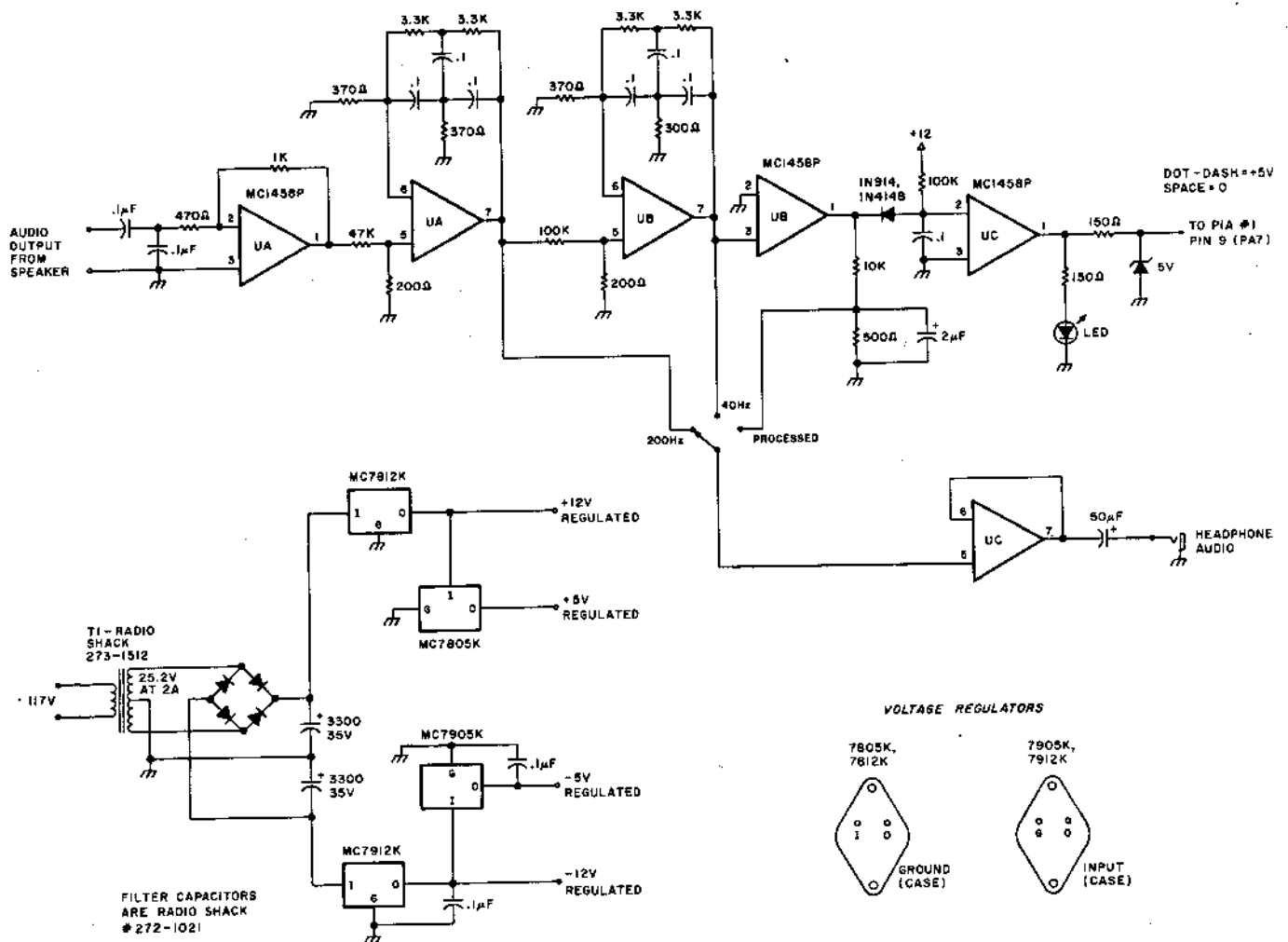


Fig. 1. This is the audio filter and recommended power supply. The input audio is filtered by the op amps and turned into dc to be fed into the PIA. Vcc = pin 8 (+12); Vee = pin 4 (-12).

wrapped deep within the bowels of my mainframe, worked, the next thought was to make it a fully self-contained system with a dedicated CPU to work with. The most logical choice was to use the MC6802—son of 6800. With clock and RAM all on silicon, at least three packages could be saved over the original 6800 design. The age of the small dedicated system has arrived.

The following evening was spent on wire-wrapping a small board with the system. The program was, of course, stored in an EPROM for automatic "boot" and for more additions later. The two biggest drawbacks that I could find were that it still required a terminal which was both large and expen-

sive, and it had a switch to go from receive to transmit, and so forth. The last time I saw one of those things was as a Novice with my Globe Scout and S100!

So, these little things had to be fixed. OK, the switch could be replaced with a different polling routine within the software. No sweat, but what about the terminal? Well, plugging in a keyboard would be no trouble, but something to peer at was also required. What to do? Well, Burroughs makes some fine display panels which can display about 30 characters on a line, but you might have to float a loan to buy one—and having to use 250 volts didn't appeal to me, anyway.

Enter the DL-1416. Litronix has done it again. The 1416 is a four-digit,


16-segment, alphanumeric intelligent display, which, when fed parallel ASCII, will display the most-used 64 characters of the ASCII set. It is a five-volt-only device, and by placing it directly on the CPU bus, will appear as "write-only RAM." Unfortunately, the slow setup times and the need to have data valid before Read/Write comes out present a few problems. The first version had the LEDs just hanging on the data bus and worked with some degree of reliability. But when Rs started coming out as Ps, I knew that the timing specifications were being violated.


After much manipulation of the clock and stretching of the E pulse, I determined that too much glue (peripheral hardware)

would be required to just leave it on the bus. Then I remembered that only half of PIA 2 was being used, so the most logical choice was to put the 1416 on the peripheral data bus. By setting the control register within the PIA first to a \$34 and then to a \$3C, the CB2 line would go low and come high again, all done while the data was latched onto the output lines. Great—use this for the \overline{W} (write) line, and tie it to CE (chip enable), too! The timing of the 1416 specifies that the falling edge of CE must be at least 500 ns before the rising edge of \overline{W} . So having them both come in at the same time is permissible. See the timing diagrams.

According to Appnote 9A from Litronix, systems which use only a 6-bit

VOLTAGE REGULATORS

 

 

ASCII code can still utilize the 1416 by inverting D5 and feeding it into D6. By doing it this way, two "spare" data lines are saved. These two lines are used for addressing either of the four digits to be written to. All of the work writing to the LEDs is now being accomplished in software.

The clock within the 6802 is really a strange beast. It can accept any parallel-resonant crystal from 1 to 4 MHz. Of course, the crystal is divided by four, so remember this when selecting your crystal. In this program, the CPU will work fine even when running at its minimum frequency (100-kHz bus speed, 400-kHz crystal frequency).

A funny thing happened

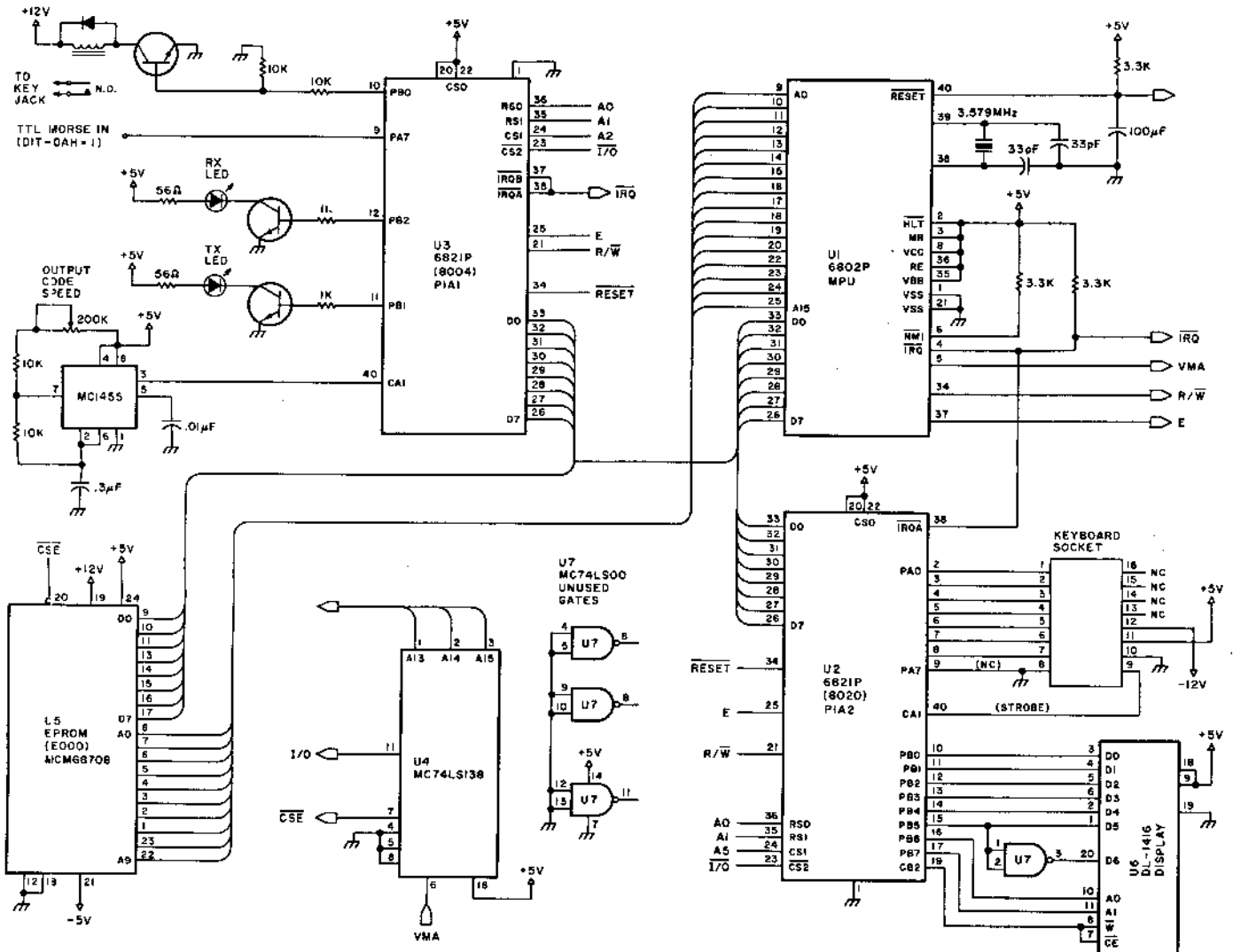


Fig. 2. The main processor, composed of the MC6802 MPU, two PIAs, and an EPROM.

while experimenting with different crystal types; the thing oscillated even without a crystal! The frequency was really slow and

quite unstable, but it worked. Even after power down and up, it continued to oscillate. Since the 6802 is not specified for use

without a crystal, Motorola won't guarantee it to work without one, but, just for fun, why not try it out on yours when you build it?

You might think that having only four digits a little bigger than a calculator display would be a real

hassle to use. Not so! The program takes the incoming data or keyboard data and puts it in the right-hand display. As the next character comes in, it is shifted left one digit. Instant "Times Square" display. I was a bit hesitant to use on-

POWER SUPPLY NOTES

The total current requirements for the reader/talker are given below. These figures are the absolute maximums for the individual components, so don't expect them to be that high, but, just in case, go ahead and plan for it.


Current requirements for the reader/talker. All values are in milliamps and are absolute maximums.

	+5 V	+12 V	-12 V	-5 V
MC6802	240	—	—	—
MC6821	110	—	—	—
MC6821	110	—	—	—
MCM68708	10	65	—	65
MC74LS138	6.4	—	—	—
MC74LS00	15	—	—	—
DL1416	100	—	—	—
MC1458	—	8	8	—
MC1458	—	8	8	—
MC1458	—	8	8	—
3 LEDs	30	—	—	—
Average Keyboard	225	—	45	—
Maximum Totals	846.4	89	69	45

As can be seen in the totals, all currents can be handled with the three-terminal-style regulators. The following calculations are to determine what the power dissipation for each device is. For the three-terminal regulators, the power dissipation can be expressed by the following equation:

$P_D = (\Delta E_{IN}) I_{OUT} + E_{IN} (I_Q)$, where: P_D = Power dissipation, E_{IN} = In-Out voltage, I_{OUT} = output current, and I_Q = current through ground lug.

 For the positive voltage regulators, the following schematic is used, and the voltages are labeled. These were typical, using the values of transformers and capacitors specified in Fig. 1.




$$7812 P_D = (6.2 \text{ V}) (.935 \text{ A}) + 17.8 (.008) = 5.94 \text{ W}$$

(Note: .935 A = .846 A + .089 A)


$$7805 P_D = (6.5 \text{ V}) (.846 \text{ A}) + 11.6 (.008) = 5.34 \text{ W}$$

 In the same light, the minus voltage regulators can be also calculated:



$$7912 P_D = (6.9 \text{ V}) (.114 \text{ A}) + (18.6) (.008) = .935 \text{ W}$$
 
$$7905 P_D = (6.9 \text{ V}) (.045 \text{ A}) + 11.7 (.008) = .404 \text{ W}$$



CB2 GOES LOW AS WRITE 0 INTO BIT 3 CB2 GOES HIGH AS WRITE 1 INTO BIT 3

LDAA #534
STAA PIA2BC
LDAA #53C 2 CYCLES
STAA PIA2BC 5 CYCLES
7 CYCLES CB2 IS LOW

7 CYCLES = 7µS AT 1MHz BUS SPEED

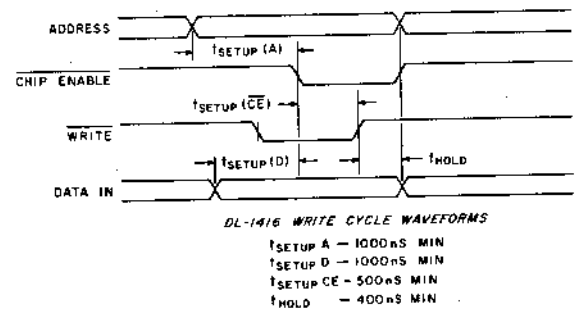


Fig. 3. PIA write-timing to displays, and Litronix-recommended write-cycles for the DL-1416.

By taking the input of the 7805 from the output of the 7812, the power dissipation of the 7812 was raised from about 1/2 Watt to almost 6 Watts. But by taking the 7805 input directly at the capacitor output, its P_D would have been 10.75 Watts! This would be very difficult to heat sink, so by doing it as shown, the total power dissipation is about the same, only divided between two parts.

According to the Motorola Linear IC Data Book, to dissipate the required power (5.9 and 5.3 W), a heat sink which can dissipate 15°C/Watt will be required. The minus voltage regulators are not as critical, as they have a lesser current demand on them. I recommend the use of the -K suffix regulators (TO-3 case), because their thermal resistance (junction-to-case vs. junction-to-air in the plastic package) is so much better. Heat sink them with an appropriate sink, preferably to a metal case, and no problems should be encountered. The negative regulators' requirements can be satisfied by simply bolting them to the chassis. (Be sure to insulate their cases!)

The voltage regulators shown in the pictures are of the plastic style and get quite hot even with the heat sinking shown. When the project is put into an enclosure, TO-3-style regulators will replace them.

ly four digits, but after using it, I find that 4 is really not too few, and the faster the code is sent, the easier it is to read. The new design now automatically

transfers from receive to transmit and back again after all characters have been sent. The algorithm used in the code conversion is set up so that

it automatically senses speed changes and adjusts itself for the correct speed. This can be anywhere between about one-half wpm to 300 wpm. Changing speed

requires only about 2 characters to be lost, so it is quite efficient. Neat, eh? Back before I built the keyboard/reader, I thought that it would be "cheating" to use one; it had been done manually for such a long time, who was I to change any preconceived ideas? Anyway, I have found just the opposite to be true! Number 1, the computer is not foolproof. It can be messed up by zero-beat QRM, sloppy fists, or high noise levels. So, when you start your QSO, try not to get carried away and go too fast, because if one of these should happen, you might be stranded by sending faster than you can receive. Another thing is that you are seeing a character appear on the display at the same time you are hearing it. No better way for associative learning than to get the code into your eyes and ears simultaneously. I've found my speed to be dramatically increasing following the use of it for a couple of weeks. Also, you have a tendency to follow the conversation along in your head—the only way to do it for above 15 or 20 wpm. The final plus is that you hear perfect code being sent by your keyboard, and it makes you wish that everyone had one of these things! So, it's not really cheating, but only another progressive learning device provided by the computer.

As this design recognizes a single input to determine a character and a single output for code, why couldn't it also be used for Baudot or ASCII teletype™? This is just a bug in your ear—look for some further programs in later articles. Wouldn't it be nice to have a truly portable TTY "machine"?

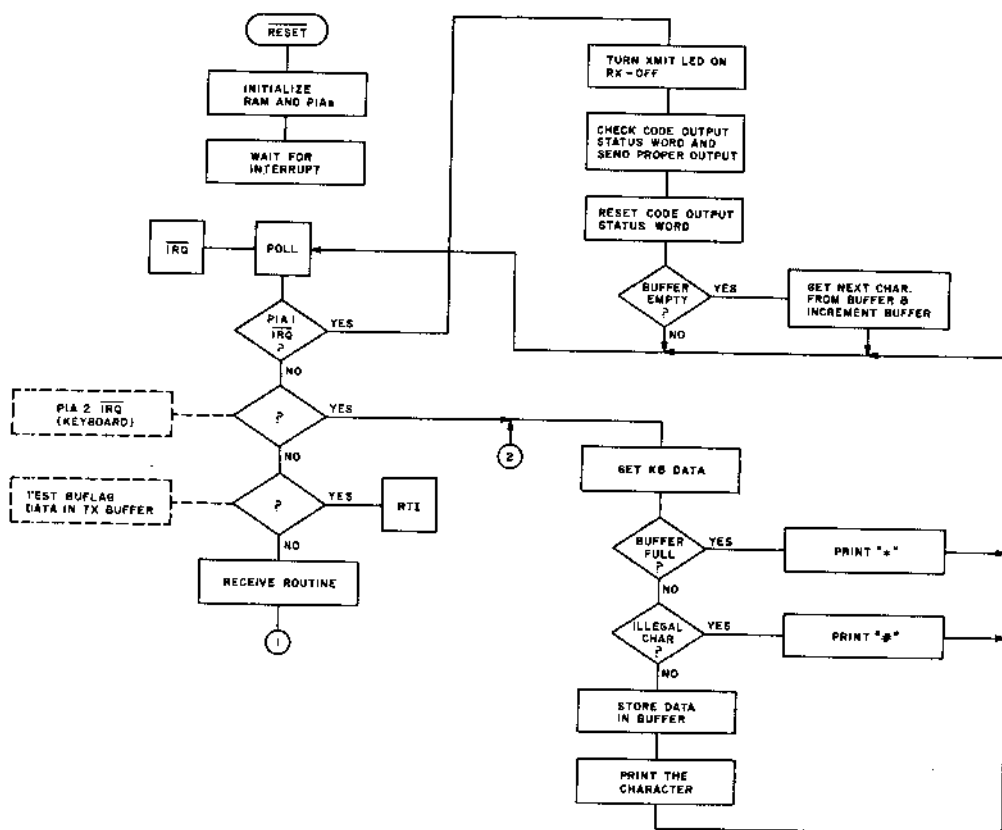


Fig. 4. Flowchart, part 1.

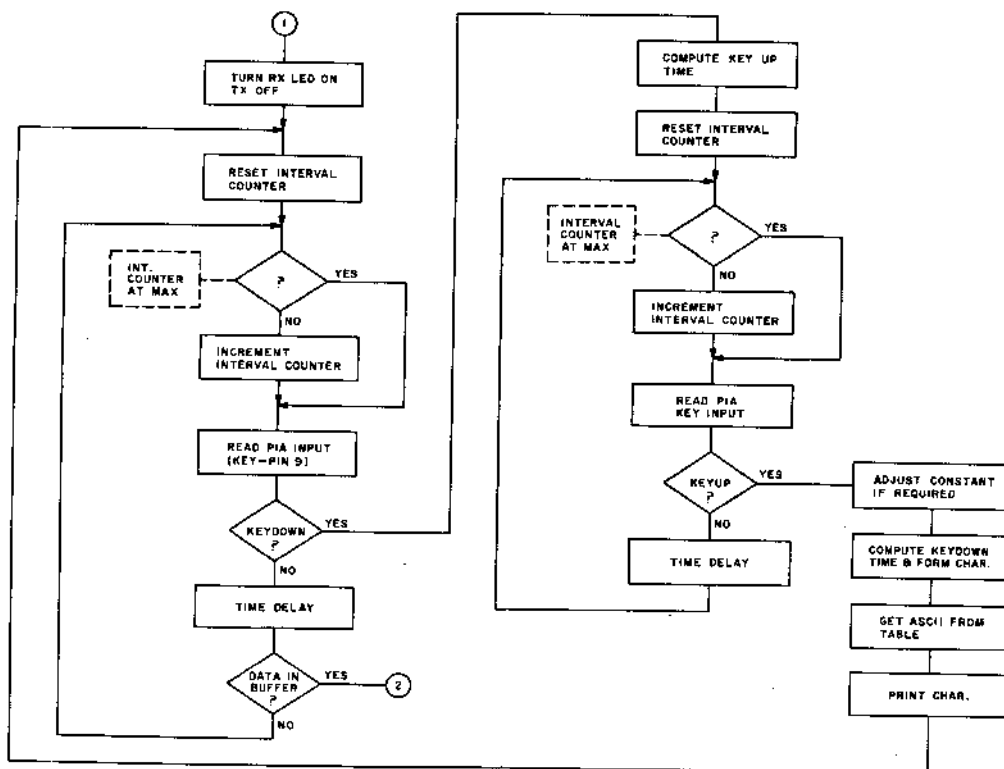


Fig. 5. Flowchart, part 2.

Construction

As you can see in Fig. 1,

the audio from a head-
phone jack or speaker tie-
in goes into a filter-pro-
cessor where it is con-
verted from audio tones to
TTL-compatible levels.

This audio input is fed into
an op amp preamplifier, so
not a whole lot of audio is
required. You might want
to pad it if your receiver
overdrives the device. You

also can plug your head-
phones into the jack on the
board and use it for a filter.
The first switch position
provides selectivity down
to about 200 Hz, the sec-

ond to 40 Hz, and the third
to processed audio—this is
a really fun feature. After it
is tuned in correctly, all
you hear is a tone. No
QRN, no static, no gar-
bage, only a pure represen-
tation of the sent charac-
ter. This is a really weird
feeling, especially if you
have never used it before.
If you don't want to build
the computer, at least
build the filter—it works
great for CW by itself.

After this processed
audio is converted to a
voltage level, it is fed into a
single bit of a PIA (Periph-
eral Interface Adapter)
parallel port. Two of these
PIAs are used on the board,
one for Morse in and out,
transmit speed timing, and
indicator LEDs. The second
PIA is for the keyboard and
LED display unit. The 555
circuit is set for the desired
speed at which you wish to
transmit. In this design, a
relay is provided for Morse
code output. Although my
HW-104 uses positive volt-
age keying and worked
great with just a single key-
ing transistor, a reed relay
provides a more versatile
interface for use with any
type of keying, from grid-
block to cathode.

The EPROM in the cir-
cuit is used to hold the pro-

CHARACTER SET												
		D0	L	H	L	H	L	H	L	H		
		D1	L	L	H	H	L	L	H	H		
		D2	L	L	L	L	H	H	H	H		
D6	D5	D4	D3									
L	H	L	L		0	1	2	3	4	5	6	7
L	H	L	H		<	>	*	+	/	--	-	/
L	H	H	L		8	9	-	/	∠	=	\	?
L	H	H	H		8	9	-	/	∠	=	\	?
H	L	L	L		a	A	B	C	D	E	F	G
H	L	L	H		H	I	J	K	L	M	N	O
H	L	H	L		P	Q	R	S	T	U	V	W
H	L	H	H		X	Y	Z	[\]	^	_

LOADING DATA

ADDRESS					DATA INPUT						
\overline{CE}	\overline{CU}	\overline{W}	A ₁	A ₀	D6	D5	D4	D3	D2	D1	D0
H	X	X	X	X	X	X	X	X	X	X	X
L	H	L	L	L	H	L	L	L	L	L	H
L	H	L	L	H	H	L	L	L	L	H	L
L	H	L	H	L	H	L	L	L	H	L	L
L	H	L	L	H	H	L	L	L	H	L	H
L	H	L	H	L	H	L	L	H	L	H	H
L	H	L	-	-	-	-	-	-	-	-	-

DIGIT 3	DIGIT 2	DIGIT 1	DIGIT 0
N/C	N/C	N/C	N/C
N/C	N/C	N/C	A
N/C	N/C	B	A
N/C	C	B	A
D	C	B	A
D	C	B	E
D	K	R	E

SEE CHARACTER SET

LOADING CURSOR

ADDRESS					DATA INPUT						
\overline{CE}	\overline{CU}	\overline{W}	A ₁	A ₀	D6	D5	D4	D3	D2	D1	D0
H	X	X	X	X	X	X	X	X	X	X	X
L	L	L	X	X	X	X	X	L	L	L	H
L	L	L	X	X	X	X	X	L	L	L	L
L	L	L	X	X	X	X	X	L	L	H	L
L	L	L	X	X	X	X	X	L	H	L	L
L	L	L	X	X	X	X	X	H	L	L	L
L	L	L	X	X	X	X	X	H	H	H	H
L	L	L	X	X	X	X	X	L	L	L	L

DIGIT 3	DIGIT 2	DIGIT 1	DIGIT 0
D	K	B	E
D	K	B	.
D	K	B	E
D	K	B	E
D	K	B	E
.	K	B	E
.	K	B	E
D	K	B	E

Fig. 6. Litronix DL-1416 character set and truth table. X=don't care; N/C=no change.

Program listing. Software for reader in 6800 assembler source code.

```

00001          NAM      MORSEMAX (LED VERSION)
00002A 0000          ORG      $0000
00003          * *****
00004          * MORSE CODE/ASCII SEND/RECEIVE PROGRAM
00005          * FOR THE MOTOROLA 6802 MICROPROCESSOR
00006          * FROM AUSTIN, TEXAS
00007          * MICROPROCESSOR CAPITOL OF THE WORLD!
00008          * *****
00009          * I/O HARDWARE CONFIGURATION:
00010          * PIAL ADDRESS - $8004
00011          * CA1 - INTERRUPT TIMING FOR XMIT CODE,
00012          * 2-50 HZ.
00013          * PA7 - RECEIVE CODE INPUT
00014          * PB0 - CODE OUT
00015          * PB1 - TRANSMIT LED
00016          * PB2 - RECEIVE LED
00017          * PIA2 ADDRESS (KBD) - $8020
00018          * LITRONIX DISPLAY DL-1416 4 DIGIT LED - $C000
00019          * WCM2708L EPROM - $E000
00020          * *****
00021          * ALL COMMONLY USED MORSE CHARACTERS
00022          * ARE AVAILABLE:
00023          *
00024          * SPACE - SPACE
00025          * ESC - AS
00026          * = - BT
00027          * CNTRL A - KN
00028          * B - BK
00029          * C - AR
00030          * D - SK
00031          * F - SN
00032          * H - ERROR ( B DOTS )
00033          *
00034          * *****
00035          * *** TEMPORARY STORAGE FOR VARIABLES AND BUFFER ***
00036          *
00037A 0000          0002 A CVCK RMB 2 INDEX REG CONVERT STORE
00038A 0002          0002 A SAVED RMB 2 K-REG TEMP STORAGE
00039A 0002          0001 A COUNT RMB 1
00040A 0004          0001 A RESMSK RMB 1 COSTA RESET MASK
00041A 0005          0001 A BUFLAG RMB 1 B7-1 DATA IN BUFFER
00042A 0006          0003 A TMSVVE RMB 3 TEMP SAVE AREA FOR LED DIS
00043A 0007          0001 A COSTA RMB 1 CODE OUTPUT STATUS
00044A 000A          *B7 DIT FLAG,B6 DAH FLAG,B5 ELEMENT SPACE FLAG
00045          *B4 WORD SPACE FLAG,B3 CHAR. SPACE FLAG
00046          *
00047A 000B          0001 A LETYPE RMB 1 LAST ELEM TYPE DOT=0 DASH
00048A 000C          0001 A HLETIM RMB 1 HALF LAST ELEM TIME
00049A 000D          0001 A TLETIM RMB 1 TWICE LAST ELEM TIME
00050A 000E          0001 A SPEEDK RMB 1 SPEED CONSTANT
00051A 000F          0001 A RCHAR RMB 1 CHAR BEING RECEIVED
00052A 0010          0001 A LDATIM RMB 1 LAST DASH TIME
00053A 0011          0001 A TOLDAT RMB 1 3/4 LAST DASH TIME
00054A 0012          0001 A TLDAT RMB 1 TWICE LAST DASH TIME
00055A 0013          0001 A KDTIM RMB 1 KEYDOWN INTERVAL TIME
00056A 0014          0001 A KUTIM RMB 1 KEYUP INTERVAL TIME
00057A 0015          0001 A CHCTR RMB 1 REC. CHARACTER COUNTER
00058A 0016          0002 A RECK RMB 2 REC. INDEX REG. TO ACCA.
00059A 0018          0055 A BUFBOT RMB 85 XMIT BUFFER BOTTOM
00060A 006D          0001 A BUFTOP RMB 1 XMIT BUFFER TOP

00062          * PIA USED FOR I/O OF CW AND LED STATUS
00063A 8004          0001 A PIALAD ORG $8004
00064A 8004          0001 A PIALAC RMB 1
00065A 8005          0001 A PIALBC RMB 1
00066A 8006          0001 A PIALBD RMB 1
00067A 8007          0001 A PIALBB RMB 1

00069          * PIA USED FOR KEYBOARD INPUT AND LED DISPLAY OUT
00070A 8020          ORG $8020
00071A 8020          0001 A PIA2AD RMB 1 *KEYBOARD
00072A 8021          0001 A PIA2AC RMB 1
00073A 8022          0001 A PIA2BD RMB 1 *DISPLAY
00074A 8023          0001 A PIA2BC RMB 1

00076          007F A STACK EQU 5007F
00077          FFFB A IRQVEC EQU 5FFF8
00078          *
00079A E000          ORG $E000
00080          * KN BK AR SK ACK
00081A E000          00 A CODE FCB 0,$B4,$8B,$54,$16,0,$14,D
00082          ERR SP
00083A E008          01 A FCB 1,0,0,0,0,$21,0,0
00084A E010          00 A FCB 0,0,0,0,0,0,0,0
00085          *
00086A E018          00 A FCB 0,0,0,$44,0,0,0,0
00087          SP *

00088A E020          21 A RTAB FCB $21,0,$4A,0,0,0,0,$7A
00089          *
00090A E028          B6 A FCB $B6,$B2,0,0,$CF,$86,$56,$94
00091          Q 1 2 3 4 5 6 7
00092A E030          FC A FCB $FC,$7C,$3C,$1C,$0C,4,$84,$C4
00093          B 9 1 ; BT(=) ?
00094A E038          E4 A FCB $E4,$F4,$E2,$AA,0,$8C,0,$32
00095          A B C D E F G
00096A E040          00 A FCB 0,$60,$88,$AB,$90,$40,$2B,$D0
00097          H I J K L M N O
00098A E048          08 A FCB $08,$20,$78,$B0,$48,$E0,$A0,$FD
00099          P Q R S T U V W
00100A E050          68 A FCB $68,$D8,$50,$10,$C0,$30,$18,$70
00101          X Y Z
00102A E058          98 A FCB $98,$B8,$C8

00104          * ***RESTART ROUTINE***
00105A E05E CE 007F A RESRT LDX $57F CLR RAM 0-7F
00106A E05E EF 00 A LI CLR 0,X
00107A E060 09 DEX
00108A E061 26 FB E05E BNE LI
00109A E063 CB 2020 A LDX $52020 TMSVVE 'CLEARS TMSVVE'
00110A E066 DF 07 A STX TMSVVE+1
00111A E068 DF 08 A LDX $50F01
00112A E06A CE 0F01 A STX SPEEDK INZ SPEED CONS & RCHAR
00113A E06D DF 0E A LDX $580
00114A E06F 86 80 A STAA BUFTOP INZ BUFTOP
00115A E071 97 6D A STRA DEX
00116A E073 09 LDX $CODE
00117A E074 CF E000 A LDX CVCK INZ CVCK
00118A E077 DF 00 A STX $BUFTOP
00119A E079 CE 006D A LDX $SAVEK
00120A E07C DF 02 A STX $POLL INZ IRQ VECTOR
00121A E07E CE E0B4 A LDX $IRQVEC
00122A E081 FF FFF8 A LDX $PIALAD
00123A E084 CE 8004 A CLR 1,X CLR PIA1AC
00124A E087 6F 01 A CLR 3,X CLR PIA1BC
00125A E089 6F 03 A LOS $50007 CA1+ & ALLOWED
00126A E08B BE 0007 A STS 0,X (PIALAD & PIALAC)
00127A E08E AF 00 A LOS $5FF34
00128A E090 BE FF34 A STS 2,X (PIALB & PIALBC)
00129A E093 AF 02 A LDAA 0,X CLR IRQA FLAGS
00130A E095 AE 00 A LDAA 2,X CLR IRQB FLAGS
00131A E097 AE 02 A LDAA $500
00132A E099 BE 00 A STAA PIA2AD $507
00133A E09B B7 8020 A LDAA PIA2AC CAL NEG INPUT
00134A E09E BE 07 A STAA PIA2BC
00135A E0A0 B7 8021 A LDAA $5F
00136A E0A3 BE FF A STAA PIA2BD SETS PIA2B FOR OUTPUTS
00137A E0A5 B7 8022 A LDAA $504
00138A E0A8 BE 04 A STAA PIA2BC SETS DDR
00139A E0AA B7 8023 A LDX $STACK INZ STACK POINTER
00140A E0AD BE 007F A CLI CLEAR INTERRUPT FLAG
00141A E0B0 0E EXEC WAI
00142A E0B1 3E EXEC BRA EXEC
00143A E0B2 20 FD E0B1 *
00144          *
00145          * ***JUMP FROM IRQ VECTOR***
00146A E0B4 7D 8005 A POLL TST PIA1AC
00147A E0B7 2B DE E0C7 BMI POLL2 (MC1455 IRQ)
00148A E0B9 7D 8021 A TST PIA2AC
00149A E0BC 2B 6A E128 BMI COMM1 (KEYBOARD IRQ)
00150A E0BE 7D 0006 A TST BUFLAG
00151A E0C1 2B 03 E0C6 BMI NOFRCV (DATA IN BUFFER)
00152A E0C3 7E E1E9 A JMP REC
00153A E0C6 3B NOTRCV RTI

00155          * ***TRANSMIT ROUTINE***
00156A E0C7 F6 8004 A POLL2 PIALAD
00157A E0CA F6 8006 A LDAB PIALBD
00158A E0CD CA 02 A ORAB $2
00159A E0CF C4 FB A ANDB $5FB REC LED OFF
00160A E0D1 F7 8006 A STAB PIALBD
00161A E0D4 96 0A A LDAA COSTA GET CODE OUTPUT STATUS
00162A E0D8 2A 07 E0DF BPL CFDAH CHECK FOR DAH
00163A E0DB C6 7F A LDAB RESMSK
00164A E0DD D7 05 A STAB $5F
00165A E0DF 5F CESI CLRB
00166A E0E0 20 29 E108 BRA CKCNT
00167A E0E2 4A CFDAH ASLA
00168A E0E4 2A 08 E0EA BPL CFES
00169A E0E6 C6 BF A LDAB $5BF
00170A E0E8 D7 05 A STAB RESMSK
00171A E0EA C6 04 A LDAB $4
00172A E0EE 20 1E E108 BRA CKCNT

00174A E0EA 48 CPES ASLA TEST FOR ELEMENT SPACE
00175A E0EB 2A 0A E0F7 BPL CFWS CHECK FOR WORD SPACE
00176A E0ED C6 DF A LDAB $5DF
00177A E0EF D7 05 A STAB RESMSK ELEMENT SPACE RESET
00178A E0F1 8D 2C E11F BSR $02E0
00179A E0F3 C6 01 A LDAB $1
00180A E0F5 20 11 E108 BRA CKCNT

```

gram permanently until it is desired to erase it. For a one-time shot, specify the plastic version. Much less expensive, but good only once. On the ceramic types, be sure to keep the adhesive paper over the quartz lid, as it might start to forget if exposed to ultraviolet light. The MC6802 processor contains an on-board clock generation circuit and 128

bytes of RAM. This RAM is used by the processor for temporary storage and for the 85-character keyboard buffer. You can type in up to 85 characters, sit back, and drink your coffee while the code dribbles out. Additional memory could be added—up to 65 thousand characters, and that's what I call a big buffer. With only a little more memory, canned messages

could be inserted and held for a later call-up (before power is turned off)—CQs, tests, QTHs, for example. As the program is right now, only what is typed will be sent out. Almost any crystal between 1 and 4 MHz can be used, so the old junk box can be used for some of the components. Look in an old color TV set—the 3.58-MHz crystal works

well, too. Reset is provided by the resistor-capacitor combination automatically upon power-up conditions. If for any reason the computer does something strange or just quits, turn the power off and back on again. This will reset everything and start over. A note about the keyboard: The program is set up to recognize any keyboard that provides the ASCII code

```

00182A E0F7 48          CPWS  ASLA
00183A E0F8 2A 08 E102 BEL  CPCS  CHECK FOR SPACE
00184A E0FA C6 EF  A    LDAB  $SEF
00185A E0FC D7 05  A    STAB  RESMSK  WORD SPACE RESET
00186A E0FE C6 08  A    LDAB  $8      WORD SPACE BEING SENT
00187A E100 20 06 E108 BRA  CKCNT

00189A E102 C6 F7  A CPCS LDAB  $SF7
00190A E104 D7 05  A    STAB  RESMSK
00191A E106 C6 04  A    LDAB  $4
00192A E108 D1 04  A CKCNT CMB  COUNT
00193A E10A 27 06 E112 BEQ  CK1
00194A E10C 7C 0004 A    INC  COUNT
00195A E10F 7E E0B4 A RETRN JMP  POLL

00197A E112 7F 0004 A CK1  CLR  COUNT
00198A E115 96 0A  A    LDAA  COSTA
00199A E117 94 05  A    ANDA  RESMSK
00200A E119 97 0A  A    STAA  COSTA
00201A E118 26 F2 E10F BNE  RETRN
00202A E11D 20 14 E133 BRA  GNEL

00204          ***SEND OUT A ZERO***
00205A E11F B6 8006 A SOZERO LDAA  PIALBD
00206A E122 84 FE  A    ANDA  $SFE
00207A E124 B7 8006 A    STAA  PIALBD
00208A E127 39          RTS
00209A E128 20 64 E18E COMMRL BRA  COMMNR

00211          ***SEND OUT A ONE***
00212A E12A B6 8006 A SOONE  LDAA  PIALBD
00213A E12D 8A 01  A    ORAA  $1      SET BIT ZERO
00214A E12F B7 8006 A    STAA  PIALBD
00215A E132 39          RTS

00217          ***GET NEW ELEMENT FOR OUTPUT***
00218A E133 96 6D  A GNEL  LDAA  BUFTOP
00219A E135 81 80  A    CMFA  $880  TEST FOR CHAR END
00220A E137 26 26 E15F BNE  GNEL1
00221A E139 86 08  A    LDAA  $808  SEND OUT CHAR. SPACE
00222A E13B 97 0A  A    STAA  COSTA
00223A E13D 8D ED E11F BSR  SOZERO
00224A E13F DE 02  A    LDX  SAVEX
00225A E141 8C 006D A    CPX  $BUFTOP
00226A E144 26 09 E14F BNE  GNELR
00227A E146 96 06  A    LDAA  BUFLAG  BUFFER EMPTY
00228A E148 84 7F  A    ANDA  $57F
00229A E14A 97 06  A    STAA  BUFLAG  RESET FLAG
00230A E14C 7E E0B4 A    JMP  POLL

00231          *
00232A E14F 8D 2D E17E GNELR BSR  MOVUP
00233A E151 96 6D  A    LDAA  BUFTOP
00234A E153 81 21  A    CMFA  $521  LOOK FOR SPACE
00235A E155 27 1A E171 BEQ  SWS
00236A E157 7D 000A A    TST  COSTA
00237A E15A 27 03 E15F BEQ  GNEL1
00238A E15C 7E E0B4 A    JMP  POLL

00239          *
00240A E15F 78 006D A GNED1 ASL  BUFTOP
00241A E162 25 04 E168 BCS  SODAH
00242A E164 86 A0  A    LDAA  $8A0  SEND OUT DAB
00243A E166 20 02 E16A BRA  SOEL  SEND OUT DIT & ELEMENT SPA
00244          *
00245A E168 86 60  A SODAH LDAA  $560  SEND OUT DAB & ELEMENT SPAC
00246A E16A 97 0A  A SOEL  STAA  COSTA  SET STATUS
00247A E16C 8D BC E12A BSR  SOONE
00248A E16E 7E E0B4 A    JMP  POLL

00249          *
00250A E171 86 80  A SWS  LDAA  $880
00251A E173 97 6D  A    STAA  BUFTOP
00252A E175 86 10  A    LDAA  $510
00253A E177 97 0A  A    STAA  COSTA  SEND OUT WORD SPACE
00254A E179 8D A4 E11F BSR  SOZERO
00255A E17B 7E E0B4 A    JMP  POLL

00256          *
00257A E17E CE 0055 A MOVUP LDX  $BUFTOP-BUFBOT
00258A E181 A6 17  A MOV1  LDAA  BUFBOT-1,X
00259A E183 A7 18  A    STAA  BUFBOT,X
00260A E185 09          DEK
00261A E186 26 F9 E181 BNE  MOV1
00262A E188 08 02  A    LDX  SAVEX  UPDATE INPUT POINTER
00263A E18A 08          INX
00264A E18B DF 02  A    STX  SAVEX
00265A E18D 39          MOVRT RTS

00266          ***COMM REC INTERRUPT ROUTINE***
00266A E18E DE 02  A COMMRL LDK  SAVEX
00266A E190 B6 8020 A    LDAA  PIA2AD  GET KB DATA
00270A E193 BC 0018 A    CPX  $BUFBOT
00271A E196 27 49 E1F1 BEQ  BUFPUL  MEMORY BUFFER FULL
00272A E198 81 5A  A    CMFA  $85A
00273A E19A 22 49 E1E5 BHI  BADCH  ILLEGAL CHAR
00274A E19C 97 01  A STM  STAA  CVCKX-1

00275A E19E DE 00  A    LDX  CVCK
00276A E1A0 E6 00  A    LDAB  0,X  DATA CONVERTED TO MORSE CO
00277A E1A2 27 41 E1E5 BEQ  BADCH  KICK OUT BAD CHAR'S
00278A E1A4 DE 02  A    LDX  SAVEX
00279A E1A6 09          DEK
00280A E1A7 E7 00  A    STAB  0,X  STORE DATA IN BUFFER
00281A E1A9 DF 02  A    STX  SAVEX  MOVE POINTER DOWN
00282A E1AB D6 06  A    LDAB  BUFLAG
00283A E1AD CA 80  A    ORAB  $880  SET FLAG BIT 7
00284A E1AF D7 06  A    STAB  BUFLAG
00285A E1B1 8D 03 E1B6 PRNT BSR  OUTCH  PRINT CHARACTER
00286A E1B3 7E E0B4 A    JMP  POLL

00287          ***PRINT CHARACTER ROUTINE***
00288A E1B6 36          OUTCH PSHA  SAVE LSR CHARACTER
00289A E1B7 C6 C0  A    LDAB  $8C0
00290A E1B9 CE 0009 A    LDX  $TMP5VE+2
00291A E1BC A6 00  A    LDAA  0,X
00292A E1BE 8D 10 E1D0 OUTCH1 BSR  STROBE
00293A E1C0 09          DEK
00294A E1C1 A6 00  A    LDAA  0,X
00295A E1C3 A7 01  A    STAA  1,X
00296A E1C5 C0 40  A    SUBB  $840
00297A E1C7 26 F5 E1BE BNE  OUTCH1
00298A E1C9 32          PULA
00299A E1CA 84 3F  A    ANDA  $83F  STRIPS BIT 6 AND 7
00300A E1CC 97 07  A    STAA  TMP5VE
00301A E1CE 20 00 E1D0 BRA  STROBE
00302A E1D0 1B          STROBE ABA
00303A E1D1 B7 8022 A    STAR  PIA2BD  WRITE INTO APPROPRIATE DIG
00304A E1D4 86 34  A    LDAA  BIT 3 = 0
00305A E1D6 B7 8023 A    STAA  PIA2BC  PULSES CB2 LOW
00306A E1D9 86 3C  A    LDAA  BIT 3 = 1
00307A E1DB B7 8023 A    STAA  PIA2BC  AND BACK AGAIN FOR
00308A E1DE 39          RTS  WRITE PULSE
00309A E1DF 20 AD E18E COMMRL BRA  COMMNR
00310          *
00311A E1E1 86 2A  A RUFFUL LDAA  $*  PRINT '*' FOR RUFFER FULL
00312A E1E3 20 CC E1B1 BRA  PRNT
00313          *
00314          *
00315A E1E5 86 23 A RADCH LDAA  $523  PRINT '#' FOR RAD CHAP
00316A E1E7 20 C8 E1B1 BRA  PRNT

00318          ***START OF RECEIVE ROUTINE***
00318A E1F9 B6 8006 A REC  LDAA  PIALBD
00320A E1FC 8A 04  A    ORAA  $4  REC LED ON
00321A E1FE 84 8D  A    ANDA  $84D  XMIT LED OFF
00322A E1F0 B7 8006 A    STAA  PIALBD
00323A E1F3 86 FF  A KEYUP LDAA  $SFF  RESET INTERVAL COUNTER
00324A E1F5 81 FE  A KULoop CMFA  $SFE  INTERVAL COUNTER AT MAX?
00325A E1F7 27 03 E1FC BEQ  NOINC  DO NOT INCR IF MAX
00326A E1F9 4C          INCA  INCR INCREMENT INTERVAL COUNTER
00327A E1FA 20 0A E206 BRA  KUCONT

00329A E1FC 97 14  A NOINC STAA  KUTIM  SAVE KU INTERVAL TIME
00330A E1FE D6 0F  A    LDAB  RCHAR  GET RCVD CHAR
00331A E200 C1 01  A    CMFB  $1  ANYTHING THERE?
00332A E202 27 02 E206 BEQ  KUCONT
00333A E204 8D 4C E252 BSR  COMPKU
00334A E206 F6 8004 A RUCONT LDAB  PIA1AD  CHECK INPUT
00335A E209 2B 09 E214 BMT  KD  BRANCH IF KEYDOWN
00336A E20B 8D 36 E243 BSR  TIMER  TIME DELAY

00338A E20D 7D 8021 A    TST  PIA2AC  TESTS BIT 7 TO SEE IF DATA
00339A E210 2B CD E1DF COMMR2 BMT  IF DATA THN XMIT
00340A E212 2D E1 E1F5 BRA  KULoop
00341A E214 97 14  A KD  STAA  KUTIM  SAVE KU INTERVAL TIME
00342A E216 8D 3A E252 BSR  COMPKU
00343A E218 86 FF  A KEYDWN LDAA  $SFF  RESET INTERVAL TIME
00344A E21A 81 FE  A KDLoop CMFA  $SFE  INTERVAL COUNTER AT MAX?
00345A E21C 27 01 E21F BEQ  MAXKD  DO NOT INCR IF MAX
00346A E21E 4C          INCA  INCR INCREMENT INTERVAL COUNTER
00347A E21F F6 8004 A MAXKD LDAB  PIA1AD  CHECK INPUT
00348A E222 2A 04 E228 BPL  KU  BRANCH IF KEYUP
00349A E224 8D 1D E243 BSR  TIMER  TIME DELAY
00350A E226 20 F2 E21A BRA  KDLoop

00352A E228 97 13  A KU  STAA  KUTIM  SAVE KU INTERVAL TIME
00353A E22A 81 04  A    CMFA  $4  KU INTERVAL TIME TOO LOW?
00354A E22C 24 05 E233 BCC  CKNI  BRANCH IF NOT TOO LOW
00355A E22E 96 0E  A    LDAA  SPEEDK
00356A E230 44          LSR  DIVIDE SPEED CONSTANT BY 2
00357A E231 20 07 E23A BRA  UNZERO

00359A E233 81 7F  A CKNI  CMFA  $87F  KD INTERVAL TIME TOO HIGH?
00360A E235 25 07 E23E BCS  CMPTND BRANCH IF OK
00361A E237 96 0E  A    LDAA  SPEEDK
00362A E239 48          ASLA  MULTIPLY SPEED CONSTANT BY

```

Continued

set and a negative-going strobe. There are many available from wholesale houses for \$20.00 and up.

Key Characters Available

The computer will generate all of the Morse characters plus some special function keys which can be generated by the use of the CNTRL key. A list of them follows:

Control A - KN
 B - BK
 C - AR
 D - SK
 F - SN
 H - ERROR (8 dots)
 = - BT
 ESC - AS
 SPACE - SPACE

A "space" will insert a space in the buffer to be transmitted along with the code, thereby making per-

fect Morse every time. While typing, if you should reach the top of the buffer, the character you try to enter will be displayed as an *, meaning that it did not get entered and you should reenter it after one character has been sent.

Any illegal character typed will appear as a # and will not get sent. Any received character which the computer cannot

figure out—like run-together characters—will be displayed as an __, and an error (8 dots) will be an @.

Parts Procurement

All parts (with the exception of the DL-1416) can be obtained from your local Motorola distributor, and the 1416 comes from a Litronix distributor. All of the parts should tally to


```

00363A E23A 8A 01 A UNZERO ORAA #1 ASCERTAIN SPEED CONSTANT I
00364A E23C 97 0E A STAA SPEEDK NOT SET TO ZERO
00365A E23E 8D 31 E271 CMPTRD COMPKD
00366A E240 7E E1F3 A JMP KEYUP

00368 ***SUBROUTINE TO CREATE TIME DELAY***
00369A E243 37 TIMER PSHB SAVE B
00370A E244 36 PSHA SAVE A
00371A E245 06 0E A LDAB SPEEDK
00372A E247 86 40 A DELOP2 LDAA #540
00373A E249 4A DELOOP DECA
00374A E24A 26 FD E249 BNE DELOOP
00375A E24C 5A DECB
00376A E24D 26 FB E247 BNE DELOP2
00377A E24F 32 PULA RESTORE A
00378A E250 33 PULB RESTORE B
00379A E251 39 RTS

00381 ***SUBROUTINE TO COMPUTE KU***
00382A E252 91 11 A COMPKD CMPA TQLDAT
00383A E254 25 1A E270 BCS MOREL BRANCH IF XUTIM ^ TQLDAT
00384A E256 96 0F A LDAA RCHAR GET CHAR BEING RECEIVED
00385A E258 81 01 A CMPA #1
00386A E25A 27 09 E265 BEQ CKFSP
00387A E25C 8D 4A E2A8 BSR GAPT GET ASCII FROM TABLE
00388A E25E 8D E1B6 A JSR OUTCH PRINT CHARACTER IN ACCA
00389A E261 86 01 A LDAA #1
00390A E263 97 0F A STAA RCHAR READY FOR NEW CHAR
00391A E265 96 12 A CKFSP LDAA TLDAT GET TWICE LAST DASH TIME
00392A E267 91 14 A CHEA RUTIM COMPARE WITH KU INTERVAL
00393A E269 24 05 E270 BCC MOREL BRANCH IF TLDAT = KU INTR
00394A E26B 86 20 A LDAA #S20 ASCII SPACE
00395A E26D 8D E1B6 A JSR OUTCH PRINT SPACE
00396A E270 39 MOREL RTS

00398 ***SUBROUTINE TO COMPUTE KD***
00399A E271 96 0D A COMPKD LDAA TLETIM GET TWICE LAST ELEM TIME
00400A E273 91 13 A CMPA KDTIM COMPARE WITH KD INTERVAL
00401A E275 25 10 E287 BCS DASHL BRANCH IF TLETIM ^ KD INTR
00402A E277 96 0C A LDAA HLETIM GET HALF LAST ELEM TIME
00403A E279 91 13 A CMPA KDTIM COMPARE WITH KD INTERVAL
00404A E27B 24 04 E281 BCC DOTEI BRANCH IF HLETIM ^ KD INT
00405A E27D 96 0B A LDAA LETYPE CHECK LAST ELEMENT TYPE
00406A E27F 26 06 E287 BNE DASHL BRANCH IF LAST ELEM WAS DA
00407A E281 7F 000B A DOTEI CLR LETYPE MAKE LAST ELEM TYPE=00=DOT
00408A E284 0C CLC
00409A E285 20 14 E29B BRA ADDEL
00410A E287 7C 000B A DASHL INC LETYPE MAKE LAST ELEM TYPE=DASH
00411A E28A 96 13 A LDAA KDTIM GET KD INTERVAL
00412A E28C 97 10 A STAA LDATIM STORE IN LAST DASH TIME
00413A E28E 16 TAB
00414A E28F 44 LSRA DIVIDE KD INTERVAL BY 2
00415A E290 97 11 A STAA TQLDAT SAVE 1/2 KD
00416A E292 44 LSRA DIVIDE 1/2 KD BY 2
00417A E293 9B 11 A ADDA TQLDAT ADD 1/2 TO 1/4 KD INTERVAL
00418A E295 97 11 A STAA TQLDAT STORE RESULT
00419A E297 58 ASLB MULTIPLY KD INTERVAL BY 2
00420A E298 D7 12 A STAB TLDAT STORE RESULT
00421A E29A 0D SEC
00422A E29B 79 000F A ADDEL ROL RCHAR ADD NEW ELEM TO CHARACTER
00423A E29E 96 13 A LDAA KDTIM GET KD INTERVAL
00424A E2A0 16 TAB
00425A E2A1 44 LSRA DIVIDE KD BY 2
00426A E2A2 97 0C A STAA HLETIM STORE 1/2 KD INTERVAL
00427A E2A4 58 ASLB MULTIPLY KD BY 2
00428A E2A5 D7 DD A STAB TLETIM STORE TWICE KD INTERVAL
00429A E2A7 39 RTS

00431 ***SUBR. TO GET ASCII CHAR FROM CODE TABLE***
00432A E2AB 0D GAPT SEC CHANGE FORMAT OF RCHAR.
00433A E2A9 49 BCC ROLA
00434A E2AA 48 GAPT1 ASLA
00435A E2AB 24 FD E2AA BCC LDAA
00436A E2AD CE E05A A LDX #RESRT-1
00437A E2B0 A1 00 A STAB1 CMPA 0,X
00438A E2B2 27 09 E2BD BEQ TABM FOUND MATCH
00439A E2B4 09 DEX
00440A E2B5 8C E021 A CPX #RTAB+1 END OF TABLE?
00441A E2B8 26 F6 E2B0 BNE STAB1 NO!
00442A E2BA 86 5F A LDAA #'_ RETURN '_' FOR NO MATCH
00443A E2BC 39 RTS
00444 *
00445A E2BD DF 16 A TABM STX RECX
00446A E2BF 96 17 A LDAA RECX+1 X(LOW) TO ACCA.
00447A E2C1 39 RTS

00449 ***INITIALIZATION AND RESTART VECTORS***
00451A E3F8 ORG CODE+S3F8
00452A E3F8 FDB POLL IRQ
00453A E3FA FDB RESRT SWI
00454A E3FC FDB RESRT NMI
00455A E3FE FDB RESRT RESET
00456 END
TOTAL ERRORS 00000

```

less than \$80-\$90, including the display, which is \$30 in quantities of one.

Operation

Operation of the reader-talker is quite simple. Hook up the required power supplies, the cords to the speaker and key jacks, and go to town. The easiest way to tune in a signal is to use the on-board headphone

jack and set the selectivity to 40 Hz. When you hear the signal, watch the LED, and when it starts to blink at the incoming CW rate, switch the filter to the processed mode and tune for the cleanest signal. An RIT control is almost a must as the input tuning is quite sharp, and if you tune the other guy for the best signal each time he gives it

back to you, you could walk right up or down the band!

The only drawback I have found is that when copying at fast speeds, the display will run words together, since most operators do not leave enough space between them. I understand that most of the keyboard keys do not have a space key on them,

and this will explain some of the problems. The others are self-explanatory. As I said earlier, the lack of more digits on the board is not a hindrance, and after you use it a while, you'll agree. Whether you use a PC board or wire-wrap this project, it will be a great addition to any ham shack and do a lot for cleaning up the airways. ■