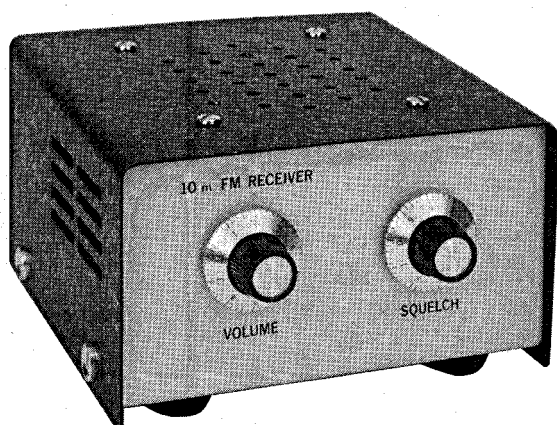


A Simple 10-Meter FM Receiver



Need a 10-meter FM receiver for the SSTV signals WØORE will be sending back from the Shuttle? Build this simple, inexpensive receiver and you'll be ready for "Live, from space, it's ham radio!"

By Jonathan F. Towle,* WB1DNL

When Astronaut Tony England, WØORE, lifts off the launch pad later this spring and heads for space, he'll be using SSTV equipment and a 10-meter FM transmitter along with the regular 2-meter FM gear. If your station equipment is not capable of receiving FM signals on the 10-meter band, here's a simple FM receiver that can be built at home.

The only active circuit components are three ICs. Most parts are available from your local electronics supply house or your local Radio Shack. The second-LO crystal, the crystal filter, the RF coil in the front-end and the coil in the first LO are available from Semiconductors Surplus, Mouser Electronics or Amidon Associates (see Table 1).

A single 9-V supply was chosen to keep the project simple. Lower voltages limit the range of the audio amplifier, and higher voltages required more extensive regulation to operate the RF front-end IC.

General Description

The block diagram in Fig. 1 may appear incomplete because many of the discrete parts you might expect to find in a typical FM receiver are contained within the ICs. The local oscillators are shown as separate blocks to indicate the frequency mixing that occurs in the circuit. The active components, however, are contained in the ICs.

The signal from the antenna is amplified and then mixed with a 39.7- to 40.4-MHz signal produced in the first LO. This creates a 10.7-MHz intermediate frequency (IF). This signal passes through a 10.7-MHz crystal band-pass filter into the narrow-band FM IC.

A second mixing process converts the 10.7-MHz IF to 455 kHz. The second IF

Table 1
Parts Suppliers

Radio Shack (RS).
Semiconductors Surplus (SS), 2822 No. 32nd St. Unit 1, Phoenix, AZ 85008, tel. 602-956-9423.
Mouser Electronics (M), P.O. Box C, Lakeside, CA 92040, tel. 619-449-2222.
Amidon Associates, 12033 Otsego Street, North Hollywood, CA 91607, tel. 213-760-4429.

is routed through a band-pass filter and then to a limiting amplifier to remove any AM signal components. Audio is recovered by a quadrature FM detector and sent to the squelch circuit and the audio amplifier. The squelch circuit is activated by noise when no audio signal is present. When the squelch circuit is triggered, the audio mute output grounds the audio amplifier input.

The audio amplifier is a high-gain device that provides more than enough output to drive an 8-ohm speaker. Frequency response is determined by the values of the components coupling the audio amplifier to the narrow-band FM IF IC.

Circuit Details

Refer to Fig. 2. Because all the active

components in this receiver are contained in the three ICs, only four parts of the circuit must be tuned. Two are in the first LO, one in the front end, and the fourth is the coil in the quadrature discriminator.

The first LO uses a parallel LC circuit. L1 is a Zenith Radio coil of 6½ turns on a molded plastic form with an adjustable slug. A fixed-value silver mica and a trimmer capacitor, C1, complete the circuit. Tuning is accomplished by adjusting the trimmer capacitor after the circuit is brought into the correct range by adjusting the inductor.

The RF front-end coil, L2, consists of 18 turns of no. 28 enameled wire, center tapped, wound on an Amidon T-37-10 black ($\mu = 6$) toroid core. Again, a fixed capacitor and a trimmer capacitor, C2, are used to resonate the circuit to the input frequency.

The SK7669 front-end chip is a low-power device that provides about 20 dB of conversion gain. The series diodes in the 9-V supply lead drop the voltage to the correct value for the device.

RF from the antenna is coupled into the device through a 0.01- μ F capacitor coupled to pin 1. The output from pin 6 is connected to the crystal filter; filter bandwidth is approximately 15 kHz. The insertion loss

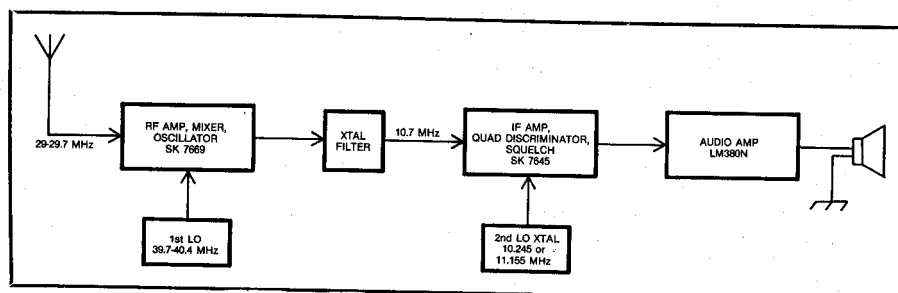


Fig. 1 — Block diagram showing frequency-mixing scheme of 10-meter FM receiver.

*ARRL Laboratory Engineer

Fig. 2 — Schematic diagram for 10-meter FM receiver.

20 Q5T-

