

A 2 metre VSWR Bridge



M. H. Tooley BA G8CKT & D. Whitfield BA G8FTB

Introduction

Matching the aerial to the transmitter, in order to obtain maximum radiated power, is an important consideration for any radio amateur hoping to obtain the best results from his equipment: this can be achieved by using some form of standing wave meter in the tuning-up procedure. The standing wave ratio (s.w.r.) is a measure of the efficiency of an aerial system: the closer the s.w.r. is to unity, the greater the proportion of transmitter power actually radiated. Although the s.w.r. only approaches unity under ideal conditions, in practical situations its measurement will provide a very useful evaluation of the system's performance.

The instrument described is an s.w.r. bridge which will provide a constant, on-the-air reading whilst allowing meaningful measurements to be made on the relative merits of different aeriels and aerial sites. It is suitable for use in the feeders of v.h.f. transmitters having outputs of between 1W and 100W.

Circuit Description

An s.w.r. bridge works by sampling the amount of power flowing in each direction along the aerial feeder. This is achieved by the use of a Maxwell bridge transmission line coupler, as shown in Fig. 1. The reactive arms of the bridge are formed by the distributed capacitance and mutual inductance of the coupled lines. The two sampling lines L1 and L2, shown in the circuit diagram of Fig. 2, are coupled to the main aerial feeder and respectively terminated at opposite ends by R1 and R2, thus providing two outputs which are proportional to the forward and reflected signals present. Diodes D1, D2 and capacitors C1, C2 convert the sampled signals to d.c. for measurement on a conventional meter M1. Potentiometer VR1 adjusts the sensitivity of the circuit and ferrite beads prevent stray r.f. pick-up in the wiring.

In practice, the bridge can be used either way round due to the symmetry of the circuit, but for convenience, SK1 is assigned to the transmitter and SK2 to the load; this allows S1 to be designated "forward" and "reflected."

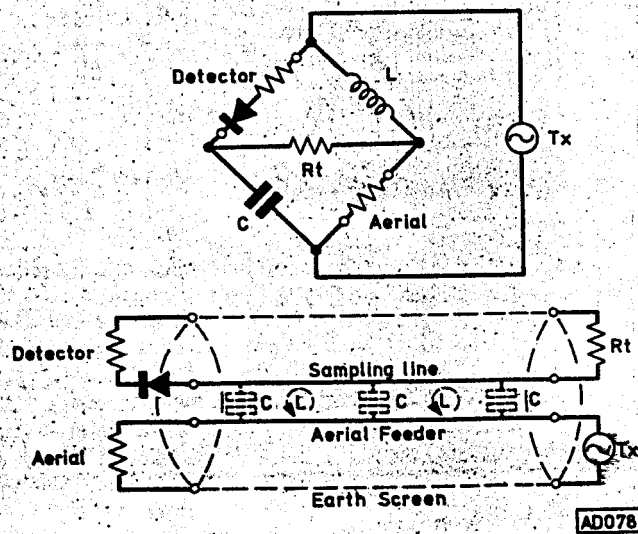


Fig. 1: Theoretical diagram of the Maxwell Bridge transmission line coupler

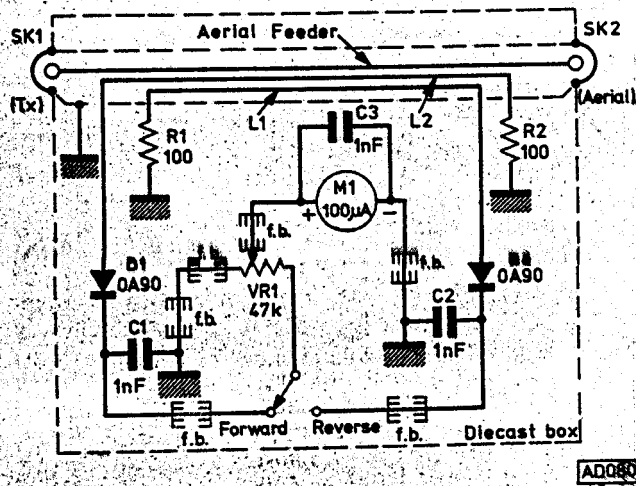


Fig. 2: Complete circuit diagram of the 2m VSWR bridge

Practical Wireless, May 1976

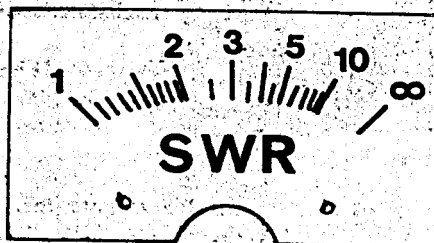
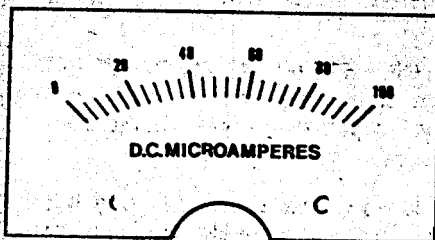


Fig. 5: Meter calibration scale for use with Maplin type '2 in PAN' meter. The original 100µA meter scale (left). Replacement scale for s.w.r. measurement (right). Both shown actual size

Calibration

Using the recommended meter movement the instrument may be calibrated simply by copying the scale shown full size in Fig. 5. For alternative types of movement a table of calibration points is given. The new meter scale is best marked with the scale plate detached from the movement, using a fine pen and drawing ink, pencil or dry transfers.

S.W.R.	Reverse Reading (µA)	S.W.R.	Reverse Reading (µA)
1:1	0	2.5:1	43
1.1:1	5	3:1	50
1.2:1	9	3.5:1	56
1.3:1	13	4:1	60
1.4:1	17	4.5:1	64
1.5:1	20	5:1	67
1.6:1	23	6:1	71
1.7:1	26	7:1	75
1.8:1	29	8:1	78
1.9:1	31	9:1	80
2:1	33	10:1	82

Using the S.W.R. Bridge

Attach the output of the v.h.f. transmitter to SK1 and the aerial system or some other form of load to SK2, using matched feeder. Set S1 to read forward power and turn VR1 fully anticlockwise for minimum meter sensitivity. Apply r.f. power from the transmitter and adjust VR1 for a full-scale meter reading. Leaving the setting of VR1 unchanged, set S1 to read reverse power: the meter will now indicate s.w.r. directly.

It should be noted that continuous high-power operation of the s.w.r. bridge without a load may cause the 100 ohm resistors and the diodes to be destroyed. The bridge may be left permanently inline with the feeder between transmitter and aerial, as it introduces no significant signal degradation in either direction. Constructors should be wary of placing too much importance on absolute s.w.r. readings; the real value of the bridge lies in its ability to indicate relative forward and reverse power levels. It will be found invaluable as a general aid in the adjustment of transmitters and aeriels.

★ components

Capacitors	
C1	1nF disc ceramic
C2	1nF disc ceramic
C3	1nF disc ceramic
Resistors	
R1	100 ohms 1W 2%
R2	100 ohms 1W 2%
VR1	47kΩ linear carbon
Diodes	
D1	0A90
D2	0A90 (See text)
Sockets	
SK1	50Ω BNC
SK2	50Ω BNC
Lines	
L1	250mm 28 swg enamelled copper wire
L2	250mm 28 swg enamelled copper wire
	140mm low-loss 50Ω coaxial cable (see Department)
	56pF in (UR250)
Miscellaneous	
	Diode box approximately 120mm diameter
	100µA 2in panel meter
	Minimizers (single)
	1000 ohm resistor
	100 500 1000 ohm resistors
	100 500 1000 ohm resistors
	100 500 1000 ohm resistors
	100 500 1000 ohm resistors
	100 500 1000 ohm resistors
	100 500 1000 ohm resistors

BINDERS FOR PW

Keep your copies together
Keep them clean
with the
PW Easi-Binder

The Easi-Binder is attractively bound with the title blocked in gold on the spine with the current (or last) volume number and year. For any previous volume numbers please advise year and volume and a separate set of gold transfer figures will be supplied.

£2.85 inclusive of VAT and post and packaging from: Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London, SE1 0PF.
(Overseas orders please add 60p).