

# HI-FI OUTPUT TRANSFORMER

BY W. GROOME

USE OF A TERTIARY FEEDBACK WINDING ARRANGEMENT SIMPLIFIES CONSTRUCTION OF THIS TRANSFORMER AND REDUCES THE COST.

(Continued from page 400 of the September issue)

Last month's article the author began an account of his home-made transformer which included descriptions of some interesting circuits. In Fig. 4, for example, a triode "see-phase-splitter" amplifier stage feeds the output. The tertiary winding, carried on one of the cathode current pentodes were used for the phase-splitter stage the sensitivity, held by the feedback and with it the amplifier unity, can be made variable using the tertiary winding and a 1000 potentiometer and the feedback voltage from it, as shown in Fig. 5 (last page). This refinement may be of use to some experimenters, but a triode circuit will be found for most domestic purposes. The ECL82 valve, comprising an amplifier triode and an ECL82 valve, comprising a pentode enables a two-pull amplifier to be around only two valves—two using only four valves a practical proposition.

**Follower Output**  
An improvement achieved by use of feedback over the output stage (apart from easing the strain of overall feedback) is a "natural sound" that is not likely to show up on instrument tests, real enough, however, and the popular cathode-follower circuit with its virtually complete elimination of its own distortion immunity from the errors that arise in a feedback loop, gives a realism that is still hard to rival. Its limitation to triode efficiency and the grid voltage swing needed for full loading caused it to decline in popularity and designs suitable for pentodes have become more numerous.



One of the author's prototype experimental output transformers.

in an earlier paragraph, is a highly desirable method of obtaining output stage feedback. Despite the strangeness, on paper, of a load distributed between anode and cathode, the relationship to the ultra-linear arrangement can be appreciated when the screen is considered, this being tapped into the transformer load in both cases. This is obvious in the ultra-linear circuit in Fig. 7, it is still loaded by the transformer because its current and signal are compelled to flow in the cathode winding.

sections with free leads, it can be connected in the ultra-linear mode as shown in Fig. 7. It is true that the tap at 50% is higher than is customary but this closer approach to triode conditions has not been found to be the slightest drawback. Ultra-linear connections are not the only, or even the first, form of distributed load circuit, for a more elegant circuit was developed in this country several years before the "ultra-linear" circuit appeared. However, the version shown in (Fig. 7) embodies cathode loading which, as stated


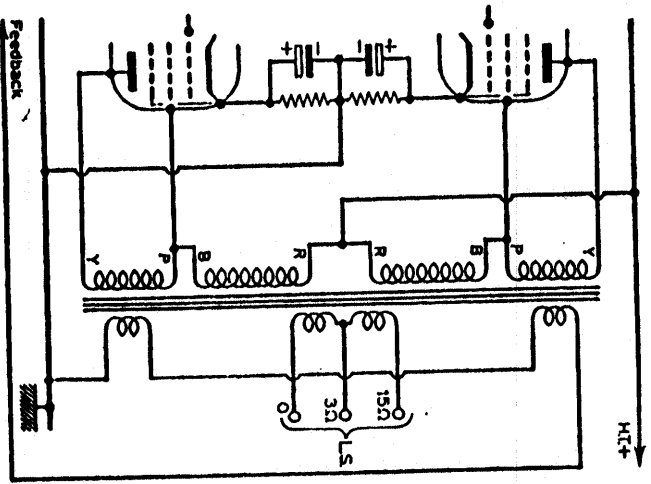


Fig. 6 (left)—Connections for ultra-linear loading.

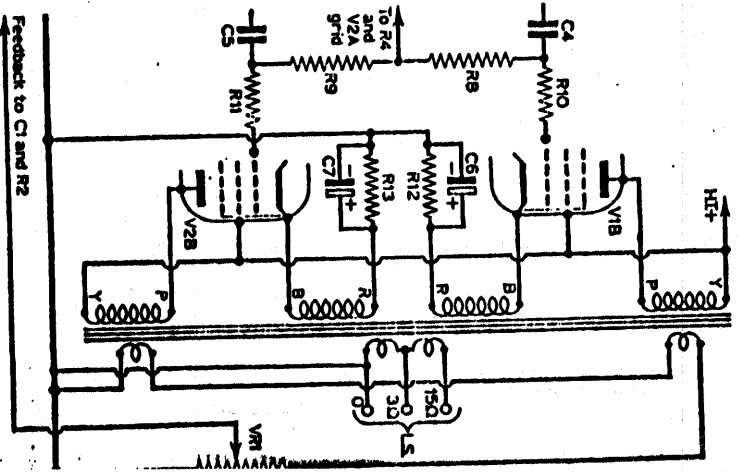

**50 : 50 Distribution**  
This form of loading can be tried by connecting the transformer as indicated in Fig. 8. Bear in mind, however, that the output circuit is patented. The transformer and its associated circuits must not be compared with a well-known make of amplifiers to which this form of loading is exclusive. As 50:50 load distribution must be used, the output stage feedback is already nearly enough to give the required reduction in distortion and output impedance and the amount needed in the overall loop is therefore small. For this reason, a potentiometer is shown across the feedback winding in Fig. 8, which shows the ECL82 circuit modified for this form of loading.

As the grid resistors are returned to earth (via the grid resistor of V2A) the D.C. resistance of the cathode loads contributes towards the bias voltage of the output stage.

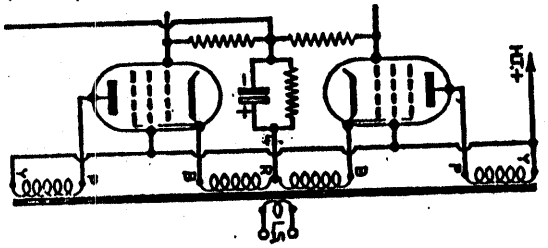


Fig. 7 (right)—Here the load is distributed between anode and cathode.

The resistance of these portions of the windings should therefore be checked at the value of the bias resistors, rather correspondingly. A variation of this for distributed loading has the cathode ends of the load and adjustment of the bias resistors is needed. It is not really suitable for use with a "see-phase splitter", but can be driven by a "conventional" circuit either in the straight form or in the big gain version, one of which employs the big resistance of the phase-splitter to load an amplifier pentode, and another using the pentode in screen anode conditions. This phase-splitter can also be used in a positive feedback circuit, "clean" at every stage rather than have to clean up an accumulation of distortions with the feedback loop.

**Input Signal**

Now that crystal pick-ups have reached the fidelity standard, with outputs so much greater than the magnetic types that were once essential for the discriminating listener, and radio tuners also deliver large signals, there is no longer any urgent need for great sensitivity in the domestic amplifier. Indeed, amplifiers requiring as much

# HI-FI OUTPUT TRANSFORMER

A HOME-MADE

BY W. GROOME

THE USE OF A TERTIARY FEEDBACK WINDING ARRANGEMENT SIMPLIFIES THE CONSTRUCTION OF THIS TRANSFORMER AND REDUCES THE COST.

THE section diagram of one of the author's tertiary-wound transformers is shown in Fig. 1, which may seem, at first glance, to be as complex as the conventional high quality product, but it is really quite a simple job for the enthusiastic home constructor. Sections 1 and 7 are only of 20 turns each spaced to form single layers and the secondary (4) is a simple winding of about a hundred turns. The primary is so arranged that sections 2 and 5, serving one valve,

(Continued from page 502 of the Odo

any audibly detectable loss of quality. Because of this, a departure has been taken from the usual rigid specification that an amateur's choice of material (and therefore the cost) is far from being a secondary detail. It is a detail which is available to the amateur.

Stripping down an old component is a simple job, and wire too. It is a slight simplification in the job of the constructor, but it is a simplification because, as stripping proceeds, the number of layers can be counted and the number of primary turns to put on the secondary at least equal to, and probably more than, the original component can be counted. It will be a useful guide, but not quite a foolproof one, because some extra insulation will be used up on the secondary winding, and the turns must be the same as the primary.

The constructor who does not possess the necessary tools will have to make do with a wire gauge and number of turns. The transformer will be given. The transformer is a special checked and partitioned bobbin of the simple former most often used in Fig. 10, can be made at 1 1/2 inches, Perspex or even cardboard. The bobbins look rather the worse for wear, but they can be made to suit the purpose.

Set the dimensions by measurement of the laminations. The end cheeks and the partition are identical, and can be scribed on a piece of card or paper. The leads to be brought out if rigidly fixed. Alternatively, with cardboard, they can be brought out through holes pierced with a sharp pointed tool. A bobbin made of square section will wind more smoothly than one made for a rectangular stack. A gear brace makes a useful winder when a gear is used. Check the gear ratio by counting the revolutions for one turn of the handle. It shows one simple way of fitting the bobbin. It comprises a woodcrescent drive piece of wood of the same size and sec-

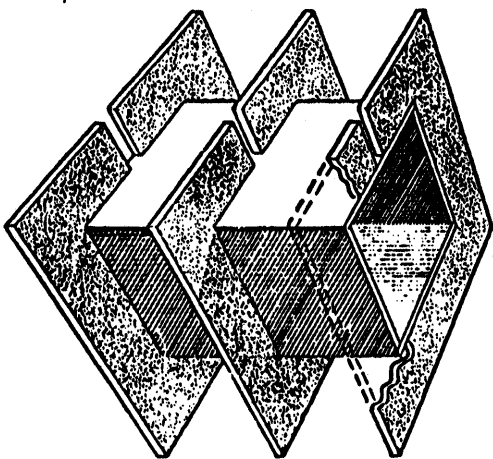


Fig. 10—The construction of the bobbin.

match 3 and 6 for the other much more accurately than the more usual arrangement in which only the number of turns—and nothing else—can be matched.

### Laminations

The amateur's main difficulty is obtaining core material for very few dealers carry laminations in stock and the delivery for small orders of one or two stacks seems somewhat lengthy. Fortunately, the tertiary-wound transformer is so stable, so free of trouble in the use of heavy negative feedback, that quite generous tolerance

# A

making a good provision when heater which it may 2. The

where in the for a 1 A then wood

Fig.

1,000

the

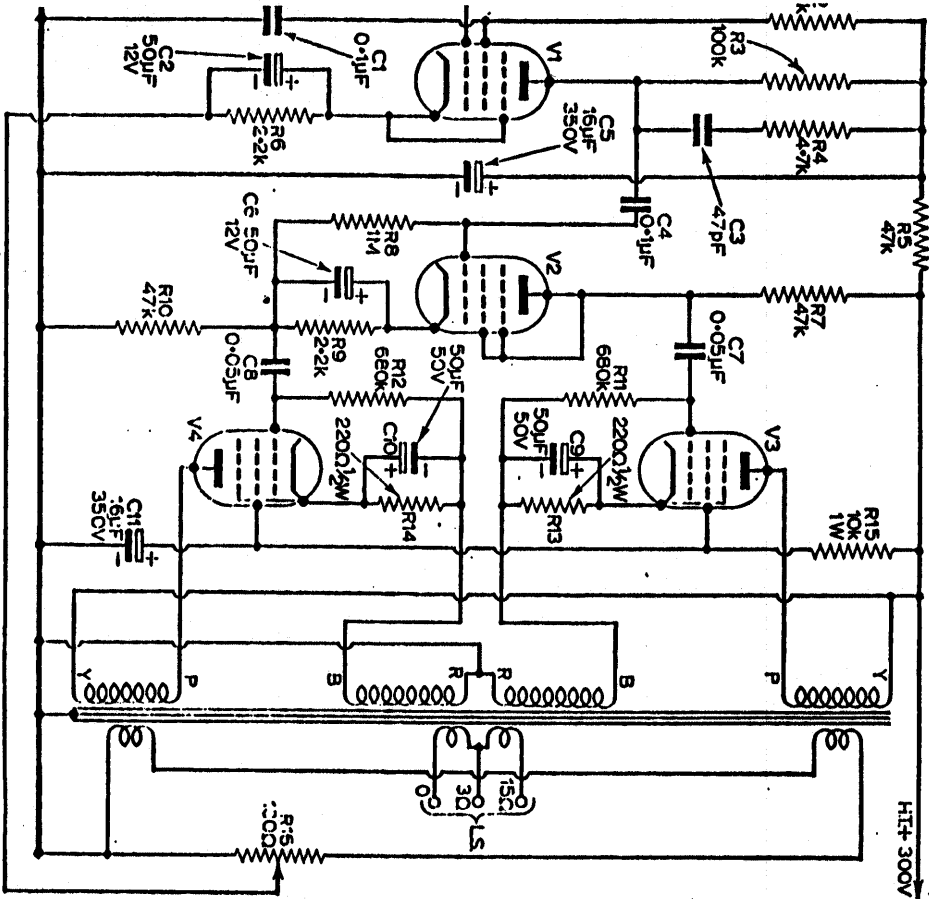


Fig. 9—A three-stage amplifier with another version of anode/cathode loading.

always passed through a pre-amplifier first, and a highly sensitive amplifier oplessly overloaded.

light pentode and concerning circuit Fig. 9 will give all the gain likely to be the grid resistors of the output valves to the cathode ends of the cathode resistors from end can be altered if it is wished e of the high-gain versions, without rations of the remainder. The use of y feedback is not likely to cause instability /2 can be used by the constructor in the experiment. V1 and V2 could ie., a double triode.

former, of which constructional details n in the next issue, has been used in f circuits, not all of which were con- rable when matters of cost and ease nt were taken into account. All, how- d to prove the inherent stability of the d-back system.

(To be continued)

## P.W. SIGNAL GENERATOR

(Continued from page 482)

so on, at 200kc/s intervals, until the generator harmonics are too weak to hear.

The fifth harmonic of 200kc/s will be 1,000kc/s, or 1Mc/s, and the generator may be tuned to this. Harmonics of the generator will then be heard at 2Mc/s, 3Mc/s, 4Mc/s and so on, at 1Mc/s intervals, until too weak to be found. It is, of course, necessary to have a receiver with short-wave ranges, for this purpose. By proceeding as described, calibration marks can be obtained at 1Mc/s intervals.

In many parts of the country the National Physical Laboratory signal on 2.5Mc/s can be received. This will furnish a 2.5Mc/s calibration of great accuracy. By proceeding as above, harmonics of this will furnish calibration marks at 5Mc/s, 7.5Mc/s, 10Mc/s and so on, at 2.5Mc/s intervals.

gadget must be made accurately, otherwise it will revolve with a wobble that will cause over-lying turns and snapped wires. Try cutting the 1/8" oversize and parting it to exact size after fitting the screw.

most the only simple aspect of transformer is the turns ratio, which is given by  $(Zp/Zs) = Zp$  and  $Zs$  are respectively the valve impedance and the nominal loudspeaker impedance. All others are so complex that no specification can be offered when the object is to enable the constructor to use available materials. Nor would it be helpful to present a formulae with an invitation to the constructor to sort it out himself. Because of these difficulties, and because the tertiary-wound transformer is tolerant to a reasonable range of variation, a procedure that seems rough and ready is one which will prove satisfactory. A general description of the method will be given first, followed by step-by-step winding instructions.

Refer to Fig. 12, which gives a cross-section of windings with the core on the left and the partition seen horizontally. The checks, which should be horizontal at top and bottom, have been placed to avoid confusing the leads in the turns. All sections are balanced equally each of the secondary winding (section 4), and for this section must be positioned accurately away through the depth of the winding space. For four layers (at the most) of 20 or 25 turns, e.g. enamelled wire plus paper interleaving Empire cloth insulation, the secondary will be either side of the true mid-point. Mark these boundaries on the outside of the turns near the slots, or on the inside if they are not slotted. The inner marks indicate the number of turns, e.g. 1, 2, 3, 4, 5, 6, 7, 8, 9, 10, 11, 12, 13, 14, 15, 16, 17, 18, 19, 20, 21, 22, 23, 24, 25. There, with all other layers, they must stop, regardless of the number of turns wound on because an equal space is needed for sections 5, 6 and 7. As all four secondary sections are equal, the number of turns in section 2 can be multiplied by 4, and the total divided by the required turns ratio to give the number of turns that must be wound on for secondary (section 4).

reference to standard wire tables will give some guidance as to the likely number of turns that can be accommodated. The distance between one check and the partition divided by the wire diameter gives the number of closed turns per layer. The section depth less 1/8" for insulation gives the actual winding space. Add 0.003in. to the wire diameter for covering paper and the layer thickness is then given. The total number of turns is then given by:

$$\text{Winding space} \times \text{turns-per-layer}$$

Layer thickness  
 from 3000 to 3500 turns is a fair total for a primary winding and the gauge can be chosen in the range 32 to 38s.w.g. to suit the available wire. If the original gauge of wire is used with the 1/8" component, it will be found that the

number of turns is less than the number removed. Use laminations of reasonably good quality and aim for a core section of about 1/4in. square for 5W and up to 1 1/2in. thickness for 10W. Make the bobbin to suit and mark the secondary boundaries on the checks. Wind section 1 (Fig. 12) straight on to the bobbin, 20 turns only, spaced to occupy the full width, passing the partition so that 10 turns lie each side of it. Gauge (25 to 30s.w.g.)

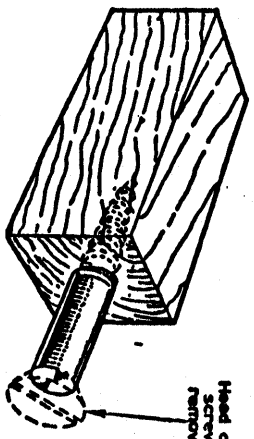


Fig. 11—A suitable bobbin holder for use with a geared brace for winding.

is not very important because the feedback network draws virtually zero current and only a few milliamperes of V1 cathode current passes through the windings.


**Insulation**

Fasten the wire ends to the checks with adhesive tape to prevent them becoming tangled as winding proceeds. This section will operate near to earth potential, but the next will have a wide A.C. swing; therefore, three layers of 0.005in. Empire cloth should be wound on for insulation. It also provides an even surface on which to commence the next winding.

The first primary layer for section 2 should be close-wound to fill the width between one check and the partition. Note the number of turns, add a layer of 0.003in. paper and continue to add similar paper-interleaved layers until it is obvious that the addition of three layers of Empire cloth will fill the allotted space up to the boundary mark. Calculate the total number of turns.

Section 3 is identical to section 2 but, as it serves the other valve of a push-pull pair, it must be wound in the reverse direction. Simply take the bobbin off its temporary wood core and put it on the other way round; then, rotation of the winder need not be reversed. This section, complete with insulation, should

Fig. 12 (right) — The arrangement of the sections.

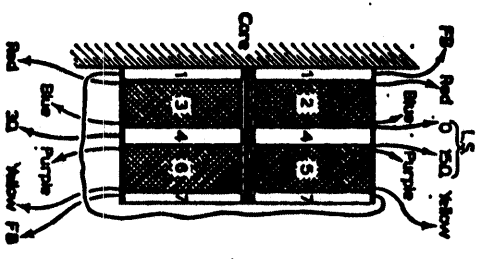

end up level with section 2 on the other side of the partition.

**Calculation**

Next is the secondary, section 4, and the number of turns has to be calculated. The number of turns in section 2, multiplied by 4, gives the total primary turns and this figure divided by the turns ratio, gives the number of secondary turns. For example, if section 2 has 750 turns and the ratio required is 30:1 the calculation is:

$$\frac{750 \times 4}{30} = 100$$

The secondary must be wound evenly right across the bobbin, passing the partition as it extends from check to check. If the last layer

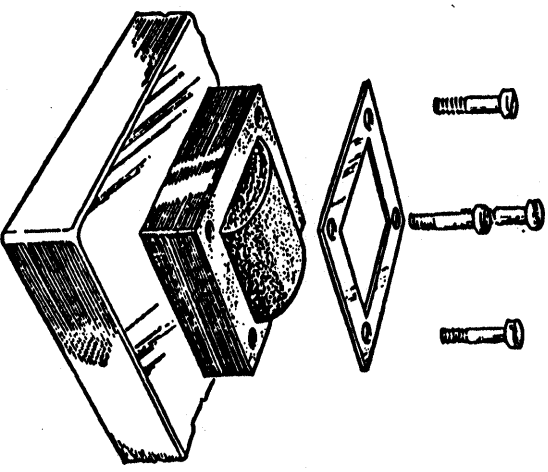


Fig. 13—A method of clamping the finished transformer to the amplifier chassis.

has insufficient turns to fill its full width the turns must be spaced evenly to distribute them equally each side of the partition. A 30 tap can be made at 50% of a 150 secondary provided it can be arranged near a check. This is impossible with a three-layer secondary and easy with a two-layer one when the wire gauge is chosen to fill the width exactly. In a four-layer winding, the second and fourth can be spaced evenly so that the tap can be at a check and the balance maintained.

When the secondary has been insulated with three layers of Empire cloth, the remaining winding space should equal that used for sections 1, 2 and 3. Wind section 5 exactly the same as section 2 and in the same direction. Section 6 must be wound in the same direction as section 3. These sections, with three-layer insulation, should leave just enough space for the outer tertiary winding which is identical with section 1 and wound in the same direction. Three more layers of Empire cloth complete the work of winding. The end of section 1 and the beginning of

primary wires should be anchored and coded immediately, those from each class a separate one-valve set. Sleeve them, in colours indicated in Fig. 12, and then sleeves firmly to the insulated window adhesive tape, or tape coloured leads to the tube and solder the wires to these. If the is delayed until after assembly of the laminations, tag-strips can be fitted to the transformer mounting.

**Assembly**

Insert the laminations with the E's at alternate directions, and butted together gaps. Firm clamping is essential to avoid chattering. Fig. 13 shows a transformer into a rectangular hole in the chassis and by a plate with a rectangular hole bolted the laminations.

In all circuits to which this versatile transformer can be applied, sections 2 and 5 together form the load for one valve of a push-pull straight anode loading they are put by joining the blue and purple leads. Yellow is then taken to the anode and red. Sections 3 and 6 are used in exactly the same way as the other valve. Ultra-linear is obtained by taking the screws to the junction of the blue and purple leads.