

## RS-232 Line Driver Power Supply

## AB-30

The current limit resistor, R4, is selected by dividing the current limit threshold voltage (approximately 100 mV) by the maximum peak current level in the output switch (750 mA steady-state). For our purposes  $R4 = 100 \text{ mV}/750 \text{ mA} = 0.13\Omega$ . A value of  $0.1\Omega$ , used here, will trip the current limit at 1A peak. A more conservative design would use  $0.15\Omega$  for this resistor.

Capacitor C1 sets the oscillator frequency according to the equation  $C1 = 80/f$ , where C1 is in nano-Farads and f is the frequency of the oscillator in kHz. This application runs at 80 kHz and used a 1 nF (1000 pF) silver-mica capacitor. The oscillator section provides a 10% deadtime each cycle to protect the output transistor.

Capacitor C2 serves as a compensation capacitor for operating the circuit in the synchronous conduction mode. That is, the output transistor will switch on each cycle, thereby eliminating the random noise spikes which occur with non-synchronous operation and are at best difficult to filter. This capacitor is optional and may be omitted if desired. If used, a value of 10 to 50 pF should be sufficient for most applications.

The choice for an output capacitor value depends primarily on the allowed output ripple voltage,  $\Delta V_{OUT}$ . In most cases, the capacitor's equivalent series resistance (ESR) at the switching frequency produces more ripple voltage than does the charging and discharging of the capacitor. The capacitor should be chosen to have an  $ESR \leq \Delta V_{OUT}/100$  mA, where 100 mA is approximately the greatest ripple current produced by the transformer secondary. Higher-value capacitors tend to have lower ESR; 1000  $\mu$ F aluminum electrolytic was used in this circuit to assure low ESR, under 0.4  $\Omega$ .

The input capacitors, C5 and C6, are used to reduce the transients that may be fed back to the main supply. Capacitor C5 is a 100  $\mu\text{F}$  electrolytic and is bypassed by C6, a 0.1  $\mu\text{F}$  ceramic disc.

For good efficiency, the diodes must have a low forward voltage drop and be fast switching. 1N5819 Schottky diodes work well

$$R3 = (|V_{OUT}| + 1V)/54.2 \mu A = 240 k\Omega$$

TL/H/8756-1

Transformer selection should be picked for an output transistor "on" time of  $0.4/f$ , and a primary inductance high enough to prevent the output transistor switch from ramping higher than the transistor's rating of 750 mA. Pulse Engineering (San Diego, Calif.) and Renco Electronics, Inc. (Deer Park, N.Y.) can provide further assistance in selecting the proper transformer for a specific application need. The transformer used in the power supply was a Pulse Engineering PE-64287 with turns ratio of  $N_p:N_s:N_s = 1:1.6:1.6$  and primary inductance of  $50 \mu\text{H}$ .

Table I is a parts listing for the components used in the building of the power supply circuit.

**TABLE I**  
**Parts List**

R1 =	10 k $\Omega$
R2 =	240 k $\Omega$
R3 =	240 k $\Omega$
R4 =	0.1 $\Omega$
C1 =	1000 pF
C2 =	18 pF
C3 =	220 $\mu\text{F}$
C4 =	220 $\mu\text{F}$
C5 =	100 $\mu\text{F}$
C6 =	0.1 $\mu\text{F}$
All diodes are 1N5819	
T1 =	Pulse Engineering PE-64287

Lit. # 114539

#### LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, and whose failure to perform, when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.
2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.



**National Semiconductor Corporation**  
1111 West Bardin Road  
Arlington, TX 76017  
Tel: 1(800) 272-9959  
Fax: 1(800) 737-7018

**National Semiconductor Europe**  
Fax: (+49) 0-180-530 85 86  
Email: cnjwge@tevm2.nsc.com  
Deutsch Tel: (+49) 0-180-530 85 85  
English Tel: (+49) 0-180-532 78 32  
Français Tel: (+49) 0-180-532 93 58  
Italiano Tel: (+49) 0-180-534 16 80

**National Semiconductor Hong Kong Ltd.**  
13th Floor, Straight Block,  
Ocean Centre, 5 Canton Rd.  
Tsimshatsui, Kowloon  
Hong Kong  
Tel: (852) 2737-1600  
Fax: (852) 2736-9960

**National Semiconductor Japan Ltd.**  
Tel: 81-043-299-2309  
Fax: 81-043-299-2408

National does not assume any responsibility for use of any circuitry described, no circuit patent licenses are implied and National reserves the right at any time without notice to change said circuitry and specifications.