

Typical DP8570A Interface to the IBM PC/XT for the Purpose of Engineering Evaluation

National Semiconductor
Application Brief 43
Milt Schwartz
March 1989



Typical DP8570A Interface to the IBM PC/XT for the Purpose of Engineering Evaluation AB-43

The following information has been provided to assist the reader in developing an evaluation setup for the DP8570A family of Real Time Clocks. This interface was prototyped and debugged for use in an IBM PC/XT or compatible bus computer with an accompanying program written in the C language.

Hardware Used

The interface consists of:

- DP8570A Timer Clock Peripheral
- 74ALS521 Address Decoder (I/O Hex 300 to 31F)
- 74ALS245 Transceiver (Data Bus Buffer)
- Lithium Battery (3.4V Nominal)
- Standard Pierce Parallel Resonant Crystal (32.768 kHz, ± 20 ppm)
- Various Capacitors ($\pm 10\%$)
- Various Resistors ($\frac{1}{8}W \pm 10\%$)

Refer to the complete schematic provided. (Figure 1)

As shown on the schematic, T1, G1, G0 MFO, INTR, and TCK are available for monitoring purposes.

Pins T1, MFO, INTR, and TCK have 3.9k pull-up resistors to V_{BB} . These resistors allow operation of T1, MFO, and INTR outputs during power down when in the battery backed mode. The resistor on TCK guarantees this input will not be floating.

Pins G0 and G1 have 10k pull-down resistors to ground. These resistors ensure that Timer 0 and Timer 1 are enabled by the hardware.

A resistor divider was placed at the $\overline{PF\!A\!I\!L}$ pin in place of an external power fail signal (as suggested in the data sheet). This facilitates bus lockout during a power fail/return. The user may wish to simulate standby mode by changing the voltage at the $\overline{PF\!A\!I\!L}$ pin. For example, this may be accomplished by connecting a resistor (fixed or variable) in parallel with the 3.4k resistor.

Separate power supplies for V_{CC} and V_{BB} may be used in place of the system 5V supply and battery for the purpose of monitoring the supply currents.

Software

A demo program, TCP, was written in C language and designed to run on MS-DOS or PC-DOS. The program TCP consists of several pop up menus with the initial display as the main menu. This menu lists the available functions which may be called. Each pop up menu prompts for an entry and provides on-screen documentation.

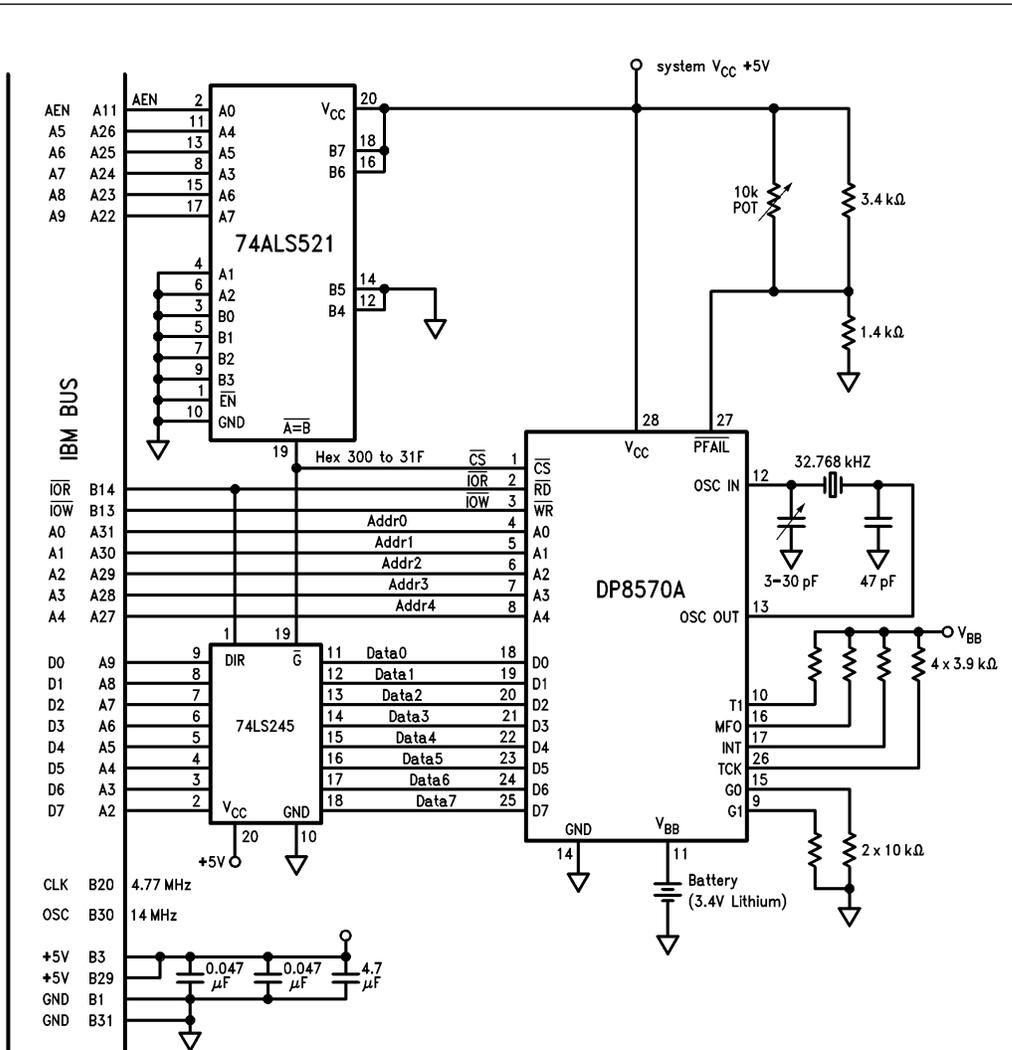


FIGURE 1. DP8570A Timer Clock Peripheral Interface to IBM/XT

TL/F/10402-1

LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, and whose failure to perform, when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.
2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.

 <p>National Semiconductor Corporation 1111 West Bardin Road Arlington, TX 76017 Tel: 1(800) 272-9959 Fax: 1(800) 737-7018</p>	<p>National Semiconductor Europe Fax: (+49) 0-180-530 85 86 Email: cnjwge@tevm2.nsc.com Deutsch Tel: (+49) 0-180-530 85 85 English Tel: (+49) 0-180-532 78 32 Français Tel: (+49) 0-180-532 93 58 Italiano Tel: (+49) 0-180-534 16 80</p>	<p>National Semiconductor Hong Kong Ltd. 19th Floor, Straight Block, Ocean Centre, 5 Canton Rd. Tsimshatsui, Kowloon Hong Kong Tel: (852) 2737-1600 Fax: (852) 2736-9960</p>	<p>National Semiconductor Japan Ltd. Tel: 81-043-299-2309 Fax: 81-043-299-2408</p>
--	--	---	---

National does not assume any responsibility for use of any circuitry described, no circuit patent licenses are implied and National reserves the right at any time without notice to change said circuitry and specifications.