Configuring DRAM to NS32GX320

1.0 ABSTRACT

This application note describes the possible configuration of DRAM with page lower than 8k byte at an NS32GX320 based system. Some examples with different bus widths are given at the appendix together with the implementation of a PAGE signal extended for pages from 0.5k to 8k.

2.0 INTRODUCTION

The NS32GX320 features the page signal optimizing the access to a DRAM memory. The page signal will be activated if the last transaction with PLAT active was to the same 8k bytes (A13:A31 are compared). Thus, row address latch can be avoided by the DRAM controller, giving a faster access to the DRAM. The PLAT signal has to be activated when accessing the DRAM. Then prefetch from PROM or accessing other devices will not affect the address comparison.

When using a DRAM configuration with page smaller than 8k byte an upgrade must be done to make sure the accesses are to the same page. More address bits must be compared.

In the sections that follow, we will describe some possible configurations of DRAM and for each one a circuit to upgrade the PAGE signal of the NS32GX320.

This application considers DRAMs with different page size, memory bus width and usage of standard SIMMs existing in the market.

3.0 DESCRIPTION

The common DRAMs used in standard designs are 256k x 4-bit, 1M x 1-bit, 1M x 4-bit, 4M x 1-bit, 4M x 4-bit and 16M x 1-bit. DRAM modules using the above mentioned elements can be used as well.

For each one, depending on the bus width used, we describe the DRAM configuration.

All the following configurations are valid for DRAM with fast page mode as well as for static column mode and nibble mode. The unique differences between these types is the behavior of the CAS signal in burst cycles.

3.1 256k x 4 DRAM

The 256k x 4 DRAM page size is 0.5k words. The address mux of a system with 8-bit bus selects A0:A8 as column address and A9:A17 as row address. If we want to optimize the DRAM access using the page feature of the NS32GX320 we must generate a signal indicating that the current access is to the same 0.5k byte page than the last DRAM access. Thus, additionally to the PAGE signal, we must compare the lines A9, A10, A11 and A12 of the access to the Isat access. The lines A13 until A31 are compared by the NS32GX320.

At 16-bit bus the column address is given by A1 until A9 and the row address is given by A10 until A18. In this case we need to generate page signal to the lines A10, A11 and A12. At 32-bit bus, the column address is given by A2:A10 and the row address by A11:A19. We need to build hardware for the lines A11 and A12

The hardware will be described in the section 4.0

PAL® is a registered trademark of and used under license from Advanced Micro Devices, Inc

© 1995 National Semiconductor Corporation TL/EE11063

National Semiconductor Application Note 719 Gerardo Nahum March 1991



3.2 DRAM 1M x 1, 1M x 4

The 1Mx1/x4 dram has a 1k word page. A system with 8-bit bus will need hardware implementing the page signal for the lines A10, A11 and A12. (The row address is given by A10 to A19.)

A system with 16-bit bus will need hardware implementing the page signal to A11 and A12. (The row address is A11 to A20.)

A system with 32-bit bus will need extra hardware because the row address is given by A12:A21, then page signal must be implemented to the signal A12 only. A13 to A31 are given by the NS32GX320 page mechanism.

3.3 DRAM 4M x 1, 4M x 4

The 4M words DRAM have a 2k words page. A system with 8-bit bus will have a column address given by A0:A10 and a row address given by A11:A21. Thus the page signal must be generated to the lines A11 and A12, additionally to the NS32GX320 page signal. A system with 16-bit bus will need a page signal for the line A12 only (the row address is given by A12:A22).

A system with 32-bit bus won't need any upgrade to the NS32GX320 page mechanism.

3.4 DRAM 16M x 1

The 16M bit DRAM have a page of 4k words. Only an 8-bit bus system will need an upgrade to the PAGE signal being the row address A12:A23. Thus only the line A12 must be included in the extra page mechanism.

Systems with 16-bit or 32-bit bus won't need any upgrade, the NS32GX320 PAGE signal must be used alone at the DRAM controller.

4.0 IMPLEMENTATION

The following section describes the circuit needed to upgrade the page mechanism of the NS32GX320. The implementation is a superset of the above described cases. A new signal is generated complementing the PAGE signal of the NS32GX320. This signal (called SPAGE in this application note) is active low and will be asserted when the current access is to the same $\frac{1}{16}$ page of the last access with PLAT active (each page 8k bytes).

The size of the new page depends on which addresses are connected. The following table summarizes the options. The unconnected pins must be pulled up.

Page size	Address signals to be connected
0.5k	A9, A10, A11, A12
1k	A10, A11, A12,
2k	A11, A12
4k	A12
8k and up	None

The hardware consists in a PAL® 16R4, the grade depends on the system frequency (see Table II), that samples at the rising edge of BCLK the addresses A12, A11, A10 and A9 if PLAT is active and CONF,RDY and BMT indicates end of last T2.



RRD-B30M75/Printed in U. S. A

Configuring DRAM to NS32GX320

The NS32GX320's PLAT must be sampled by a 74F74 using \overline{BCLK} to extend it until the end of last T2, if the system supply PLAT valid until the end of last T2, this sampling level can be avoided and PLAT can be used as input direct-ly.

The SPAGE signal is generated by comparing the sampled address lines to the current ones. If they are equal and the NS32GX320's PAGE is active the SPAGE is asserted (low).

The comparison and the mask are done at the PAL. The PAL generates two SPAGE signals (SPAGEL corresponding to A9 and A10 and SPAGEH corresponding to A11 and A12). They are both active low and not masked by PAGE. The PAL generates a third line, SPAGE, that is active if all the SPAGEh, SPAGEL and PAGE signal are active.

The user can use SPAGE signal alone or if timing is more critical than number of input pins, the above mentioned 3 signals can be used and the AND function can be implemented directly at the DRAM controller.

Commonly the DRAM controller will sample the SPAGE signal, if the timing is critical (e.g., the DRAM controller is implemented in to an ASIC), then the two AND functions can be implemented at the sampling level. This will eliminate the second asynchronous pass at the PAL. (See Timing considerations section.)

4.1 Timing Considerations

The signal SPAGE is generated asynchronously from the Address bits.

TSPAGEv = max (TAv + 2 * Tpal delay, TPAGEv + Tpal delay)

 $\mathsf{TSPAGEv}=\mathsf{max}\ (9+2*10,\,18+10)=\mathsf{max}\ (29,\,28)=29$ ns using a PAL grade D

if the AND function is implemented at the DRAM controller TSPAGEv = max (TAv + Tpal delay TPAGEv)

TSPAGEv = max (9 + 10, 18) = 19 ns

5.0 TABLES

TABLE I. Page Upgrade							
Memory	PAGE Size	Bus Width	Address Signals				
	512	8-Bit	A9, A10, A11, A12				
256k x 4		16-Bit	A10, A11, A12				
		32-Bit	A11, A12				
1M x 1	1024	8-Bit	A10, A11, A12				
		16-Bit	A11, A12				
		32-Bit	A12				
4M x 1	2048	8-Bit	A11, A12				
		16-Bit	A12				
		32-Bit	None				
16M x 1		8-Bit	A12				
	4096	16-Bit	None				
		32-Bit	None				

5.1 SPAGE Timing

TABLE II. SPAGE Setup Time

Mask Function at the PAL outside DRAM Controller						
Number of Input Pins	PAL GRADE	25 MHz	20 MHz			
1	GRADE C	7 ns	17 ns			
1	GRADE D	11 ns	21 ns			
Mask Function at DRAM Controller						
Number of Input Pins	PAL GRADE	25 MHz	20 MHz			
3	GRADE C	19 ns	29 ns			

```
6.0 PAL EQUATIONS
module lpage
flag '-r3', '-t2', '-s','-q2'
title 'Low Page signal generator
                                               22-Apr-90'
" This pal generates the SPAGE signal used together with the \ensuremath{\texttt{NS32GX320}}\xspace PAGE
" signal to identify in-page access to DRAM with less than 4{\bf k} word page
   LPAGE device 'P16R4';
CLK pin l; "r.e. of BCLK
OE pin ll; "Always GND
"Inputs
A9
          pin 2; " NS32GX320 address signals
          pin 3; " The not needed address lines must be left constant
A10
          pin 4; " high (pulled up)
A11
A12
          pin 5;
CONF
          pin 6; " Control signals to identify last T2
RDY
          pin 7;
BMT
          pin 8;
PLAT
          pin 9; " Plat if continued until last T2 or sampled Plat.
         pin 12; " Page signal from NS32GX320
PAGE
" Outputs
SPAGEL
        pin 19; " Low Page signal to DRAM controller
          pin 18; " High page signal to DRAM controller
SPAGEH
         pin 13; " New PAGE signal
SPAGE
" Internal registers
         pin 14; " Sampled address of last DRAM access
LA9
LA10
          pin 15;
LAll
          pin 16;
LA12
         pin 17;
" Definitions
   x,c,z = .X.,.C.,.Z.;
    LA = [LA12, LA11, LA10, LA9];
    A = [A12, A11, A10, A9];
Equations
" Sample address at last T2 with PLAT active
!LA := !A & !PLAT & !CONF & !RDY & BMT " if LAST T2 with PLAT sample new A
      # !LA & !( !PLAT & !CONF & !RDY & BMT); " else hold sampled address
" SPAGEx : assert when LA==A
!SPAGEL = (LA9==A9) & (LA10==A10);
!SPAGEH = (LA11==A11) & (LA12==A12);
" SPAGE active if both SPAGEH and SPAGEL active and PAGE active
!SPAGE = !SPAGEL & !SPAGEH & !PAGE;
" Note: The SPAGEx signal is split because of the number of minterms of
        this pal. In an ASIC design they can be unified in one single
        equation.
END lpage
```



























LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

- Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, and whose failure to perform, when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.
- A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.



National does not assume any responsibility for use of any circuitry described, no circuit patent licenses are implied and National reserves the right at any time without notice to change said circuitry and specifications.