# Using National's NMC87C257 256K EPROM with On-Chip Latches

National Semiconductor Application Note 731 Sean Pitonak April 1992



## INTRODUCTION

The standard EPROM available from most manufacturers limits the on-chip circuitry to just the minimum needed to operate the EPROM and the minimum of user interface handles. Users of standard EPROMs are forced to include latches in their design to interface with most microcontrollers and microprocessors.

Probably one of the most desirable user-interface features is the ability to directly interface the EPROM to a host device that has a multiplexed address and data port. This type of interface is present on many microcontrollers and microprocessors such as the HPC, 80C51 and many of the Intel and Motorola microcontrollers. National is now manufacturing an EPROM that can directly interface with a host device—the NMC87C257.

### NATIONAL'S NMC87C257 SOLUTION

The NMC87C257 is pin-compatible with the standard 27C256 (1 Megabit EPROM, organized as 128K x 8 bits), shown in *Figure 1*. In fact, the NMC87C257 can be directly substituted into the many existing 27C256 sockets when used in the unlatched mode. The internal latches are trans-

parent and the Address Latch Enable (ALE) is on a shared pin with Vpp. By tying Vpp to V<sub>CC</sub>, the NMC87C257 behaves exactly like the 27C256. The NMC87C257 is available in both quartz-windowed Ceramic DIP and Plastic LCC packages as is the 27C256.

National's latched EPROM is useful because the same ALE used for the 74F373 latch can be tied to the ALE of the NMC87C257, eliminating the need for the 74F373 latch. As shown in *Figure 2*, it is as simple as removing the two octal latches and routing the appropriate bus and control line to the EPROM.

# SUMMARY

The NMC87C257 allows the user the combination of familiar functionality, pinout and programmability (due to its compatibility with existing 27C256 EPROMs) and the advantages of saved board space, cost of the octal latches and their insertion and system power consumption. The NMC87C257 gives the system designer the needed flexibility of interfacing directly with microcontrollers and microprocessors that have multiplexed address and data ports.





# Using National's NMC87C257 256K EPROM with On-Chip Latches

AN-73

©1995 National Semiconductor Corporation TL/D/11089

RRD-B30M75/Printed in U. S. A

AN-731



National does not assume any responsibility for use of any circuitry described, no circuit patent licenses are implied and National reserves the right at any time without notice to change said circuitry and specifications.