

# 20 Watt Simple Switcher Forward Converter

National Semiconductor  
Application Note 776  
Frank DeStasi  
Tom Gross  
June 1991



20 Watt Simple Switcher Forward Converter

A 20W, 5V at 4A, step-down regulator can be developed using the LM2577 Simple Switcher IC in a forward converter topology. This design allows the LM2577 IC to be used in step-down voltage applications at output power levels greater than the 1 A LM2575 and 3 A LM2576 buck regulators. In addition, the forward converter can easily provide galvanic isolation between input and output.

The design specifications are:  $V_i$  Range : 20V–24V  
 $V_o$  : 5V  
 $I_o(max)$  : 4A  
 $\Delta V_o$  : 20 mV

With the input and output conditions identified, the design procedure begins with the transformer design, followed by the output filter and snubber circuit design.

## TRANSFORMER DESIGN

1. Using the maximum switch voltage, input voltage, and snubber voltage, the transformer's primary-to-clamp windings turns ratio is calculated:

$$V_{SW} \geq V_{i_{max}} + V_{i_{max}} (N_p/N_c) + V_{snubber}$$

$$N_p/N_c \leq (V_{SW} - V_{i_{max}} - V_{snubber})/V_{i_{max}}$$

$$N_p/N_c \leq (60V - 24V - 5V)/24V = 1.29$$

$$\Delta \text{ let } N_p/N_c = 1.25$$

The  $V_{snubber}$  voltage is an estimate of the voltage spike caused by the transformer's primary leakage inductance.

2. The duty cycle,  $t_{on}/T$ , of the switch is determined by the volt-second balance of the primary winding.

During  $t_{on}$ :

$$V_i = L_p (\Delta i / t_{on}) \rightarrow \Delta i = (V_i / L_p) t_{on}$$

During  $t_{off}$ :

$$V_i = (N_p/N_c) L_p (\Delta i / t_{off}) \rightarrow \Delta i = (N_p/N_c) (V_i / L_p) t_{off}$$

Setting  $\Delta i$ 's equal;

$$(V_i / L_p) t_{on} = (N_p/N_c) (V_i / L_p) t_{off}$$

$$t_{on}/t_{off} = N_p/N_c$$

$$\text{Since } D = t_{on}/T = t_{on}/(t_{on} + t_{off})$$

$$\text{max. duty cycle} = D_{max} = (N_p/N_c) / [(N_p/N_c) + 1]$$

$$D_{max} = (1.25) / (1.25 + 1) = 0.56 (56\%)$$

3. The output voltage equations of a forward converter provides the transformer's secondary-to-primary turns ratio:

$$V_o + V_{diode} \leq V_{i_{min}} \times D_{max} (N_s/N_p)$$

$$N_s/N_p \geq (V_o + V_{diode}) / (V_{i_{min}} \times D_{max})$$


$$N_s/N_p \geq (5.5V) / (20V)(56\%) = 0.49$$

$$\Delta \text{ let } N_s/N_p = 0.5$$

4. Calculate transformer's primary inductance by finding the maximum magnetizing current ( $\Delta i_{LP}$ ) that does not allow the maximum switch current to exceed its 3 A limit (capital I for DC current,  $\Delta i$  for AC current, and lower case i for total current):

$$i_{sw} = i_{pri} = i_{LO} + \Delta i_{LP}$$

Basic Forward Converter

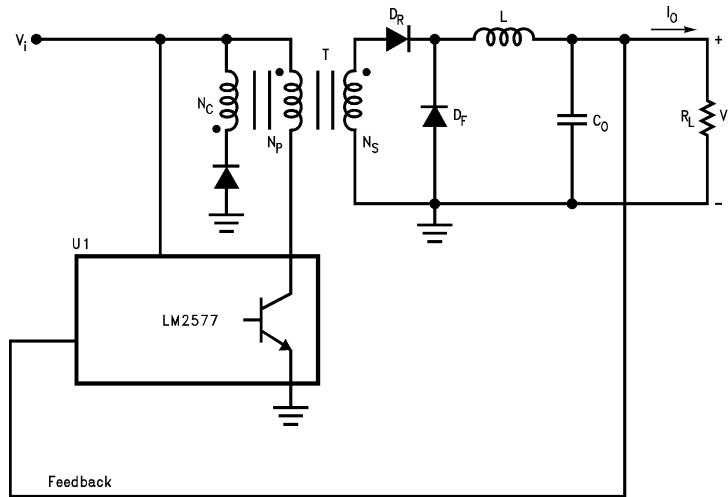

TL/H/11216-1

where  $i_{Lo}$  is the reflected secondary current and  $\Delta i_{LP}$  is the primary inductance current.

$$i_{Lo'} = i_{Lo}(N_s/N_p) \quad (i_{Lo} \text{ reflected to primary})$$

$$i_{Lo} = I_{Lo} \pm \Delta i_{Lo}/2$$

$\Delta i_{Lo}$  is the output inductor's ripple current

$$I_{Lo} = I_o \text{ (the load current)}$$


$$i_{Lo'} = (I_o \pm \Delta i_{Lo}/2)(N_s/N_p)$$

$$i_{Lo'}(pk) = (I_o(max) + \Delta i_{Lo}/2)(N_s/N_p)$$


$$i_{sw} = I_{sw} + \Delta i_{sw}$$

$$i_{sw}(pk) = i_{Lo'}(pk) + \Delta i_{LP}(pk)$$
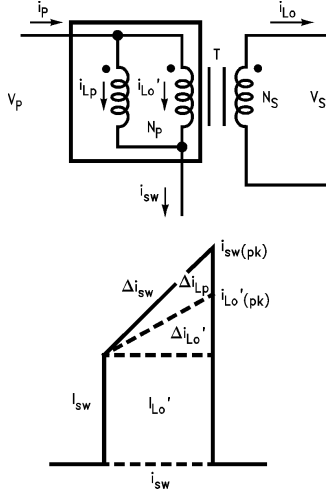
$$i_{sw}(pk) = (I_o(max) + \Delta i_{Lo}/2)(N_s/N_p) + \Delta i_{LP}(pk)$$



TL/H/11216-2

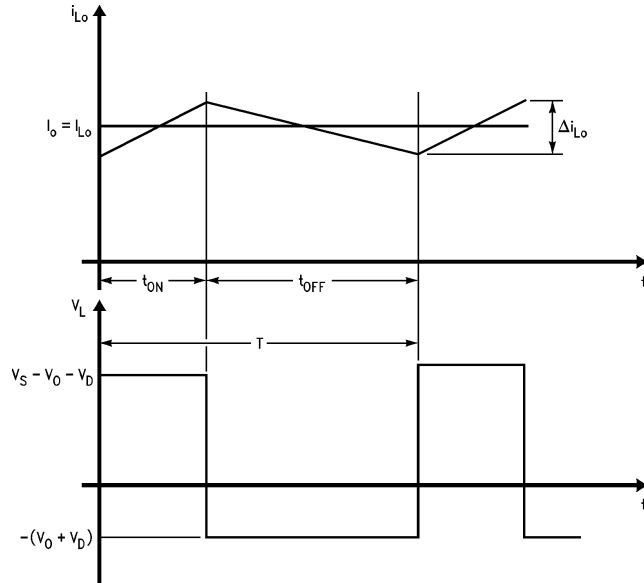

TL/H/11216-3

Using standard inductors, a good practical value to set the output inductor current ( $\Delta i_{Lo}$ ) to is 30% of the maximum load current ( $I_o$ ). Thus;

$$i_{sw}(pk) = (I_o(max) + 0.15\Delta i_{Lo})(N_s/N_p) + \Delta i_{LP}(pk)$$

$$\Delta i_{LP}(pk) = i_{sw}(pk) - (I_o(max) + 0.15\Delta i_{Lo})(N_s/N_p)$$

$$\Delta i_{LP}(pk) = 3A - (4A + 0.15 \times 4A)(0.5) = 0.7A$$

$$L_p = V_{pri} \times \Delta t / \Delta i = (V_i - V_{sat})(t_{on} / \Delta i_{LP}(pk))$$

$$= (V_{i(max)} - V_{sat})(D_{max} / (\Delta i_{LP}(pk) \times f))$$

$$= (24V - 0.8V)(0.56 / 0.7 \times 52 \text{ kHz})$$

$$L_p = 357 \mu H \quad \Delta i_{LP} = 350 \mu H$$

#### OUTPUT FILTER—INDUCTOR

The first component calculated in the design is the output inductor, using the current-to-voltage relationship of an inductor:

$$V_L = L_o (\Delta i_{Lo} / t_{on})$$

Choosing an inductor ripple current value of  $0.3I_o$  and a maximum output current of 4A:

$$\Delta i_{Lo} = 0.3 (4A) = 1.2A$$

During  $t_{on}$ :

$$V_L = V_S - V_D - V_o \text{ [where } V_S = (V_i - V_{sat})(N_s/N_p)]$$

Thus,

$$[(V_i - V_{sat})(N_s/N_p) - V_d - V_o] = L_o (\Delta i_{Lo} / D) f$$

$$L_o = [(V_i - V_{sat})(N_s/N_p) - V_d - V_o] \times D / \Delta i_{Lo} \times f$$

$$L_o = [(24V - 0.8V)(0.5) - 0.5V - 5V] 56\% / 1.2A \times 52 \text{ kHz}$$

$$L_o = 55 \mu H \quad \Delta i_{LP} = 60 \mu H$$

### OUTPUT FILTER—CAPACITOR

Since the output capacitor's current is equal to inductor's ripple current, the output capacitor's value can be found using the inductor's ripple current. Starting with the current-voltage relationship, the output capacitance is calculated:

$$\begin{aligned}\Delta V_o &= 1/C_o \int i \, dt \\ &= \Delta i_{L_o} / 4C_o (TR/2) \\ &= (\Delta i_{L_o} \cdot T) / 8C_o \\ C_o &= (\Delta i_{L_o} \cdot T) / 8\Delta V_o\end{aligned}$$

However, the equivalent series resistance (ESR) of the capacitor multiplied by the inductor's ripple current creates a parasitic output ripple voltage equal to:

$$\Delta V_o = ESR_{co} \cdot \Delta i_{L_o} = ESR_{co} \cdot 0.3 I_o$$

This parasitic voltage is usually much larger than the inherent ripple voltage. Hence, the output capacitor parameter of interest, when calculating the output ripple voltage, is the equivalent series resistance (the capacitance of the output capacitor will be determined by the frequency response analysis). Using a standard-grade capacitor with ESR of 0.05Ω produces a total output ripple voltage of:

$$\Delta V_o = 0.05\Omega \cdot 1.2A \approx 60 \text{ mV}$$

To get output ripple voltage of 20 mV or less (as was part of the design specs) requires a capacitor with ESR of less than 17 mΩ.

### SNUBBER CIRCUIT

A snubber circuit ( $C_S$ ,  $R_S$ ,  $D_S$ ) is added to reduce the voltage spike at the switch, which is caused by the transformer's leakage inductance. It is designed as follows: when the switch is off,

$$\begin{aligned}V_R &= V_{CE} - V_{IN} - V_D \\ V_{LL} &= V_D + V_R - V_{IN}(N_p/N_c)\end{aligned}$$

Substituting for  $V_R$ , the voltage across the leakage inductance,  $V_{LL}$ , is,

$$V_{LL} = V_{CE} - V_{IN}(1 + N_p/N_c)$$

Using the current-voltage relationship of inductors,

$$t_S = I_{PRI}(L_L/V_{LL})$$

Substituting for  $V_{LL}$ ,

$$t_S = I_{PRI} L_L / (V_{CE} - V_{IN}(1 + N_p/N_c))$$

Calculating for the average leakage inductance current,  $I_{LL(AVE)}$ ,

$$\begin{aligned}I_{LL(AVE)} &= I_{PRI(MAX)} (t_S) / 2T \\ &= I_{PRI(MAX)}^2 L_L f / 2(V_{CE} - V_{IN}(1 + N_p/N_c))\end{aligned}$$

Solving for the snubber resistor;

$$R_S = V_R / I_{LL(AVE)}$$

Substituting  $I_{LL(AVE)}$  and  $V_R$  results in,

$$\begin{aligned}R_S &= 2(V_{CE} - V_{IN}(1 + N_p/N_c)) \times \\ &\quad (V_{CE} - V_{IN} - V_D) / (L_L (I_{PRI(MAX)})^2 f)\end{aligned}$$

Choosing  $L_L$  to equal 10% of  $L_p$ ,

$$\begin{aligned}R_S &= 2(65V - 24V - 1V) \times (65V - 24V(2.25)) / \\ &\quad (7 \mu H (3A)^2 52 \text{ kHz}) \\ &= 268.9\Omega \approx 270\Omega\end{aligned}$$

Using the current-voltage relationship of capacitors,

$$\Delta V_R = (T - t_S) I_C / C_S = (T - t_S) V_R / R_S C_S \approx V_R / R_S C_S f$$

The capacitor  $C_S$  equates to,

$$C_S = V_R / R_S f \Delta V_R$$

$$C_S = 40V / (270\Omega)(52 \text{ kHz}) 10V = 0.28 \mu F \approx 0.33 \mu F$$

The snubber diode has a current rating of 1A peak and a reverse voltage rating of 30V.


### OTHER COMPONENTS

Diodes,  $D_R$  and  $D_F$ , used in the secondary are 5A, 30V Schottky diodes. The same diode type is used for  $D_C$ , however a lower current diode could have been used.


A compensation network of  $R_C$  and  $C_C$  optimizes the regulator's stability and transient response and provides a soft-start function for a well-controlled power-up.

The finished circuit is shown below.

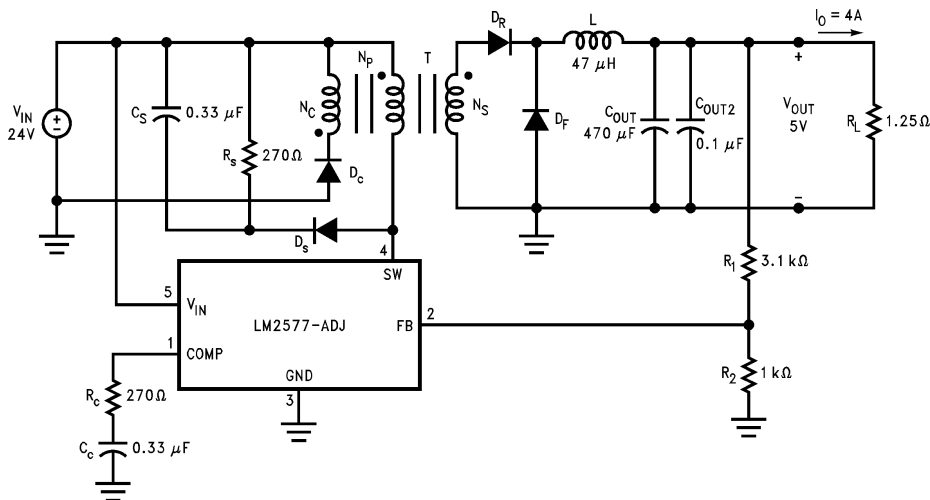5V, 4 A Forward Converter Circuit Schematic




TL/H/11216-4

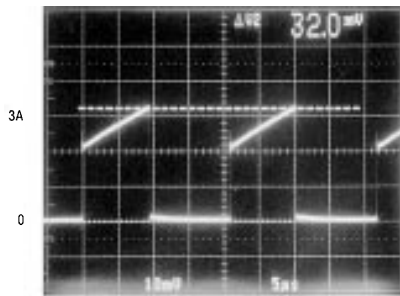

TL/H/11216-5

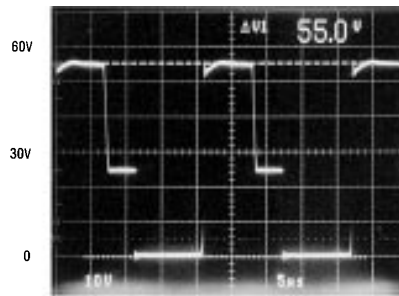**Switch Current**


Vertical: 1 A/div  
Horizontal: 5  $\mu$ s/div



TL/H/11216-6

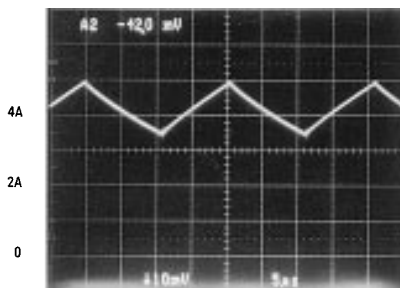**Switch Voltage**


Vertical: 10 V/div  
Horizontal: 5  $\mu$ s/div



TL/H/11216-7

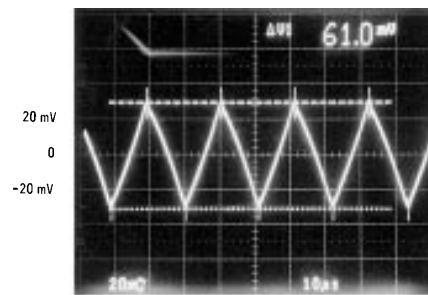**Inductor Current**


Vertical: 1 A/div  
Horizontal: 5  $\mu$ s/div



TL/H/11216-8

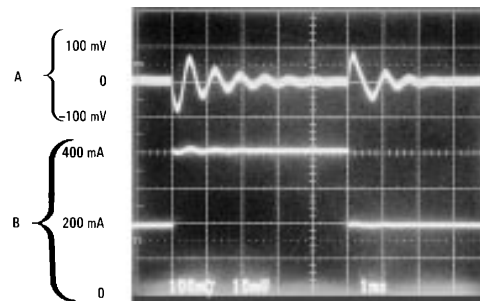**Output Ripple Voltage**

Vertical: 20 mV/div  
Horizontal: 10  $\mu$ s/div



TL/H/11216-9

**Load Step Response**

A: Output Voltage Change, 100 mV/div  
B: Output Current, 200 mA/div  
Horizontal: 10 ms/div



**LIFE SUPPORT POLICY**

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, and whose failure to perform, when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.
2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.



**National Semiconductor Corporation**  
2900 Semiconductor Drive  
P.O. Box 58090  
Santa Clara, CA 95052-8090  
Tel: 1(800) 272-9959  
TWX: (910) 339-9240

**National Semiconductor GmbH**  
Livny-Gargan-Str. 10  
D-82256 Fürstenfeldbruck  
Germany  
Tel: (81-41) 35-0  
Telex: 527849  
Fax: (81-41) 35-1

**National Semiconductor Japan Ltd.**  
Sumitomo Chemical  
Engineering Center  
Bldg. 7F  
1-7-1, Nakase, Mihama-Ku  
Chiba-City,  
Chiba Prefecture 261  
Tel: (043) 299-2300  
Fax: (043) 299-2500

**National Semiconductor Hong Kong Ltd.**  
13th Floor, Straight Block,  
Ocean Centre, 5 Canton Rd.  
Tsimshatsui, Kowloon  
Hong Kong  
Tel: (852) 2737-1600  
Fax: (852) 2736-9960

**National Semicondutores Do Brazil Ltda.**  
Rue Deputado Lacorda Franco  
120-3A  
Sao Paulo-SP  
Brazil 05418-000  
Tel: (55-11) 212-5066  
Telex: 391-1131931 NSBR BR  
Fax: (55-11) 212-1181

**National Semiconductor (Australia) Pty, Ltd.**  
Building 16  
Business Park Drive  
Monash Business Park  
Nottingham, Melbourne  
Victoria 3168 Australia  
Tel: (3) 558-9999  
Fax: (3) 558-9998

National does not assume any responsibility for use of any circuitry described, no circuit patent licenses are implied and National reserves the right at any time without notice to change said circuitry and specifications.