

# Calculating Power Dissipation for Differential Line Drivers

National Semiconductor  
Application Note 805  
Joe Vo  
February 1992



## INTRODUCTION

In many board and system level designs, it is often necessary to determine the total power dissipated by the individual components of that application. This determination of total device power dissipation is important for two reasons. First, it can be used to select the power supply best suited to satisfy the needs of the application. And second, a power dissipation calculation facilitates the analysis of how the board or system's operating conditions might adversely affect the reliability of, or otherwise damage, the on board components.

The purpose of this application note is to provide end users with a sample power dissipation calculation for typical TIA/EIA-422 and TIA/EIA-485 differential line drivers. Other topics which will be addressed by this application note include worst case power dissipation, and packaging/thermal considerations.

## CONTRIBUTIONS TO TOTAL DEVICE POWER DISSIPATION

Under normal operating conditions, the total device power dissipation is determined primarily by output load current and quiescent current. These current terms are modified by external loading conditions, device switching frequency, power supply voltage and ambient operating temperature. The following discussion of device power dissipation will take all these factors into consideration.

The power dissipated by a device in its quiescent state and that dissipated by the outputs when the device is switching constitute the primary contributions to total device power dissipation. Quiescent power dissipation is defined as the product of power supply voltage ( $V_{CC}$ ) and power supply current ( $I_{CC}$ ).

$$(1) \quad PD_{QUIESCENT} = (V_{CC}) (I_{CC})$$

The power dissipation by the outputs, takes into account the power dissipated by the output structures of the device when the outputs are driving a load. When the device output is in the LOW state, the output sinks a sufficient amount of load current to develop a  $V_{OL}$  with respect to ground. Conversely, when the device output is in the HIGH

state, the output sources a load current sufficient to develop a  $V_{OH}$  with a respect to ground. The power dissipated, then, by a single channel is:

$$(2) \quad PD_{OUTPUT} = I_{OH}(V_{CC} - V_{OH}) + I_{OL}(V_{OL})$$

where,  $I_{OH}$  = HIGH level output current  
 $I_{OL}$  = LOW level output current

The general expression to describe the dissipated power for all outputs is:

$$(3) \quad PD_{OUTPUTS} = (\# \text{ of channels}) [I_{OH}(V_{CC} - V_{OH}) + I_{OL}(V_{OL})]$$

Together, the sum of quiescent power dissipation and power dissipation at the device outputs approximates the total power dissipated by the device.

$$(4) \quad PD_{TOTAL} = PD_{QUIESCENT} + PD_{OUTPUTS}$$

A more comprehensive total device power dissipation calculation, however, might also incorporate the contribution to device power dissipation from the device's switching frequency. Therefore, Equation (4) could be changed to look like the following.

$$(5) \quad PD_{TOTAL} = PD_{QUIESCENT} + PD_{OUTPUTS} + C_{OUT}(V_{CC})^2(f)$$

where,  $C_{OUT}$  = device output capacitive load  
 $f$  = device switching frequency

For this application note, the last term of Equation (5) was intentionally omitted. These are several reasons for this omission. First, switching frequency does not lend itself well to this general discussion of power dissipation since it varies from application to application. Second, in terms of the quiescent and output power dissipation components, the magnitude of the  $CV^2f$  term on total device power dissipation is negligibly small for most line drivers. And third, Figure 1 demonstrates that switching frequency will not heavily impact quiescent device power dissipation (see Equation 1) since the magnitude of the change in  $I_{CC}$  due to switching frequency is small.

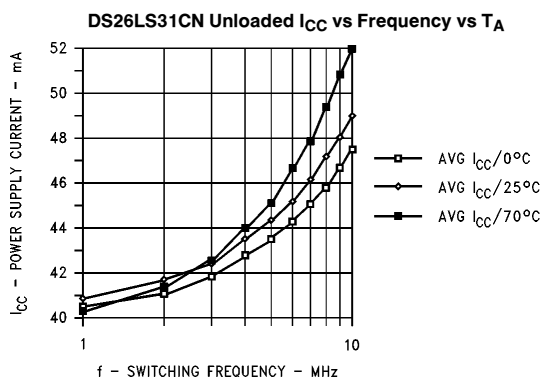


FIGURE 1. Supply Current vs Switching Frequency vs Temperature

# **TYPICAL POWER DISSIPATION CALCULATIONS USING THE DS26LS31CN**

To better illustrate a total power dissipation calculation in a typical TIA/EIA-422 application, consider the DS26LS31CN (molded DIP package) Quad Differential Line Driver operating under following conditions:

$V_{CC} = 5.0V$   
 Ambient Operating Temperature =  $25^{\circ}C$   
 Switching Frequency = 1 MHz  
 Duty Cycle = 50%  
 Measured  $V_{OH} = 3.2V$   
 Measured  $V_{OL} = 0.3V$   
 Termination Resistor = 100 $\Omega$


Figure 2 indicates that the  $I_{CC}$  typically associated with a  $V_{CC}$  of 5.0V, at room temperature, is approximately 39 mA. Figure 1 indicated that a device, operating at room temperature, switching at 1 MHz will generate an  $I_{CC}$  of approximately 41 mA. Note in both Figures 1 and 2 that the change in  $I_{CC}$  with respect to switching frequency and the change in  $I_{CC}$  with respect to  $V_{CC}$ , respectively, is rather small. Also note that in both figures there is little  $I_{CC}$  dependence on temperature.

For this typical calculation, 41 mA will be used for  $I_{CC\text{typical}}$  since it is a better representation of actual device operating conditions.

From (1), the static power dissipation is:


$$\begin{aligned} P_{D\text{QUIESCENT}} &= (V_{CC\text{typical}})(I_{CC\text{typical}}) \\ &= (5.0V)(41.0\text{ mA}) \\ &= 205.0\text{ mW} \end{aligned}$$

 Given that the measured  $V_{OH}$  is 3.2V, one can extract the corresponding  $I_{OH}$  from Figure 3. The  $I_{OH}$  required to develop a  $V_{OH}$  of 3.2V is approximately 30 mA.



TL/F/11335-2

**FIGURE 2. Supply Current vs Supply Voltage vs Temperature**

 

TL/F/11335-3

**FIGURE 3. High Output Voltage vs High Output Current vs Temperature**

From Figure 4, one can likewise obtain an  $I_{OL}$  of approximately 30 mA given a measured  $V_{OL}$  of 0.3V.

The outputs, then, of the DS26LS31CN dissipate power according to the following relationship:

$$\begin{aligned} PD_{OUTPUTS} &= (\# \text{ of Channels}) [I_{OH} (V_{CC} - V_{OH}) + I_{OL} (V_{OL})] \\ &= (4) [30 \text{ mA} (5.0\text{V} - 3.2\text{V}) + 30 \text{ mA} (0.3\text{V})] \\ &= (4) [54.0 \text{ mW} + 0.9 \text{ mW}] \\ &= 252.0 \text{ mW} \end{aligned}$$

From the given typical operating conditions, the total power dissipated by the DS26LS31CN is:

$$\begin{aligned} PD_{TOTAL} &= PD_{QUIESCENT} + PD_{OUTPUTS} \\ &= 205.0 \text{ mW} + 252.0 \text{ mW} \\ &= 457.0 \text{ mW} \end{aligned}$$

#### WORST CASE POWER DISSIPATION CALCULATIONS

While a typical power dissipation calculation is informative, a board or system level designer will invariably be forced to also perform a worst case calculation. With the exception of several minor changes, the same procedure is followed for both typical and worst case power dissipation calculations.

Starting with static power dissipation, this calculation must now use the maximum values for both power supply voltage ( $V_{CCmax}$ ) and power supply current ( $I_{CCmax}$ ). The  $I_{CCmax}$  used is normally that specified by the data sheet. However, if the application were to force the device beyond its 10 MHz operating window, the  $I_{CCmax}$  could exceed the data sheet specifications of 60 mA (see Figure 1). In either case, the larger current value must be used for  $I_{CCmax}$  in the worst case quiescent power calculation.

The next step is to calculate the power dissipation from the device outputs. To do so, place the device under the worst case board or system conditions, and measure the resulting  $V_{OH}$  and  $V_{OL}$  levels. Given these worst case  $V_{OH}$  and  $V_{OL}$  values, one can extract the corresponding worst case  $I_{OH}$  and  $I_{OL}$  values with the help of Figures 3 and 4, respectively. A substitution of these values into Equation (3) will then yield the worst case power dissipation due to the device outputs.

An alternative method to calculate the power dissipated by the device outputs requires that a differential output voltage versus output current ( $V_{OD}$  vs  $I_O$ ) curve be generated. Keeping in mind that  $V_{OD} \equiv V_{OH} - V_{OL}$ , a  $V_{OD}$  vs  $I_O$  curve can be developed by "subtracting" the  $V_{OL}$  vs  $I_{OL}$  curve from the  $V_{OH}$  vs  $I_{OH}$  curve. On the resulting  $V_{OD}$  vs  $I_O$  curve, draw a load line corresponding to the worst case loading conditions. This will then yield the output differential voltage and output currents being sourced and sunk by the device under a worst case loading condition. A substitution of these quantities into Equation (6) will yield the power being dissipated by the device outputs.

$$(6) \quad PD_{DIFFERENTIAL OUTPUTS} = (\# \text{ of channels}) [I_O (V_{CC} - V_{OD})]$$

As an example, consider the output voltage versus output current curves previously given for the DS26LS31CN (Figures 3 and 4). The  $V_{OD}$  vs  $I_O$  curve for the DS26LS31CN, as illustrated in Figure 5, can be drawn by "subtracting" Figure 4 from Figure 3.

 


FIGURE 4. Low Output Voltage vs Low Output Current vs Temperature

TL/F/11335-4

 


FIGURE 5. Output Differential Voltage vs Output Current vs Temperature

A sample worst case load line of 100Ω superimposed upon Figure 5 reveals the corresponding worst case operating point for the DS26LS31CN; that is, it reveals the device's output differential voltage and output current given a sample worst case output load. When substituted into Equation (6), these voltage and current quantities will yield the worst case power dissipation at the device outputs.

The sum of the worst case quiescent and output power dissipation components will approximate the total worst case device power dissipation.

#### POWER CALCULATION FOR TIA/EIA-485 DIFFERENTIAL LINE DRIVERS

Let's first compare a typical TIA/EIA-422 output structure to a typical TIA/EIA-485 output structure. As shown in Figure 6, the presence of Schottky diodes in the output stage of an TIA/EIA-485 device clearly differentiates it from a similar TIA/EIA-422 device. The addition of the Schottky diodes to the TIA/EIA-485 output stage enable it to safely operate in multipoint (multiple driver) applications over a -7V to +12V common mode range versus the -250 mV to +6V common mode range of TIA/EIA-422. However, the

Schottky diodes in the TIA/EIA-485 outputs have the net effect of raising the value of  $V_{OL}$  by one diode drop and decreasing the value of  $V_{OH}$  by the same amount. This change in output voltage levels will, in turn, affect the amount of power being dissipated in the output stage.

Despite the fact that the output structure of an TIA/EIA-422 line driver differs from that of the TIA/EIA-485 line driver, the procedure outlined earlier to calculate power dissipation is applicable for both TIA/EIA-422 devices and TIA/EIA-485 devices. Quiescent and output power dissipation calculations for an TIA/EIA-485 line driver will again employ Equations (1) and (3) respectively.

As with the sample power calculation for the TIA/EIA-422 device, the sum of the quiescent and output power components will yield the total approximated power dissipated by the TIA/EIA-485 device.

As an example, consider the worst case power dissipation of the DS96F172CJ (ceramic DIP package). Other than the fact that the DS96F172CJ is an TIA/EIA-485 device, it is pin for pin compatible with the DS26LS31CN. As outlined earlier, the first step is to calculate the quiescent power dissipa-

 


FIGURE 6. TIA/EIA-422 and TIA/EIA-485 Output Structures

 


FIGURE 7. High Output Voltage vs High Output Current vs Temperature

TL/F/11335-8

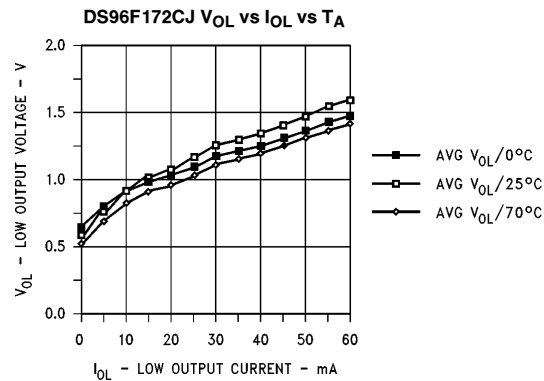


FIGURE 8. Low Output Voltage vs Low Output Current vs Temperature


TL/F/11335-9

tion. From Equation (1), the worst case quiescent power dissipation is:

$$\begin{aligned} PD_{\text{QUIESCENTmax}} &= (V_{CC\text{max}}) (I_{CC\text{max}}) \\ &= (5.25\text{V}) (50\text{ mA}) \\ &= 262.5\text{ mW} \end{aligned}$$

The next step is to calculate the power dissipated at the device outputs under a worst case load condition. Again, there are two ways to do this. First, one can measure the worst case output voltage levels and reference them with *Figures 7 and 8* to extract the corresponding worst case output currents.

A substitution of these resulting quantities into Equation (3) will yield the power dissipated at the device outputs given a worst case load. The second method to calculate output power dissipation involves drawing a worst case load line on the differential output voltage versus output current curve. In the case of the DS96F172CJ, the worst case load line is assumed to be  $60\Omega$ . This assumption was made because in a typical TIA/EIA-485 application, both ends of the transmission line are terminated with  $120\Omega$  and so the TIA/EIA-485 driver is effectively loaded with  $60\Omega$ . In *Figure 9* a  $60\Omega$  load line has been superimposed upon the differential output versus output current curve and consequently, worst case values of output current and differential output voltage (under the given load) have been obtained.

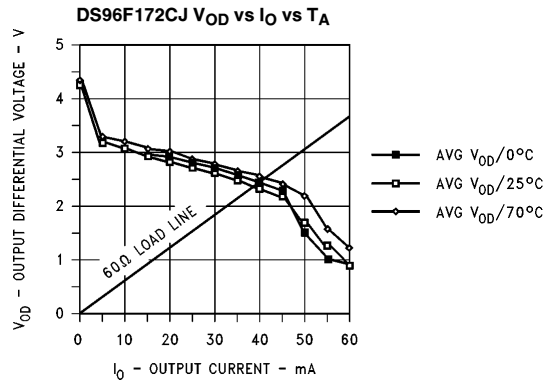

TL/F/11335-10

FIGURE 9. Output Differential Voltage vs Output Current vs Temperature

At room temperature, the worst case power dissipation at the device outputs is (from Equation (6)):

$$\begin{aligned} PD_{\text{DIFFERENTIAL OUTPUTS}} &= \\ &= (\# \text{ of channels}) [I_O (V_{CC} - V_{OD})] \\ &= (4) [39 \text{ mA} (5.25\text{V} - 2.4\text{V})] \\ &= 444.6 \text{ mW} \end{aligned}$$

The only remaining task is to sum together the quiescent and output power dissipation terms to obtain a total worst case power dissipation. From (4), the DS96F172CJ operating at room temperature, under a worst case load of 60Ω, will dissipate:

$$\begin{aligned} PD_{\text{TOTAL}} &= PD_{\text{QUIESCENT}} + PD_{\text{OUTPUTS}} \\ &= 262.5 \text{ mW} + 444.6 \text{ mW} \\ &= 707.1 \text{ mW} \end{aligned}$$

#### PACKAGING AND THERMAL CONSIDERATIONS

Having calculated the total power dissipated by the device, the next logical step is to ascertain that the power dissipated does not thermally damage the device. To do so, the following equation is used:

$$(7) \quad T_J = [PD_{\text{TOTAL}} (\theta_{JA})] + T_A$$

where,  $\theta_{JA}$  = Thermal Resistance from Junction to Ambient (°C/W)

$$\begin{aligned} PD_{\text{TOTAL}} &= \text{Total Power Dissipated by Device (W)} \\ T_J &= \text{Junction Temperature (°C)} \\ T_A &= \text{Ambient Temperature (°C)} \end{aligned}$$

The only variable which remains unknown is  $\theta_{JA}$ .  $\theta_{JA}$  information for the available package types of most devices can be found in the respective device's data sheet. Keep in mind that the data sheet often refers to  $\theta_{JA}$  in terms of derate factors. Determining  $\theta_{JA}$  involves taking the inverse of the derate factor.

$$(8) \quad \theta_{JA} = 1/\text{Derate Factor}$$

For example, all the information is now available for a sample calculation of the DS26LS31CN's junction temperature using the operating conditions specified earlier. The data sheet of the DS26LS31CN specifies a derate factor, for the plastic DIP package, of 11.9 mW/°C. From (8), the  $\theta_{JA}$  is:

$$\begin{aligned} \theta_{JA} &= 1/\text{Derate Factor} \\ &= 1/(0.0119 \text{ W/°C}) \\ &= 84.0 \text{ °C/W} \end{aligned}$$

The thermal resistance from junction to ambient for the DS26LS31CN is now known. Also known are the ambient operating temperature and the total power dissipated (obtained earlier). From (7), the junction temperature is:

$$\begin{aligned} T_J &= [(PD_{\text{TOTAL}}) (\theta_{JA})] + T_A \\ &= [(0.457\text{W}) (84.0\text{°C/W})] + 25\text{°C} \\ &= 63.4\text{°C} \end{aligned}$$

The maximum allowable junction temperature for plastic DIP packages is 150°C. The junction temperature of the DS26LS31CN operating under the conditions specified earlier, by the typical power dissipation calculation, is well within the allowed maximum. Applications where the maximum

allowable junction temperature is exceeded should be avoided since this condition may thermally damage the device and package.

Looking at this thermal analysis from a slightly different perspective, Equation (7) can be rewritten as:

$$(9) \quad P_{DPACKAGE_{max}} = (T_{Jmax} - T_A) / \theta_{JA}$$

By substituting 150°C for the maximum allowable junction temperature, the maximum allowable package power dissipation at 25°C can be calculated using the  $\theta_{JA}$  for the DS26LS31CN plastic DIP (N) package.

$$\begin{aligned} P_{DPACKAGE_{max}} @ 25^\circ C &= (T_{Jmax} - T_A) / \theta_{JA} \\ &= (150^\circ C - 25^\circ C) / 84.0^\circ C/W \\ &= 1.48W \end{aligned}$$

To calculate the maximum allowable package power dissipation at 70°C, the 1.48W maximum at 25°C must be derated using the following procedure:

$$\begin{aligned} (10) \quad P_{DPACKAGE_{max}} @ 70^\circ C &= \\ P_{DPACKAGE_{max}} @ 25^\circ C - (\text{Derate}) (\Delta T_A) &= \\ = 1.48W - (0.0119W/^\circ C) &= \\ (45^\circ C) &= \\ = 0.94W \end{aligned}$$

This sample calculation illustrates that as ambient temperature increases, the DS26LS31CN is able to dissipate less power before the maximum allowable junction temperature specification is violated. Keep in mind that this thermal analysis also applies to TIA/EIA-485 devices such as the DS96F172CJ.

It should be noted that this general thermal analysis is applicable to all other packages and device types assuming that the maximum power dissipation and  $\theta_{JA}$  are known.

## SUMMARY

A method for calculating the total power dissipated by an TIA/EIA-422 driver was presented. This method is also applicable to similar devices conforming to the TIA/EIA-485 standard. Samples calculations for the DS26LS31CN and the DS96F172CJ were presented. Worst case considerations were also discussed. And finally, the relationship between power dissipation and thermal/package limitations was introduced.

## SPECIAL NOTES

*Figure 1* : Ten samples from three data codes.

*Figure 2* : Ten samples from three data codes. Outputs unloaded and  $V_{CC} = 5.0V$ .

*Figures 3, 4, 5* : Ten samples from three data codes.

$$V_{CC} = 5.0V$$

*Figures 7, 8, 9* : Ten samples from two data codes.

$$V_{CC} = 5.0V$$

The graphical data referenced in this application note are not intended to guarantee performance as they only represent typical values.

## REFERENCES

HC-CMOS Power Dissipation, K. Karakotsios, National Semiconductor, 1988 CMOS Logic Data Book, Application Note AN-303.

Understanding Integrated Circuit Package Power Capabilities, C. Carinalli and J. Huljev, National Semiconductor, 1990 Interface Data Book, Application Note AN-336.

**LIFE SUPPORT POLICY**

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, and whose failure to perform, when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.

2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.



**National Semiconductor Corporation**  
1111 West Bardin Road  
Arlington, TX 76017  
Tel: 1(800) 272-9959  
Fax: 1(800) 737-7018

<http://www.national.com>

**National Semiconductor Europe**

Fax: +49 (0) 180-530 85 86  
Email: [europa.support@nsc.com](mailto:europa.support@nsc.com)  
Deutsch Tel: +49 (0) 180-530 85 85  
English Tel: +49 (0) 180-532 78 32  
Français Tel: +49 (0) 180-532 93 58  
Italiano Tel: +49 (0) 180-534 16 80

**National Semiconductor Hong Kong Ltd.**

19th Floor, Straight Block,  
Ocean Centre, 5 Canton Rd.  
Tsimshatsui, Kowloon  
Hong Kong  
Tel: (852) 2737-1600  
Fax: (852) 2736-9960

**National Semiconductor Japan Ltd.**

Tel: 81-043-299-2308  
Fax: 81-043-299-2408

National does not assume any responsibility for use of any circuitry described, no circuit patent licenses are implied and National reserves the right at any time without notice to change said circuitry and specifications.