

CIRCLE 521 EXTEND THE RANGE OF RS485 NETWORKS


CLIVE BOLTON and PACE WILLISSON

Bolton Engineering Inc., 37 Washington St., Melrose, MA 02176. and Blitz Product Development Corp., 4 Spruce Rd., Medway, MA 02053, respectively.

Standard RS485 drivers can be used to implement a collision-based multimaster network much like Ethernet, but at a substantially lower speed and cost. With this circuit, the network's speed can be increased eight-fold.

In a typical setup, the RS485 driver is left tri-stated unless a Space is sent. Resistors pull the network to the resting Mark state. Each station observes the network to make sure that another is not sending before it tries to transmit. However, two stations may observe at the same time that the network is free, and thus attempt to transmit simultaneously.

If more than one station sends simultaneously, the transmitters don't fight each other because only the Space state is driven. The combinations of Spaces being sent at different times garbles the transmission and causes a "collision." Each sender monitors its own transmission to determine whether such a collision has occurred. If there's a collision, the stations wait a random length of time and try to transmit again. The random time is usually determined differently for each station, based on the time since the station was turned on. If several collisions occur in a row, the stations wait

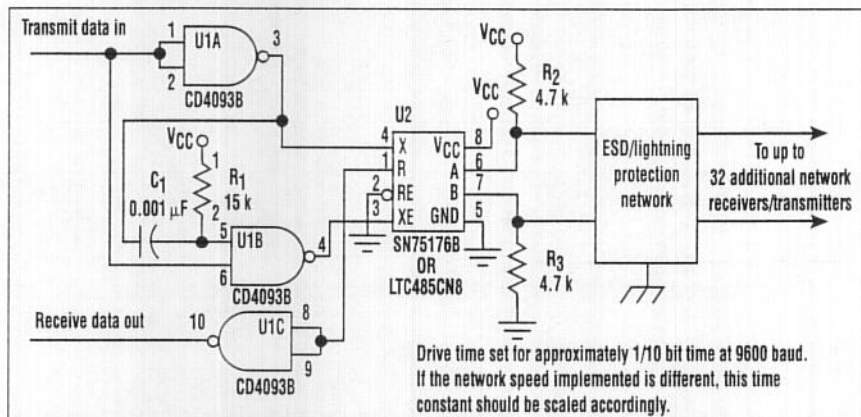

Drive time set for approximately 1/10 bit time at 9600 baud. If the network speed implemented is different, this time constant should be scaled accordingly.

A COLLISION-BASED RS485 NETWORK'S speed can be increased by eight times using this setup. The circuit helps drive the cable to the Mark state by forcing the network driver on for the first 1/10 of a bit time during a Mark. This forces the network back to its resting condition without interfering with collision detection.

exponentially longer until the transmission is successful.

The transmission speed of a collision-based RS485 network is limited by the speed at which the network may return to its undriven Mark state. In a large network, the wiring capacitance can be substantial and the network pull-up and pull-down resistors may not be able to return the cable to the undriven state fast enough for reliable transmission.

The circuit depicted in the figure "helps" drive the cable to the Mark

RS485 specification are designed to withstand indefinite short circuits to either supply rail.

NAND gate U1A inverts the incoming data and U1C inverts the received data. C₁, R₁, and Schmitt trigger U1B extend the network enable signal to drive the network transmitter for one-tenth of a bit time of a Mark. The values shown support 9600-baud network operation. R₂ and R₃ should be selected so that the combined resistance of all network nodes is greater than 60 Ω per side. □

CIRCLE 522 CREATE ULTRA-LOW DROPOUT REGULATOR

CHESTER SIMPSON

National Semiconductor Corp., P.O. Box 58090, C2500, 2900 Semiconductor Dr., Santa Clara, CA 95051.

Portable phones, which typically run off three NiCd cells, ideally require linear regulators that will operate down to a 3-V output with a super low dropout voltage (as low as possible). To answer that call, this circuit

(see the figure) works for output voltages down to 3.0 V at load currents up to 130 mA.

The battery in today's phones provides a nominal voltage of about 3.6 V, but will drop to about 3.2 V at the end of discharge. In addition, most

portable phones are designed using internal regulated rails in the 3-V to 3.3-V range, but require the phone to operate (possibly at reduced performance) as the rail drops down to about 3 V. The low battery voltage sets the dropout voltage requirement at about 150 mV maximum (for

RESULTS OF DROPOUT VOLTAGE TESTING

Q1	V _{drop}
2N3906	144 mV
2N6554	58 mV
MDS77	55 mV